

Important Question

Q.1. Find the overall parameter for series-parallel connection.


Ans. Series Parallel Connection: Two part networks are said to be connected in series parallel if the input ports are connected in series while the output port are connected in parallel as shown below:

$$V_1 = V_{1a} + V_{1b}$$

$$I_1 = I_{1a} = I_{1b}$$

$$V_2 = V_{2a} = V_{2b}$$

$$I_2 = I_{2a} + I_{2b}$$

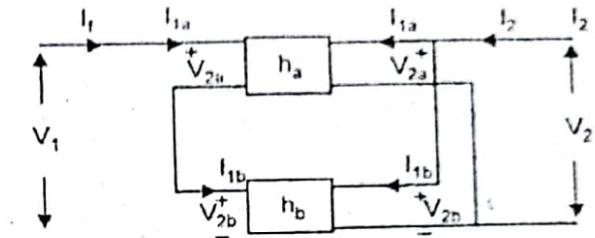

for network 1

$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = \begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ V_{2a} \end{bmatrix}$$

for Network 2

$$\begin{bmatrix} V_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ V_{2b} \end{bmatrix}$$

Now

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{1b} & h_{12b} \\ h_{2b} & h_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{a1a+h11b} & h_{12a+12b} \\ h_{21a+h21b} & h_{22a+22b} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

As we know

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12a+12b} \\ h_{21} & h_{22a+22b} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Now on comparing we get


$$h_{11} = h_{11a} + h_{11b}$$

$$h_{12} = h_{12a} + h_{12b}$$


$$h_{21} = h_{21a} + h_{21b}$$

$$h_{22} = h_{22a} + h_{22b}$$

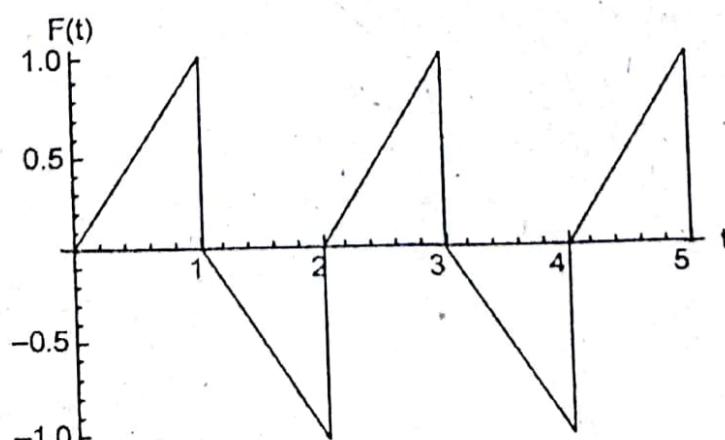Q.2. Find the Laplace of the periodic waveform as shown in Fig.



Ans.

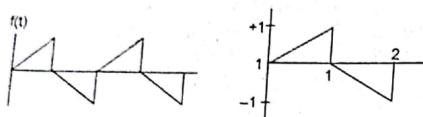

$$\begin{aligned}f(t) &= t[u(t) - u(t-1)] + (-t+1)[u(t-1) - u(t-2)] \\&= tu(t) - tu(t-1) - tu(t-1) + u(t-1) \\&\quad + tu(t-2) - u(t-2) \\&= tu(t) - 2tu(t-1) + u(t-1) + tu(t-2) - u(t-2)\end{aligned}$$

On taking LT

$$= \frac{1}{s^2} - 2e^{-s} \left[t + 1 \right] + \frac{e^{-s}}{s} + e^{-2s}$$

$$\lambda[t+2] - \frac{e^{-2s}}{s}$$

$$F(s) = \frac{1}{s^2} - 2e^{-s} \left[\frac{1}{s^2} + \frac{1}{s} \right] + \frac{e^{-s}}{s} + e^{-2s} \left[\frac{1}{s^2} + \frac{2}{s} \right] \frac{e^{-2s}}{s}$$

As we know for the LT of a periodic function we multiply the term $\frac{1}{1-e^{-Ts}}$ to the LT of the single period of the function.

$$F(s) = \frac{1}{1-e^{-2s}} F'(s)$$

FIRST TERM EXAMINATION THIRD SEMESTER (B. TECH) ETEE-207 CIRCUIT & SYSTEMS-2013

Time : $1\frac{1}{2}$ hrs.

M.M. : 30


Note: Question number 1 is compulsory and attempt any two from the rest.

Q.1. (a) Define even signal and odd signal with examples. (2)

Ans. Even Signal:

$$\text{if } f(-t) = f(t)$$


Then signal is known as even signal.

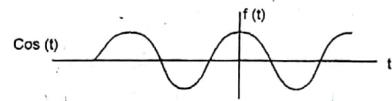e.g.; $\cos(t)$ 

odd signal

$$\text{If } f(-t) = -f(t)$$


then signal is known as odd signal

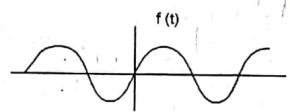
e.g.; $\sin(t)$ 

Q.1. (b) Draw the waveform of (i) $f(t) = 5(t-2)U(t-2)$, (ii) $f(t) = V_m \sin \omega (t - \frac{T}{2})U(t - \frac{T}{2})$. (2)

Ans. (i)

$$f(t) = 5(t-2)u(t-2)$$

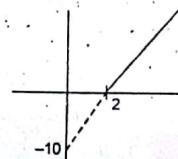

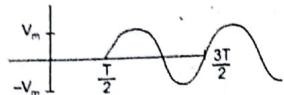

Q.1. (c) Define step, ramp, impulse signal and their Laplace transform. (2)

Ans. Step signal $\begin{cases} A & t \geq 0 \\ 0 & t < 0 \end{cases}$

Step signal $\xrightarrow{LT} \frac{A}{s}$

Ramp signal $r(t) = \begin{cases} At & t \geq 0 \\ 0 & t < 0 \end{cases}$

$r(t) \xrightarrow{LT} \frac{A}{s^2}$

Impulse signal $\delta(t) = \begin{cases} 1 & t = 0 \\ 0 & \text{otherwise} \end{cases}$

$\delta(t) \rightarrow 1$

Q.1. (d) What do you mean by transient response and steady state response of an electrical circuit? (2)

Ans. The value of current and voltage during transient time are known as transient response.

The value of current and voltage after transient time are known as steady state response.

Q.1. (e) Define graph, tree, twigs, and links. (4)

Ans. Graph: A graph is defined as a collection of nodes and branches. It shows the geometrical interconnection of the elements of a network.

Tree: Is defined as any set of branches in the original graph that is just sufficient to connect all the nodes this number is $(n - 1)$.

Twigs: The branch of the tree is known as twigs $n_t = n - 1$.

Link: The branches of the graph which are not in tree form the co-tree complement of the tree.

where

$$n_t = b - n_r = b - n + 1$$

n = total no. of branch in the tree

n_r = no. of twigs

n_l = no. of links

Q.2. (a) Synthesize the waveform using gate signal as shown in Fig. 1.

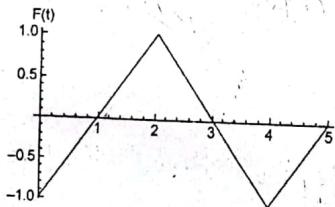


Fig. 1

Ans.

$$x(t) = (t-1)[u(t)-u(t-2)] \\ + (-t+3)[u(t-2)-u(t-4)] \\ + (t-5)[u(t-4)-u(t-5)]$$

Q.2. (b) Find the Laplace of the periodic waveform as shown in Fig. 2. (3)

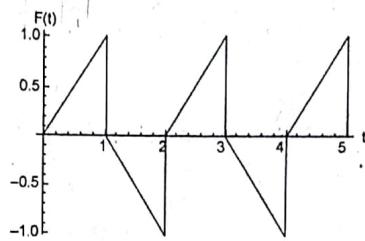


Fig. 2

Ans.2.(b) Refer Q. No. 2 ; Important question page 119

Q.2. (c) Find the initial values of inductor and capacitor as shown in figure 3. (3)

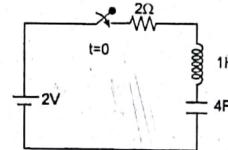


Fig. 3

Ans. $t = 0^+$

Capacitor behave as a short circuit & inductor behave as open circuit.

$$V_C = 0$$

$$V_L = 2V$$

Q.3. (a) For R-L circuit, when switch was closed at $t = 0$, (steady state) $= 10 \cos(\omega t - 60^\circ)$. The supply voltage is having a value $v = 80 \cos(\omega t)$. Find $i(t)$ in fig. 4.

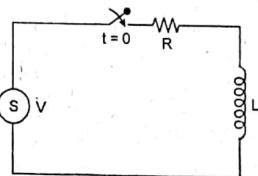


Fig. 4

Ans.

$$V = iR + L \frac{di}{dt}$$

$$\begin{aligned}
 \frac{di}{dt} + \frac{iR}{L} &= \frac{V}{L} \\
 CF &= Ae^{\frac{Rt}{L}} \\
 PI &= \frac{80\cos wt}{D + \frac{R}{L}} \\
 &= \frac{80\cos wt}{D^2 - \left(\frac{R}{L}\right)^2} \left(D - \frac{R}{L} \right) \\
 &= \frac{(80\cos wt)\left(D - \frac{R}{L}\right)}{-w^2 - \left(\frac{R}{L}\right)^2} \\
 &= \frac{1}{-\left(w^2 + \left(\frac{R}{L}\right)^2\right)} \left(D - \frac{R}{L} \right) 80\cos wt \\
 &= \frac{1}{-\left(w^2 + \left(\frac{R}{L}\right)^2\right)} \left\{ -80w\sin wt - \frac{R}{L} 80\cos wt \right\} \\
 &= \frac{1}{-\left(w^2 + \left(\frac{R}{L}\right)^2\right)} \left\{ -80w\sin wt - \frac{R}{L} 80\cos wt \right\}
 \end{aligned}$$

$$i(t) = CF + PI$$

$$i(t) = Ae^{\frac{Rt}{L}} - \frac{1}{\left(w^2 + \left(\frac{R}{L}\right)^2\right)} \left\{ -80w\sin wt - \frac{R}{L} 80\cos wt \right\}$$

at

$$t = 0, i = 10 \cos(wt - 60)$$

Putting this value in $i(t)$

We get


$$A = 10\cos(wt - 60) - \frac{80R}{w^2 + \left(\frac{R}{L}\right)^2} L$$

Putting the value of A in equation of $i(t)$.

We get final $i(t)$.

$$\begin{aligned}
 i(t) &= \left\{ 10\cos(wt - 60) - \frac{80R}{w^2 + \left(\frac{R}{L}\right)^2} z \right\} e^{\frac{Rt}{L}} \\
 &\quad - \frac{1}{\left(w^2 + \left(\frac{R}{L}\right)^2\right)} 80w\sin wt - \frac{R80}{L} \cos wt
 \end{aligned}$$

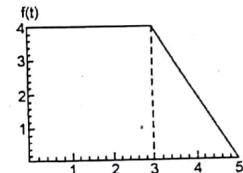Q.3. (b) Determine the Laplace transform of the following waveform as shown in figure 5.



Ans.

$$f(t) = [u(t) - u(t-3)] + (-t+5)[u(t-3) - u(t-5)]$$

$$u(t) \rightarrow \frac{1}{s}$$

$$u(t-3) \rightarrow \frac{e^{-3s}}{s}$$

$$- (t-3)u(t-3) + 2u(t-3) + (t-5)u(t-5)$$

$$- \frac{e^{-3s}}{s^2} + 2 \frac{e^{-3s}}{s} + \frac{e^{-5s}}{s^2}$$

$$F(s) = \frac{1}{s} - \frac{e^{-3s}}{s} - \frac{e^{-5s}}{s^2} + \frac{2e^{-3s}}{s} - \frac{e^{-5s}}{s^2}$$

Q.3. (c) Find the value of $F(0)$ and $f(\infty)$ for $\frac{7s+1}{s(s+2)}$.

Ans. Using Initial Value Theorem

$$F(0) = \lim_{s \rightarrow \infty} sF(s)$$

$$= \lim_{s \rightarrow \infty} \frac{s(7s+1)}{s(s+2)} = \lim_{s \rightarrow \infty} \frac{7s+1}{s+2} = 7$$

$F(\infty)$ final value theorem


$$F(\infty) = \lim_{s \rightarrow 0} sF(s)$$

$$= \lim_{s \rightarrow 0} \frac{s(7s+1)}{s(s+2)} = \frac{1}{2}$$

Q.4. (a) For the given the complete incidence matrix form the graph. (3)

$$A_c = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ a & 1 & 0 & 1 & -1 & 0 \\ b & -1 & 1 & 0 & 1 & 0 \\ c & 0 & -1 & 0 & 0 & -1 \\ d & 0 & 0 & -1 & 0 & 1 \end{bmatrix}$$

Ans.

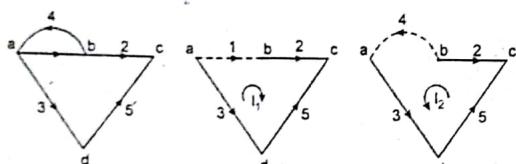

Q.4. (b) Find out the fundamental tie-set matrix $[B_f]$ considering twigs as (3, 5, 2). (4)

$$\text{Ans. } B_f = \begin{array}{c|ccccc} \text{Branch} & 1 & 2 & 3 & 4 & 5 \\ \hline l_1 & 1 & 1 & -1 & 0 & -1 \\ l_2 & 0 & -1 & 1 & 1 & 1 \end{array}$$

Q.4. (c) Write the properties of complete incidence matrix. (3)

Ans. Properties of complete incidence matrix:

- (i) Sum of the entries in any column is zero.
- (ii) The rank of a complete incidence matrix of a connected graph is $n-1$.
- (iii) The determinant of a complete incidence matrix is always zero.

Q.4. (d) State super position theorem with its limitations.

Ans. Super position theorem: In an active linear network containing several source (including dependent sources). The overall response in any branch in the network equals the algebraic sum of the responses of each individual source considered separately with all other sources made inoperative, i.e., replaced by their internal resistance or impedance.

Limitations:

- (i) Not applicable to ckt consisting of only dependent sources
- (ii) Not applicable to the ckt consisting of non linear elements like diode, transistor etc.
- (iii) Not applicable for calculation of power
- (iv) Not useful to the circuits consisting of less than two independent sources.

SECOND TERM EXAMINATION THIRD SEMESTER (B. TECH) ETEE-207 CIRCUIT & SYSTEMS-2013

Time : $1\frac{1}{2}$ hrs.


M.M. : 30

Note: Question number 1 is compulsory and attempt any two from the rest.

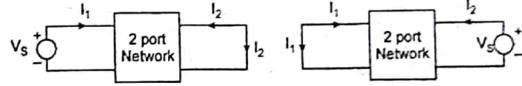Q.1. (a) Find the condition of Reciprocity for Y parameter. (2)

Ans.

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \\ V_1 &= V_s, I_1 = I_2, V_2 = 0, I_2 = -I'_2 \end{aligned}$$



Putting this value in above eqn. we get

$$\begin{aligned} I'_2 &= -Y_{21}V_s \\ V_2 &= V_s, I_2 = I'_2, V_1 = 0, I_1 = -I'_1 \end{aligned}$$

Putting the value in above eqn. we get

$$I'_1 = -Y_{12}V_s$$


Now comparing I'_2 & I'_1

$$Y_{12} = Y_{21}$$

Q.1. (b) Find the overall parameter for series-parallel connection. (2)

Ans.1. (b) Refer Q. No.1 ; Important Question page 119

Q.1. (c) Derive the condition for maximum power transfer for the circuit given in Fig. 1. (2)

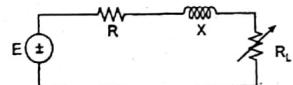

Ans.1. (c) Refer Q. No.4(c) ; Second term 2013

Q.1. (d) State the Superposition Theorem.

Ans.1. (d) Refer Q. No.4(d) ; First term 2013

Q.1. (e) Draw equivalent circuit of inverse transmission parameter. (2)


Ans. $(V_2, I_2) = f(V_1, I_1)$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

$$V_2 = A'V_1 + B'(-I_1)$$

$$I_2 = C'V_1 + D'(-I_1)$$

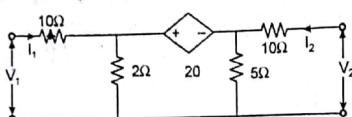Q.2. (a) Find out the Y parameters for the network given in fig. 2. (5)



Ans.

$$V_1 = Y_{11}I_1 + Y_{12}I_2$$

$$V_2 = Y_{21}I_1 + Y_{22}I_2$$

Note: There is some mistake in this Question

Represent dependent source
but here it does not depend
on any parameter

Q.2. (b) Derive the relationship for the conversion of Y parameter to inverse h parameter; and find the inverse hybrid parameter. (8)

Ans.

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \dots(1)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \dots(2)$$

Rewriting equation (1) we get

$$I_1 = \frac{1}{h_{11}}V_1 - \frac{h_{12}}{h_{11}}V_2 \quad \dots(3)$$

$$Y_{11} = \frac{1}{h_{11}} \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$


Putting the value of I_1 in equation 2

$$I_2 = h_{21} \left[\frac{1}{h_{11}}V_1 - \frac{h_{12}}{h_{11}}V_2 \right] + h_{22}V_2 \quad Y_{21} = \frac{h_{21}}{h_{11}}$$

$$Y_{22} = \frac{\Delta h}{h_{11}}$$

$$I_2 = \frac{h_{21}}{h_{11}}V_1 + \frac{\Delta h}{h_{11}}V_2$$

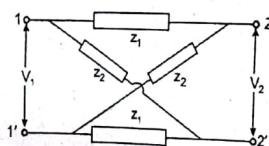Q.3. (a) Show that $Z_{12} = Z_{21}$ for the network given in fig. 3. (5)



Ans. This is a symmetrical circuit So

$$Z_{12} = Z_{21}$$

Applying KVL at loop abd, bdc, abdc

$$V_1 = Z_{11}I' + Z_{21}(I' + I_2) \quad \dots(1)$$

$$V_2 = Z_{21}(I' + I_2) + Z_{12}(I' + I_2 - I_1) \quad \dots(2)$$

$$Z_{11}I' + Z_{21}(I' + I_2) + Z_{12}(I' + I_2 - I_1) - Z_{21}(I_1 - I') = 0 \quad \dots(3)$$

$$I' = \frac{I_1 - I_2}{2} \quad \dots(4)$$


Putting the value of I' in equation (1) and (2) we get

$$V_1 = \frac{Z_1 - Z_2}{2} I_1 + \frac{Z_2 - Z_1}{2} I_2$$


$$V_2 = \frac{Z_2 - Z_1}{2} I_1 + \frac{Z_1 + Z_2}{2} I_2$$

$$Z_{12} = Z_{21}$$

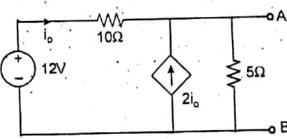Q.3. (b) Determine the Thevenin's equivalent circuit across AB in fig. 4.(5)



Ans.

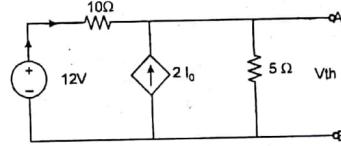


for I_N short AB

$$10I_0 = 12$$

$$I_0 = \frac{12}{10} = 1.2A$$

$$I_N = I_0 + 2I_0 = 3I = 3 \times 1.2 = 3.6A$$

$$10I_0 + 5 \times 3I_0 = 12$$

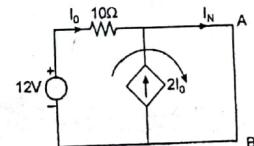


$$V_0 = \frac{12}{25}$$

$$V_{th} = 5 \times \frac{12}{25} = \frac{12}{5} = 2.4$$


$$R_{th} = \frac{2.4}{1.2} = 2\Omega$$

Q.4. (a) Using Superposition theorem, find the voltage across $(1 + 2j)$ impedance in network as shown in fig. 5. (5)

Ans.

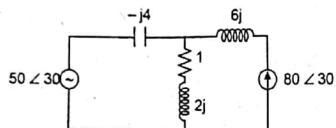


Case 1 : Short Voltage Source

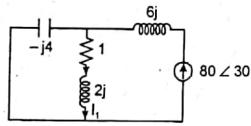

Applying current division rule current I_1

$$I_1 = \frac{-j4}{1+2j-4j} I = \frac{-j4}{1-j2} 80 \angle -30$$

Case 2 : Open the current source

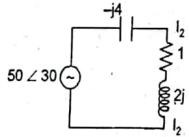


$$I_2 = \frac{50 \angle 30}{1+2j-4j} = \frac{50 \angle 30}{1-2j}$$

Total Current

$$I = I_1 + I_2$$


$$V = I(1+2j)$$

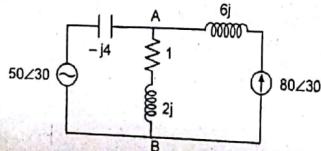Q.4. (b) Determine the Norton's equivalent impedance between point A and B. Draw Norton's equivalent circuit shown in fig. 5. (5)




Ans.

Case 1 : Short voltage source

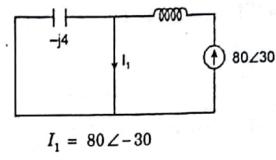

$$I_1 = 80 \angle -30$$

Case 2 :

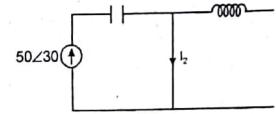

$$I_2 = \frac{50 \angle 30}{-4j}$$


$$I_N = 80L-30 + \frac{50 \angle 30}{-4j}$$

$$V_{th} = 50 \angle 30 - (-j4 \times 80 \angle -30)$$

Q.4. (c)

Find the condition for maximum power transfer for the circuit fig. 1(c).

Ans.

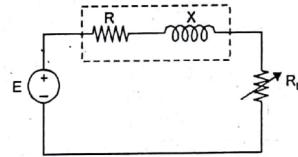

$$I = \frac{E}{R + jx + R_L}$$

$$\text{Power } P = I^2 R_L = \left(\frac{E}{R + jx + R_L} \right)^2 R_L$$

$X = 0$ } Condition for maximum power transfer
 $R_L = R$ }

**END TERM EXAMINATION
THIRD SEMESTER (B. TECH) ETEE-207
CIRCUIT & SYSTEMS-2013**


M.M.: 75

Time : 3 hrs.

Note: Attempt any five questions including Q.no. 1 which is compulsory.

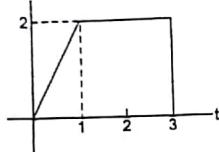Q.1. (a) Draw the waveform of the signal $V(t) = 2t u(t) - 2(t-1) u(t-1) - 2 u(t-3)$. (5)

Ans. $2t u(t) - 2(t-1) u(t-1) - 2 u(t-3)$



Q.1. (b) The transfer function of a network is given by $\frac{V(s)}{I(s)} = \frac{(s+3)}{(s+2)(s+4)}$. (5)

For a unit step input, find the steady state value of $v(t)$.

Ans. If $I(s)$ is input then

$$V(s) = \frac{(s+3)}{(s+2)(s+4)} \times I(s)$$

Input is $U(t)$

$$I(s) = \frac{1}{s}$$

$$V(s) = \frac{(s+3)}{(s+2)(s+4)s}$$

$$V(s) = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+4}$$

$$A = \frac{(s+3)}{(s+2)(s+4)s} \times (s+2) \Big|_{s=0} = \frac{3}{8}$$

$$B = \frac{s+3}{(s+2)(s+4)s} \times (s+2) \Big|_{s=-2}$$

$$= \frac{1}{-2 \times 2} = -\frac{1}{4}$$

$$C = \frac{s+3}{(s+2)(s+4)s} \times (s+4) \Big|_{s=-4}$$

$$= \frac{-1}{-2 \times -4} = -\frac{1}{8}$$

I.P. University-(B.Tech)-Akash Books

133

$$V(s) = \frac{3}{85} + \left\{ -\frac{1}{4(s+2)} \right\} - \frac{1}{8} \left(\frac{1}{s+4} \right)$$

taking ILT

$$V(t) = \frac{3}{8} u(t) - \frac{1}{4} e^{-2t} u(t) - \frac{1}{8} e^{-4t} u(t)$$

Q.1. (c) In a two terminal network, the open circuit voltage at the load terminal is 125V and the short circuit at the same terminal gives 25A current. Determine the value of maximum power transfer which can take place at the load terminal. (5)

Ans.

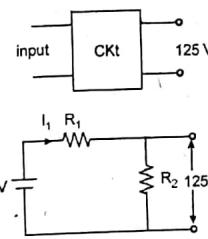


Fig. 1

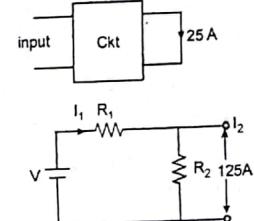


Fig. 2

$$I_1 = \frac{V}{R_1 + R_2}, V_{out} = \frac{V}{R_1 + R_2} \times R_2 = 125 \quad \dots(1)$$

for fig. 2

$$I_2 = \frac{V}{R_1} = 25 \quad \dots(2)$$

From equation 1 & 2

$$\frac{\sqrt{R_2}}{R_1 + R_2} = \frac{125}{25} \rightarrow \frac{R_1 R_2}{R_1 + R_2} = 5$$

For maximum power transfer.

Q.1. (d) Find the current i_r through the $1\text{k}\Omega$ resistor of Fig. 1 at $t = 1\text{sec}$, If $i_r(0^*) = 6\text{A}$. (5)

Ans.

$$L \frac{dI_r}{dt} + I_r R = 0$$


$$50 \times 10^{-9} \frac{dI_r}{dt} + I_r 1 \times 10^3 = 0$$

$$\frac{dI_r}{dt} + \frac{1}{50} \times 10^{12} I_r = 0$$

$$\frac{dI_r}{dt} + 10^{10} I_r = 0$$

$$I_r = A e^{-10^{10} t}$$

at $t = 0, I_r = 6\text{A}$

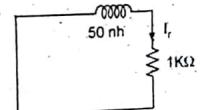


... (1)

Putting this value in equation 1,
 $A = 6$

$$\begin{aligned} I_r &= 6e^{-10^9 t} \\ \text{at } t &= 1 \times 10^{-9} \text{ s} \\ I_r &= 6e^{-10^{10} \times 10^{-9}} \\ &= 6e^{-1} = \frac{6}{e} \end{aligned}$$

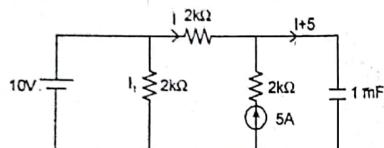Q.1. (e) Obtain the time constant for the network shown in Fig. 2.



Ans.
Applying kLI

$$10 = 2000I + \frac{1}{C} \int (I+5) dt$$

On differentiating we get

$$0 = 2000 \frac{dI}{dt} + 1000(I+5)$$

$$\frac{2dI}{dt} + I + 5 = 0$$

$$\frac{dI}{dt} + \frac{I}{2} = -\frac{5}{2}$$

$$CF = Ae^{-\frac{1}{2}t}$$


$$PI = -5$$

$$I = Ae^{-\frac{1}{2}t} - 5$$

Time constant


$$T = 2 \text{ sec}$$

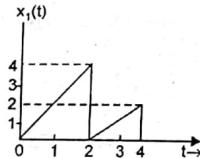Q.2. (a) Write the equation for the waveforms shown in Fig. 3(a) & (b) (6)




$$\text{Ans. } x_1(t) = 2t[u(t) - u(t-2)] + t - 2[u(t-2) - u(t-4)]$$
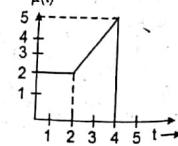
$$x_2(t) = [u(t) - u(t-2)] + \left[\frac{3}{2}t - 1 \right] [u(t-2) - u(t-4)]$$




Q.2. (b) Draw the directed graph and obtain the incidence matrix for the network shown in Fig. 4. (6.5)

Ans.

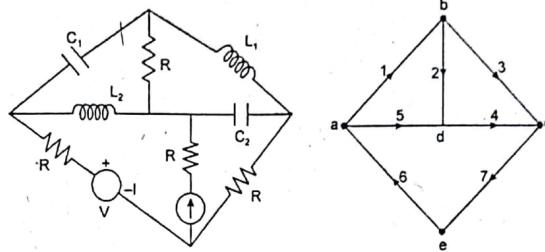

	1	2	3	4	5	6	7
a	1	0	0	0	1	-1	0
b	-1	1	1	0	0	0	0
c	0	0	-1	-1	0	0	1
d	0	-1	0	1	-1	0	0
e	0	0	0	0	0	1	-1

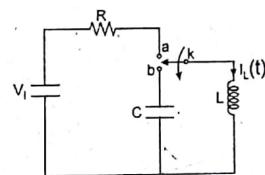Q.3. (a) The switch k (Fig. 5) is the steady state position a for $t < 0$. At $t = 0$, it is connected to position b. Find the expression for current $i_L(t)$, for $t > 0$. (6)



Ans. at $t = (0^-)$
Inductor work as short circuit

$$L = \frac{V_1}{R}$$

at $t = 0^+$

$$\frac{1}{c} \int_0^t i(t) + L \frac{di(t)}{dt} = 0$$


taking LT of equation (1)

$$\frac{1}{cs} I(s) + L \left[sI(s) - b_L(0^+) \right] = 0$$

$$\left(\frac{1}{Cs + Ls} \right) I(s) = L \frac{v_1}{R}$$

$$I(s) = \frac{LV_1/R}{(1+LCs^2)/Cs} = \frac{V_1}{R} \left(\frac{s}{s^2 + \frac{1}{LC}} \right)$$

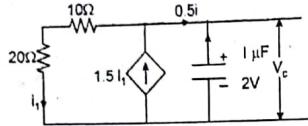Q.3. (b) Find expressions for $v_c(t)$ for $t > 0$ if $V_c(0^+) = 2V$.



Ans.

$$C \frac{dv}{dt} = \frac{V_c}{30} + 1.5 \frac{V_c}{30}$$

$$C \frac{dv}{dt} = \frac{V_c}{30} + \frac{V_c}{20}$$

$$C \frac{dv}{dt} = \frac{5\beta}{30 \times 2\beta} V_c = \frac{5}{60} V_c$$

$$C_s V(s) - 2 = \frac{5}{60} V_c s$$

$$V_s \left(sC - \frac{5}{60} \right) = 2 \Rightarrow V_s(s) = \frac{2}{sC - \frac{5}{60}}$$

$$V(s) = \frac{2}{1 \times 10^{-6}s - \frac{5}{60}}$$

$$= \frac{2}{10^{-6} \left(s - \frac{5}{60 \times 10^{-6}} \right)}$$

$$= 2 \times 10^6 \frac{1}{\left(s - \frac{5}{6 \times 10^{-5}} \right)}$$

$$= 2 \times 10^6 e^{\left(\frac{5}{6 \times 10^{-5}} t \right)}$$

Q.4. (a) For a unit step input, find the forced and natural responses of the system described by

$$\frac{d^2y(t)}{dt^2} + 6 \frac{dy(t)}{dt} + 2y(t) = 3 \frac{dx(t)}{dt} + 9x(t),$$

the initial conditions of the system are $y(0^+) = 1$ and $y'(0^+) = 2$.

(6.5)

$$\text{Ans. } \frac{d^2y(t)}{dt^2} + 6 \frac{dy(t)}{dt} + 2y(t) = 3 \frac{dx(t)}{dt} + 9x(t)$$

$$s^2 Y(s) - sy(0) - y'(0) + 6sY(s) - 6y(0) + 2y(s)$$

$$= 3[sX(s) - x(0^+)] + 9X(s)$$

$$s^2 Y(s) - s - 2 + 6sY(s) - 6 + 2Y(s) = 3sX(s) + 9X(s)$$

$$\text{given } x(t) = u(t)$$


$$X(s) = \frac{1}{s}$$

$$Y(s)[s^2 + 6s + 2] = 3s \times \frac{1}{s} + \frac{9}{s} + s + 8$$

$$= \frac{s^2 + 11s + 9}{s}$$

$$Y(s) = \frac{s^2 + 11s + 9}{s(s^2 + 6s + 2)}$$

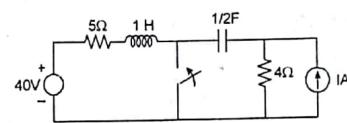Q.4. (b) The circuit shown in Fig. 7 achieved steady state before switching and at $t = 0$ the switch k is closed. Determine the expression for the current $i(t)$. (6)



Ans.

Applying KVL in loop 1

$$40 = 5i + L \frac{di}{dt} \quad L = 1H$$

$$40 = 5i + \frac{di}{dt}$$

$$CF = Ae^{-5t} \quad PI = \frac{40}{5} = 8$$

$$i_1 = Ae^{-5t} + 8$$

$$t = 0 \quad i = 0$$

$$A = -8$$

$$i_1 = -8e^{-5t} + 8$$

Applying KVL in loop 2

$$40 = \frac{1}{C} \int i_2 dt + i_2 4$$

On differentiating we get

$$0 = \frac{1}{C} i_2 + 4 \frac{di_2}{dt} \quad C = \frac{1}{2}$$


$$2i_2 + 4 \frac{di_2}{dt} = 0$$

$$\frac{di_2}{dt} + \frac{1}{2} i_2 = 0$$

$$i_2 = Be^{-\frac{1}{2}t}$$

$$\text{at } t = 0 \quad i_2 = \frac{40}{4} = 10$$


Putting this value in

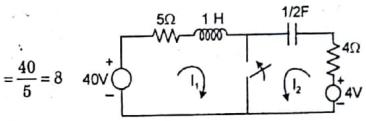

Putting the value in above eqn.
We get $B = 10$

$$\begin{aligned} i_2 &= 10e^{\frac{-t}{2}} \\ i &= i_1 + i_2 \\ &\approx -8e^{-\frac{t}{2}} + 8 + 10e^{\frac{-t}{2}} \end{aligned}$$

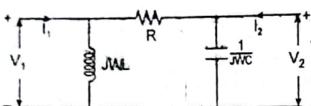Q.5. (a) Determine the T-parameters for the network shown in Fig. (6)



Ans. Apply KCL at node (B)

$$I_2 = V_2 jwC + \frac{V_2 - V_1}{R}$$

$$V_1 = (1 + jwCR)V_2 + R(-I_2)$$

Applying KCL at node (A)

$$I_1 = \frac{V_1 + V_2 - V_2}{jwL}$$

$$I_1 = V_1 \left(\frac{1}{jwL} + \frac{1}{R} \right) - \frac{V_2}{R}$$

Putting the value of V_1 in above eqn.

$$\begin{aligned} I_1 &= \frac{R + jwL}{jwRL} \{ [1 + jwCR]V_2 - RI_2 \} - \frac{V_2}{R} \\ &= V_2 \left[\frac{(R + jwL)(1 + jwCR)}{jwRL} - \frac{1}{R} \right] - R \frac{jwL}{jwRL} \end{aligned}$$

$$A = 1 + jwCR$$

$$B = R$$

$$C = \frac{C}{L} \left\{ jwL + R + \frac{1}{jwC} \right\}$$

$$D = 1 + \frac{R}{jwL}$$

Q.5. (b) Determine the relationship for conversion of Y parameter to h-parameter. Find the conditions for symmetry in terms of h parameters. (6.5)

Ans.

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad (1)$$

$$I_1 = h_{21}I_2 + h_{22}V_2 \quad (2)$$

$$I_1 = \frac{1}{h_{11}}V_1 - \frac{h_{12}}{h_{11}}V_2$$

$$Y_{11} = \frac{1}{h_{11}}, \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

Putting the value of I_1 in equation (2)

$$\begin{aligned} I_2 &= h_{21} \left[\frac{1}{h_{11}}V_1 + \frac{\Delta h}{h_{11}}V_2 \right] + h_{22}V_2 \\ &= \frac{h_{21}}{h_{11}}V_1 + \frac{\Delta h}{h_{11}}V_2 \\ Y_{21} &= \frac{h_{21}}{h_{11}}, \quad Y_{22} = \frac{\Delta h}{h_{11}} \end{aligned}$$

Condition for symmetry

Case I

$$V_1 = V_s I_1 = I_1 I_2 = 0, \quad V_2 = V_2$$

$$V_s = h_{11}I_1 + h_{12}V_2$$

$$0 = h_{21}I_1 + h_{22}V_2$$

$$\frac{V_s}{I_1} = \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{22}}$$

Case II

$$V_2 = V_2 I_2 = I_2 I_1 = 0, \quad V_1 = V_1$$

$$V_1 = h_{12}V_s$$

$$I_2 = h_{22}V_s \text{ or } \frac{V_s}{I_2} = \frac{1}{h_{22}}$$

On equating both we get

$$h_{11}h_{22} - h_{12}h_{21} = 1$$

$$\Delta h = 1$$

Q.6. (a) A voltage source V_1 whose internal impedance is $R_1 + jX_1$ delivers power to a load R_2 , where R_2 is variable. Find the value of R_2 at which the power delivered to the load is a maximum. (5)

Ans. 6.(a) Out of syllabus

Q.6. (b) State Norton's theorem. Obtain the Thevenin's and Norton's equivalent of the network across the terminal AB as shown in Fig. 9. (all element values are in ohm).

(7.5) Ans. Vth is voltage across $(3 + j4)\Omega$

$$\begin{aligned} V_{th} &= \frac{10}{3 + j4 + 10} (3 + j4) \\ &= 3.67 [36^\circ] V \end{aligned}$$

$$Z_{th} = [10(11 + 3 + j4)] + (-j10)$$

$$= \frac{(3 + j4)10}{10 + 3 + j4} - j10$$

$$= 8.38 \angle -69.3^\circ \Omega$$


$$I_n = \frac{V_{th}}{Z_{th}} = \frac{3.67 [36^\circ]}{8.38 \angle -69.3^\circ}$$

$$= .438 [105.3^\circ]$$

$$Z_{th} = Z_N$$

Q.7. (a) Test whether the polynomial $F(s) = 4s^4 + 2s^3 + 5s^2 + 3s + 2$ is Hurwitz or not. (4)

Ans. $4s^4 + 2s^3 + 5s^2 + 3s + 2$

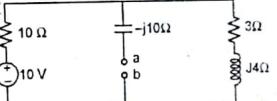

$$\begin{aligned}
 M(s) &= 4s^4 + 5s^2 + 2 \\
 N(s) &= 25s^3 + 3s \\
 2s^3 + 3s &\overline{(4s^4 + 5s^2 + 2)} \\
 &\underline{+ 4s^4 + 6s^2} \\
 &\overline{s^2 + 2} \quad 2s^3 + 3s + 2(-2s) \\
 &\underline{+ 2s^3 + 4s} \\
 &\overline{7s} \quad -s^2 + 2\left(-\frac{1}{7}s\right) \\
 &\underline{-s^2} \\
 &\overline{2} \quad 7s\left(\frac{7}{2}s\right) \\
 &\underline{7s} \\
 &\times
 \end{aligned}$$

-ve coefficient.
Not Hurwitz.

Q.7. (b) For the LC driving point impedance function $Z_D(s) = \frac{(s^2 + 1)(s^2 + 16)}{s(s^2 + 4)}$ (8.5)

synthesize in Foster-I and Cauer-II form.


Ans. $Z_D = \frac{(s^2 + 1)(s^2 + 16)}{s(s^2 + 4)} = \frac{s^4 + 17s^2 + 16}{s^3 + 4s}$

Foster-I

$$\begin{aligned}
 s^3 + 4s &\overline{s^4 + 17s^2 + 16} \\
 &\underline{-s^4 \pm 4s^2} \\
 &\overline{13s^2 + 16} \\
 &= s + \frac{13s^2 + 16}{s^3 + 4s} = s + \frac{13s^2 + 16}{s(s^2 + 4)} \\
 &= s + \frac{A}{s} + \frac{Bs + c}{s^2 + 4} \\
 Bs^2 + As^2 &= 13s^2 \\
 A &= \frac{13s^2 + 16}{s(s^2 + 4)} \Big|_{s=0} \\
 &= 4 \\
 B &= 9 \\
 C &= 0
 \end{aligned}$$

$$\begin{aligned}
 s + \frac{4}{s} + \frac{9s}{s^2 + 4} \\
 \downarrow & \\
 \text{LS } \frac{1}{CS} & \quad \frac{\frac{1}{s}}{s^2 + \frac{1}{L}}
 \end{aligned}$$

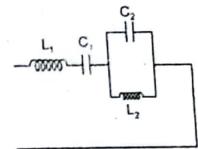
$$\begin{aligned}
 L_1 &= 1 \quad C_2 = \frac{1}{9} \\
 C_1 &= \frac{1}{4} \quad L_2 C_2 = \frac{1}{4} \\
 L_2 &= \frac{9}{4}
 \end{aligned}$$



Cauer-II

$$\begin{aligned}
 s^3 + 4s &\overline{s^4 + 17s^2 + 16} \\
 &\underline{-s^4 + 4s^2} \\
 &\overline{13s^2 + 16} \quad s^3 + 4s \quad \left(\frac{1}{13}s \leftrightarrow y_1 \right) \\
 &\underline{-s^3 + \frac{16}{13}s} \\
 &\overline{\frac{36}{13}s} \quad 13s^2 + 16 \quad \left(\frac{169}{36}s \right. \\
 &\underline{-13s^2} \\
 &\overline{16} \quad \left. \frac{36}{13}s \right)
 \end{aligned}$$
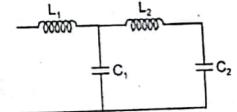
$$\begin{aligned}
 16 &\overline{\frac{36}{13}s} \quad \left(\frac{36}{13} \times 16 \right. s \rightarrow y_2 \\
 &\underline{\frac{36}{13}} \\
 &\times \\
 &s \rightarrow z_1 \\
 &z = L_1 s \\
 &L_1 = 1 \\
 &\frac{1}{13}s \rightarrow y_1 \\
 &c_1 s \\
 &c_1 = \frac{1}{13}
 \end{aligned}$$



$$\frac{169}{36}s \rightarrow z_2$$


$$\begin{aligned}
 L_2 s \\
 L_2 = \frac{169}{36}
 \end{aligned}$$

$$\frac{36}{13 \times 16}s \rightarrow y^2$$

$$\begin{aligned}
 C_2 s \\
 C_2 = \frac{36}{13 \times 16}
 \end{aligned}$$

For New Syllabus Circuit & System

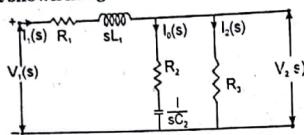Q. For the circuit shown in figure. Determine the network transfer function.



Ans. The network equation are

$$\begin{aligned} V_2(s) &= R_2 I_2(s) \\ &= \left(R_2 + \frac{1}{sC_2} \right) I_0(s) \end{aligned} \quad \dots(1)$$

$$\text{or } I_0(s) = \frac{V_2(s)}{R_2 + \frac{1}{sC_2}} \quad \dots(2)$$

$$I_1(s) = I_2(s) + I_0(s)$$

$$V_1(s) = V_2(s) + (R_1 + sL_1) I_1(s)$$

Transfer impedance function,

$$\begin{aligned} Z_{21}(s) &= \frac{V_2(s)}{I_1(s)} \\ V_2(s) &= \left(R_2 + \frac{1}{sC_2} \right) I_0(s) \\ I_1(s) &= I_2(s) + I_0(s) = I_0(s) \left[\frac{I_2(s)}{I_0(s)} + 1 \right] \\ &= I_0(s) \left[\frac{R_2}{R_2 + \frac{1}{sC_2}} + 1 \right] \end{aligned} \quad \text{[From Equation (1)]}$$

$$Z_{21}(s) = \frac{R_2 (sC_2 R_2 + 1)}{C_2 (R_2 + R_3)s + 1}$$

(ii) Transfer admittance function,

$$\begin{aligned} Y_{21}(s) &= \frac{I_2(s)}{V_1(s)} \\ V_1(s) &= V_2(s) + (R_1 + sL_1) I_1(s) \\ &= R_3 I_2(s) + (R_1 + sL_1)[I_2(s) + I_0(s)] \end{aligned} \quad \text{[From Equations (1) and (3)]}$$

$$\begin{aligned} &= I_2(s) \left[R_3 + (R_1 + sL_1) + (R_1 + sL_1) \left(\frac{R_2}{R_2 + \frac{1}{sC_2}} \right) \right] \\ &= I_2(s) \left[\frac{(R_3 + R_1 + sL_1)(sC_2 R_2 + 1) + (R_1 + sL_1) R_3 s C_2}{(sC_2 R_2 + 1)} \right] \end{aligned}$$

$$Y_{21}(s) = \frac{sC_2 R_2 + 1}{L_1 C_2 (R_2 + R_3)s^2 + [C_2 (R_1 R_2 + R_2 R_3 + R_3 R_1) + L_1]s + (R_1 + R_3)}$$

(iii) Voltage transfer function,

$$G_{21}(s) = \frac{V_2(s)}{V_1(s)} = \frac{V_2(s)}{I_1(s)} \cdot \frac{I_2(s)}{V_1(s)} \cdot \frac{I_1(s)}{I_2(s)} = Z_{21}(s) \cdot Y_{21}(s) \cdot \frac{I_1(s)}{I_2(s)}$$

$$I_1(s) = I_2(s) + I_0(s) = I_2(s) \left[1 + \frac{I_0(s)}{I_2(s)} \right]$$

$$= I_2(s) \left[1 + \frac{\frac{R_3}{R_2 + \frac{1}{sC_2}}}{\frac{1}{sC_2}} \right] = I_2(s) \left[\frac{[(aR_2 C_2 + 1)] + sC_2 R_3}{(sR_2 C_2 + 1)} \right]$$

$$\frac{I_1(s)}{I_2(s)} = \frac{C_2 (R_2 + R_3)s + 1}{sR_2 C_2 + 1}$$

$$G_{21}(s) = \frac{R_3 (sC_2 R_2 + 1)}{L_2 C_2 (R_2 + R_3)s^2 + [C_2 (R_1 R_2 + R_2 R_3 + R_3 R_1) + L_1]s + (R_1 + R_3)}$$

(iv) Current transfer function,

$$\alpha_{21}(s) = \frac{I_2(s)}{I_1(s)} = \frac{sR_2 C_2 + 1}{C_2 (R_2 + R_3)s + 1}$$

Q. Find the open circuit driving point impedance at terminals 1-1' of the ladder work shown in figure below.

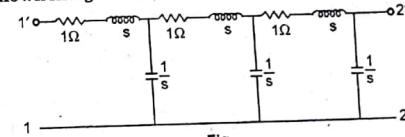


Fig.

Ans. From figure

$$Z_1(s) = s + 1, Y_2(s) = s, Z_3(s) = s + 1, Y_4 = s, Z_5 = s + 1, Y_6 = 2.$$

Therefore,

$$\begin{aligned} Z_{11}(s) &= Z_1 + \frac{1}{Y_2 + \frac{1}{Z_3 + \frac{1}{Y_4 + \frac{1}{Z_5 + \frac{1}{Y_6}}}}} \\ &= (s+1) + \frac{1}{s + \frac{1}{(s+1) + \frac{1}{s + \frac{1}{(s+1) + \frac{1}{s}}}}} \end{aligned}$$

$$\begin{aligned}
 &= (s+1) + \frac{1}{s+} \\
 &\quad (s+1) + \frac{1}{s+} \\
 &\quad \quad s+ \frac{s}{s^2+s+1} \\
 &= (s+1) + \frac{1}{s+} \\
 &\quad (s+1) + \frac{s^2+s+1}{s^2+s+2s} \\
 &= \frac{s^6+6s^5+11s^4+13s^3+10s^2+5s+1}{s^5+5s^4+5s^3+3s^2+3s}
 \end{aligned}$$

Q. Write necessary conditions for

- (a) Driving Point Immittance Functions and
- (b) Transfer functions

Ans. (a) Necessary Conditions for Driving Point Immittance Function (with common factors in $N(s)$ and $D(s)$ cancelled):

1. The coefficients in the polynomials $N(s)$ and $D(s)$ must be real and positive.
2. Poles and zeros must be conjugate if imaginary or complex.
3. The real part of all poles and zeros must be negative or zero, if the real part is zero, then that pole or zero must be simple, i.e. all the roots of $N(s) = 0$ and $D(s) = 0$ lie on the left half of s-plane and simple roots may lie on the imaginary or jw-axis.
4. The polynomials $N(s)$ and $D(s)$ may not have missing terms between those of highest and lowest degrees, unless all even or all odd terms are missing.
5. The highest degree of $N(s)$ and $D(s)$ may differ by either zero or one only.
6. The lowest degree of $N(s)$ and $D(s)$ may differ by either zero or one only.

(b) Necessary Conditions for Transfer Functions (with common factors in $N(s)$ and $D(s)$ cancelled)

1. The coefficients in the polynomials $N(s)$ and $D(s)$ of $T = N/D$ must be real and those for $D(s)$ must be positive.
2. Poles and zeroes must be conjugate if imaginary or complex.
3. The real part of poles must be negative or zero, if the real part is zero, then that pole must be simple. This includes the origin.
4. The polynomial $D(s)$ may not have any missing term between that of highest and lowest degrees, unless all even or all odd terms are missing.
5. The polynomial $N(s)$ may have terms missing, and some of the coefficients may be negative.
6. The degree of $N(s)$ may be as small as zero independent of the degree of $D(s)$.
7. (a) for G and α : The maximum degree of $N(s)$ is equal to the degree of $D(s)$.
(b) For Z and Y: The maximum degree of $N(s)$ is equal to the degree of $D(s)$ plus one.

THIRD SEMESTER (B.TECH) FIRST TERM EXAMINATION [2014] CIRCUITS AND SYSTEMS [ETEE-207]

Time : 1.30 hrs.

M.M.: 30

Note: Attempt Question no. 1. which is compulsory and any two more questions from remaining. There is step-marking and use of scientific calculator (non-programmable) is permitted. Assume missing data, if any.

Q.1. (a) Clearly distinguish between Transient Analysis and Steady State Analysis. Under what interval of time, as a multiple of Time Constant of the series R-L, or series R-C circuit, can we approximate the values of $v(t)$ or $i(t)$ as its steady state value? Why? [4]

Ans. The value of voltage and current during the transient period are known as transient response.

The values of voltage and current after the transient has died out are known as the steady state response *

4 time constant.

Q.1. (b) An LTI system has an impulse response $h(t)$ for which the Laplace Transform is

$H(s) = 1/(s+1) : \text{Re}(s) > -1$. Determine the step response for the same LTI system assuming it to be initially relaxed. [2]

$$\text{Ans. } H(s) = \frac{1}{s+1}$$

On taking Inverse LT we get

$$h(t) = e^{-t} u(t)$$

$$\text{If input is } u(t) \text{ then } U(s) = \frac{1}{s}$$

$$y(s) = \frac{1}{s+1} \times \frac{1}{s} = \frac{1}{s} - \frac{1}{s+1}$$

on taking LT

$$y(t) = u(t) - e^{-t} u(t)$$

Q.1. (c) What is the rate of change of current at $t = 0+$ in a coil of resistance 20Ω and inductance of 0.8 H when connected to a 200 V DC supply? Determine its value using classical method. [2]

$$\text{Ans. } V = R i(t) + L \frac{di(t)}{dt}$$

$$20 = 20 i(t) + 0.8 \frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} + 25 i(t) = 250$$

$$\text{C.F.} = K e^{-25t}$$

at

$$P.I. = \frac{250 e^{\alpha t}}{D+25} = \frac{250}{25} = 10$$


$$i(t) = K e^{-25t} + 10$$

$$t = 0^+ i = 0 =$$

$$0 = K + 10 \Rightarrow K = -10$$

$$i(t) = 10(1 - e^{-25t})$$

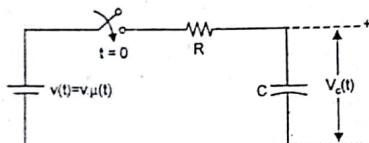Q.1. (d) Derive an expression for $V_c(t)$ for the circuit given below for $t > 0$, assuming zero initial condition. (2)



Ans.

$$V = R i(t) + \frac{1}{c} \int i(t) dt$$

On taking LT

$$\frac{V}{s} = R I(s) + \frac{1}{c} I(s)$$

$$I(s) = \frac{V}{s(R + \frac{1}{CS})} = \frac{CV}{RCS + 1} = \frac{V}{R} \times \frac{1}{\left(S + \frac{1}{CR}\right)}$$

On taking ILT we get $i(t) = \frac{V}{R} e^{-t/RC}$

$$V_c(t) = \frac{1}{C} \int \frac{V}{R} e^{-t/RC} dt$$

$$= \frac{1}{C} \times \frac{V}{R} \times e^{-t/RC} = V e^{-t/RC}$$

Q.1. (e) Solve the differential equation, with $y(0) = 0.5$ and $y(0) = 0$

$$\frac{d^2y(t)}{dt^2} + 9 \frac{dy(t)}{dt} + 20y(t) = 1$$

$$\text{Ans. } \frac{d^2y(t)}{dt^2} + 9 \frac{dy(t)}{dt} + 20y(t) = 1$$

On taking LT

$$s^2 Y(s) - s y(0^+) - y(0) + 9[sY(s) - y(0^+)] + 20Y(s) = \frac{1}{5}$$

$$s^2 Y(s) - .5S + 9sY(s) - 4.5 + 20Y(s) = \frac{1}{5}$$

$$Y(s)[s^2 + 9s + 20] = \frac{1}{s} + .5s + 4.5$$

on taking ILT, we get $y(t)$

Other method to solve

$$Y(s) = \frac{.5s^2 + 4.5s + 1}{s(s^2 + 9s + 20)} = \frac{(s^2 + 9s + 2)}{2s(s^2 + 9s + 20)}$$

$$\begin{aligned} CF &= D^2 + 9D + 20 \\ CF &= Ae^{-5t} + Be^{-4t} \\ &= D^2 + 5D + 4D + 20 \\ &= (D+5)(D+4) \\ D &= 5, 4 \end{aligned}$$

$$\text{for } P.I. \frac{1 e^{5t}}{D^2 + 9D + 20} = \frac{1}{20}$$

$$Y(t) = Ae^{-5t} + Be^{-4t} + \frac{1}{20}$$

$$\text{at } t = 0, Y(0) = .5A + B = .45$$

$$\text{on differentiating } y(t) = -5Ae^{-5t} + e^{-4t} Br - 4$$

$$\text{at } t = 0, y'(0) = 0 \quad -5A - 4B = 0$$

$$5A = -4B \Rightarrow A = -\frac{4B}{5}$$

$$\frac{4B}{5} + B = .45$$

$$B = 2.25$$

$$A = -1.8$$


$$y(t) = -1.8e^{-5t} + 2.25e^{-4t} + \frac{1}{20}$$

Q.2. (a) Let $x(t)$ and $y(t)$ be periodic signals with fundamental periods T_1 and T_2 respectively. Under what conditions is the sum $[x(t) + y(t)]$ periodic, and what shall be the fundamental period of the signal, if it is periodic. (2)

Ans. if $\frac{T_1}{T_2}$ is a rational number

T_1 is the Fundamental period

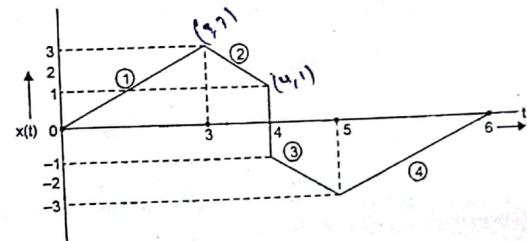Q.2. (b) Synthesize the given waveform using step, ramp signals only. (4)



$$\text{Ans. } y(t) = t[u(t) - u(t-3)] + (-2t+4)[u(t-3) - u(t-4)] + (-2t+7)[u(t-4) - u(t-5)] + (t-8)[u(t-5) - u(t-8)]$$

Q.2. (c) Determine $x(t)$ for the following conditions if $X(s)$ is given by $X(s) = \frac{1}{(s+1)(s+2)}$

when

(i) $x(t)$ is right-sided.

(ii) $x(t)$ is two-sided with ROC lying in between -1 and -2.

Ans.

$$X(s) = \frac{1}{(s+1)(s+2)} = \frac{1}{s+1} - \frac{1}{s+2}$$


(1)

$$x(t) = e^{-t} u(t) - e^{-2t} u(t)$$

(2)

$$x(t) = -e^{-t} u(t) - e^{-2t} u(t)$$

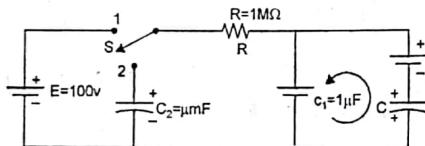Q.3. (a) In the circuit of the figure below, switch S has been in position 1 for a long time:



(i) Find the complete solution for the current in the circuit when S is put to position 2.

(ii) How long does it take in seconds for the transient to disappear? (current to decay within 1%)

(iii) Determine the voltage which appears across each capacitor at steady state.

Ans.

$$V_c(0^-) = 1000 V$$

$$1000 = R i(t) + \frac{1}{c_2} \int i(t) dt + \frac{1}{c_1} \int i(t) dt$$

on differentiating above equation we get

$$R \frac{di(t)}{dt} + \frac{1}{c_2} i(t) + \frac{1}{c_1} i(t) = 0$$

$$10^6 \frac{di(t)}{dt} + \frac{2}{10^{-6}} i(t) = 0$$

$$\frac{di(t)}{dt} + 2i(t) = 0 \Rightarrow i(t) = A e^{-2t}$$

at

$$t = 0^+ i(0^+) = \frac{-1000}{10^6} = -10^{-3}$$

$$A = -10^{-3}$$


$$i(t) = -10^{-3} e^{-2t}$$

Q.3. (b) Define Time Constant of an RL and RC circuit. Why there are no transients in purely resistive circuits?

Ans. In RL circuit time constant = $\frac{L}{R}$

In RC circuit = RC

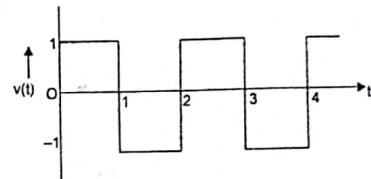Q.3. (c) For the given square wave, determine the Laplace transform, using its properties:




$$x(t) = u(t) - 2u(t-1) - 2u(t-2) - 2u(t-3)$$

Ans.
on taking LT

$$\begin{aligned} X(s) &= \frac{1}{s} - 2 \frac{e^{-s}}{s} - 2 \frac{e^{-2s}}{s} - 2 \frac{e^{-3s}}{s} + \dots \\ &= \frac{1}{s} - \frac{2}{s} (e^{-s} + e^{-2s} + e^{-3s} \dots \infty) \\ &= \frac{1}{s} - \frac{2}{s(1-e^{-s})} = \frac{1}{s} \left[\frac{1-e^{-s}-2}{1-e^{-s}} \right] = \frac{-1}{s} \left(\frac{1+e^{-s}}{1-e^{-s}} \right) \end{aligned}$$

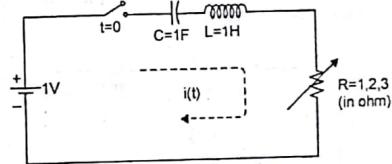Q.4. (a) A series R-L-C circuit having a pure Inducto having Inductance 1 H and a pure Capacitor having Capacitance 1 F is connected with a variable resistor which can take three values: 1 Ω, 2 Ω and 3 Ω.



Determine $i(t)$ for $t > 0$ in each of the three cases, indicating the nature of response. (Assume all initial conditions to be zero)

$$\text{Ans. } L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt = 1$$

On differentiating above equation we get

$$L \frac{d^2i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$$

$$\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

$$D^2 + \frac{R}{L} D + \frac{1}{LC} = 0$$

$$\text{if } R = 1, L = 1, C = 1$$

$$D^2 + D + 1 = 0$$

$$$$

Third Semester, Circuits & Systems


$$D = \frac{-1-i\sqrt{3}}{2}, \frac{-1+j\sqrt{3}}{2}$$

$$i(t) = A e^{-\left(\frac{1-j\sqrt{3}}{2}\right)t} + B e^{-\left(\frac{1+j\sqrt{3}}{2}\right)t}$$

at $t = 0 i = 0$
 $A + B = 0$
 $R = 2$
 $p^2 + 2p + 1 = 0$
 $p = -1, -1$
 $i(t) = A e^{-t} + B t e^{-t}$
 $t = 0 i = 0$
 $A = 0$
 $R = 3$
 $p^2 + 3p + 1 = 0$
 $D = b^2 - 4ac$
 $P = \frac{5-3+\sqrt{5}}{2} = \frac{3-\sqrt{5}}{2}$
 $i(t) = A e^{-\left(\frac{3-\sqrt{5}}{2}\right)t} + B e^{-\left(\frac{3+\sqrt{5}}{2}\right)t}$

at $t = 0 i = 0$
 $A + B = 0$

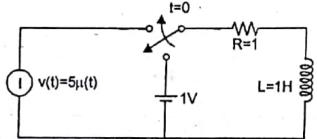Q.4. (b) The switch S is moved from the position 1 to position 2 at $t = 0$, when a 5 V DC is impressed to the R-L circuit. At what time does the voltage across Inductor become half of the voltage impressed? (4)



Ans.

$$i(0^-) = iA \quad (\text{because inductor behave as short circuit})$$

$$5u(t) = 1i(t) + L \frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} + i(t) = 5u(t)$$

$$C.f = A e^{-t}$$

$$PI = \frac{5}{D+1} = 5$$

$$i(t) = 5+A e^{-t}$$

$$t = 0 \quad i = 1A$$

$$1 = 5+A \quad A = -4$$

$$i(t) = 5 - 4e^{-t}$$

at

THIRD SEMESTER (B.TECH) SECOND TERM EXAMINATION [2014] CIRCUITS AND SYSTEMS [ETEE-207]

M.M.: 30

Time : 1.30 hrs.

Note: Attempt Question no. 1, which is compulsory and any two more questions from remaining. There is step-marking and use of scientific calculator (non-programmable) is permitted. Assume missing data, if any.


Q.1. (a) Give an expression for the transient response of an initially relaxed purely inductive circuit having an inductance of 1 H when subjected to an input $v(t) = 2 \cos t$ volt.

Ans.

$$i(t) = \frac{1}{L} \int V(t) dt$$

$$i(t) = \frac{1}{1} \int 2 \cos t dt = 2 \sin t$$

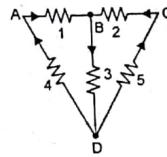
Q.1. (b) Define node and branch of an oriented graph. Draw any electrical circuit without using Inductor and Capacitor which represents the following graph with A, B, C, D as nodes and 1 to 5 as branches.




Ans. The components in a circuit is replaced by line segments called branch.

Two or more branches meet at a point is called node.

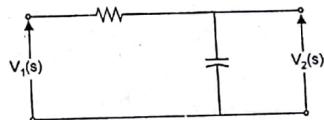Q.1. (c) Determine $V_2(s)/V_1(s)$ for the given R-C circuit, where R is in ohm and C is in Farad.



Ans.

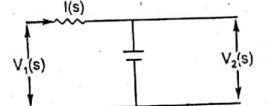


$$V_1(s) = I(s)R + I(s) \times \frac{1}{cs}$$

$$I(s) = \frac{V_1(s)}{R + \frac{1}{cs}}$$

$$V_2(s) = I(s) \times \frac{1}{cs} = \frac{V_1(s)}{R + \frac{1}{cs}} \times \frac{1}{cs}$$

$$\frac{\dot{V}_2(s)}{V_1(s)} = \frac{1/cs}{R + 1/cs} = \frac{1}{1 + Rcs}$$

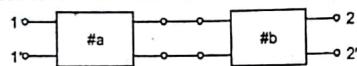Q.1. (d) Two networks 'a' and 'b' are connected in cascade as shown below. If $[T_a]$ and $[T_b]$ are their inverse transmission parameters, derive for $[T]$ the overall value for cascaded network.



Ans. For the cascaded network, T-parameters are given as:

$$[T] = [T_a][T_b]$$

For the inverse parameters,

$$[T^*] = [[T_a][T_b]]^*$$

By using matrix property

$$[AB]^{-1} = [B^{-1}A^{-1}]$$

$$T^* = [T_a^*][T_b^*]$$

Q.1. (e) Check whether the polynomial $F(s) = s^3 + 4s^2 + 2s + 8$ is Hurwitz or not.

Ans.

$$s^3 + 4s^2 + 2s + 8$$

$$\text{odd port} = s^3 + 2s$$

$$\text{even port} = 4s^2 + 8$$

$$4s^2 + 8 \quad s^3 + 2s \quad (1/9s)$$

$$\frac{s^3 + 2s}{0}$$

$$F(s) = s^3 + 2s \left(1 + \frac{4}{s}\right)$$


From above, equation we can say $\left(1 + \frac{4}{s}\right)$ is hurwitz

Now check for $s^3 + 2s$


$$s(s^2 + 2) = s(s + i\sqrt{2})(s - i\sqrt{2})$$
 is hurwitz

So $F(s)$ is hurwitz

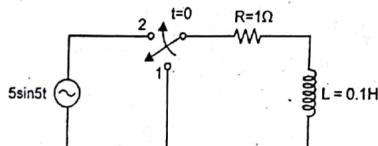Q.2. (a) Obtain the current for $t > 0$, if an AC voltage $v = 5 \sin 5t$ is applied when the switch 'k' is moved from position 1 to 2 at $t = 0$.



Ans.

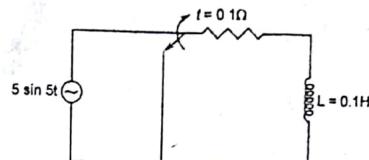

$$5 \sin 5t = I(t) \times R + L \frac{dI(t)}{dt}$$

$$= I(t) + .1 \frac{dI(t)}{dt}$$

$$\frac{dI(t)}{dt} + 10 I(t) = 50 \sin 5t$$

$$CF = D + 10 = 0$$

$$D = -10$$

$$CF = A e^{-10t}$$

$$PI = \frac{50 \sin 5t (D - 10)}{(D + 10)(D - 10)}$$

$$= \frac{(D - 10)(50 \sin 5t)}{D^2 - 10^2}$$

$$= \frac{D(50 \sin 5t) - 500 \sin 5t}{-25 - 100}$$

$$= \frac{5 \times 50 \cos 5t}{-75} + \frac{500}{75} \sin 5t$$

$$E(t) = CF + PI$$

$$= A e^{-10t} - \frac{10}{3} \cos 5t + \frac{20}{3} \sin 5t$$


$t = 0$ $i = 0$ (inductor behave as open circuit)

$$0 = A - \frac{10}{3}$$

$$A = \frac{10}{3}$$

$$I(t) = \frac{10}{3} e^{-10t} - \frac{10}{3} \cos 5t + \frac{20}{3} \sin 5t$$

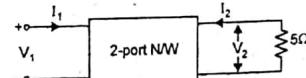
Q.2. (b) The following equation give the voltage V_1 and V_2 at the two ports of a two port network:



$$\begin{aligned} V_1 &= 5I_1 + 6I_2 & \dots(1) \\ V_2 &= 2I_1 + I_2 & \dots(2) \\ V_2 &= -5I_2 \text{ from fig.} & \end{aligned}$$

A load resistor of 5 ohm is connected across port 2. Calculate the input impedance.

Ans.

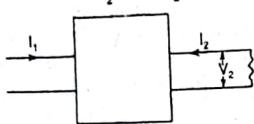

on putting this value in equation (2)

$$\begin{aligned} -5I_2 &= 2I_1 + I_2 \\ -6I_2 &= 2I_1 \Rightarrow I_1 = -3I_2 \end{aligned}$$


Putting the value of I_1 in equation (1)

$$V_1 = 5I_1 + 6 \times -\left(\frac{I_1}{3}\right)$$

$$V_1 = 5I_1 - 2I_1$$


$$Z_{in} = \frac{V_1}{I_1} = 3$$

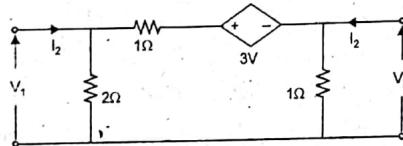Q3. (a) Determine the Z parameters for the following network shown in figure below:



State whether it is reciprocal, symmetrical or not.

Ans.

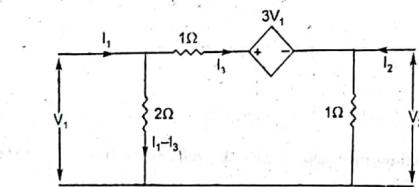

$$\begin{aligned} V_1 &= 2(I_1 - I_3) & \dots(1) \\ I_3 + 3V_1 - 2(I_1 - I_3) - (I_2 + I_3) &= 0 & \dots(2) \\ 4I_3 - 2I_1 + I_2 + 3V_1 &= 0 & \dots(3) \\ V_2 &= I_2 + I_3 & \end{aligned}$$

$$\begin{aligned} V_1 &= 2I_1 - 2\left(\frac{I_1}{2} - \frac{I_2}{4} - \frac{3V_1}{4}\right) \\ V_1 &= 2I_1 - I_2 & \dots(4) \\ V_2 &= I_2 + \frac{1}{4}(2I_1 - I_2 - 3V_1) \end{aligned}$$

$$V = 2I_1 + \frac{3}{2}I_2 \quad \dots(5)$$

$$Z = \begin{bmatrix} -2 & -1 \\ 2 & 3/2 \end{bmatrix}$$

Q3. (b) Determine the Incidence Matrix, Cut-set Matrix and Tie-Se matrix, graph.
(5)


Ans.

Incident matrix

$$A = B \begin{vmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 1 & 0 & 0 & -1 & 0 & -1 & 0 \\ -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 & -1 \\ 0 & -1 & 1 & 1 & 0 & 0 & 1 \end{vmatrix}$$

Cut set matrix

$$\begin{array}{c|ccccccc} c_1 & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ c_1 & 1 & 0 & 0 & -1 & 0 & -1 & 0 \\ c_2 & 0 & 0 & 1 & 0 & 1 & -1 & 0 \\ c_3 & 0 & 1 & 0 & -1 & 1 & -1 & 0 \end{array}$$

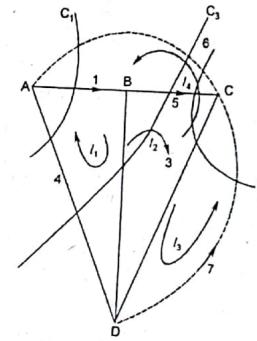

Tie set

$$\begin{array}{c|ccccccc} l_1 & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ l_1 & 1 & 0 & 0 & -1 & 0 & -1 & 0 \\ l_2 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ l_3 & 0 & 0 & -1 & 0 & -1 & 1 & -1 \\ l_4 & 0 & -1 & 1 & 1 & 0 & 0 & 1 \end{array}$$

Q4. (a) The driving point impedances of a one port reactive network is given by

$$Z(s) = \frac{4s(s^2 + 4)}{(s^2 + 1)(s^2 + 16)}$$

Obtain Foster's I OR Foster's II form of realization. Draw the circuit. (5)

12-2014

Third Semester, Circuits & Systems

Ans.

On partial fraction

$$Z(s) = \frac{4s(s^2 + 4)}{(s^2 + 1)(s^2 + 16)}$$

$$\frac{A_1 s}{s^2 + 1} + \frac{A_2 s}{s^2 + 16}$$


$$A_1 = \left. \frac{4s(s^2 + 4)}{(s - 1j)(s^2 + 16)} \right|_{s=-j} = .8$$

$$A_2 = \left. \frac{4s(s^2 + 4)}{(s^2 + 1)(s - 4j)} \right|_{s=-4j} = 3.2$$

$$Z = \frac{.8s}{s^2 + 1} + \frac{3.2s}{s^2 + 16}$$

$$Z(s) = \frac{\frac{1}{s}}{s^2 + \frac{1}{Lc}}$$


for faster I

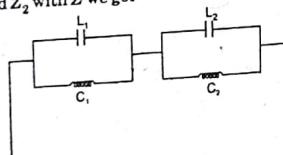on comparing Z_1 and Z_2 with Z we get

$$L_1 = .8 \quad C_1 = \frac{1}{0.8} \quad \frac{1}{LC} = 16$$

$$L_2 = .2 \quad C_2 = \frac{1}{3.2} \quad L = \frac{1}{16 \times C} = \frac{3.2}{16} = .2$$

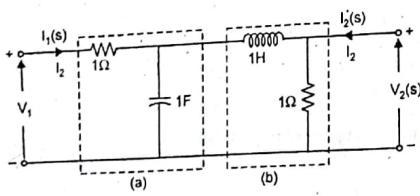Q.4. (b) Obtain the Transmission parameters for the network shown below, using properties of inter-connection or otherwise. Check for reciprocity condition. (5)




Ans.

$$V_1 = AV_2 + B(-I_2)$$

$$I_1 = CV_2 + D(-I_2)$$

I.P. University-(B.Tech)-Akash Books

2014-13

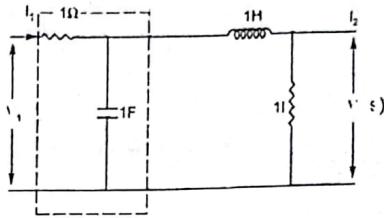

$$V_1 = I_1 + (I_1 + I_2) \frac{1}{s}$$

$$= I_1 \left(1 + \frac{1}{s} \right) + I_2 / s \quad \dots(1)$$

$$V_2 = \frac{(I_2 + I_1)}{s}$$

$$I_1 = SV_2 - I_2' \quad \dots(2)$$

Putting the value of I_1 and in equation (1)

$$V_1 = (SV_2 - I_2') \left(1 + \frac{1}{s} \right) + I_2' / s$$

$$= S \left(1 + \frac{1}{s} \right) V_2 + I_2' \left(s - 1 - \frac{1}{s} \right)$$

$$= (S + 1) V_2 + I_2' - 1 \quad \dots(3)$$

From equation (3) and (2)

$$I_a = \begin{bmatrix} (s+1) & +1 \\ s & 1 \end{bmatrix} \quad \dots(1)$$

$$V_1 = S I_a + (I_1 + I_2)$$

$$V_2 = (I_2 + I_1) \quad \dots(2)$$

$$I_1 = V_2 - I_2$$

$$V_1 = (S+1)(V_2 - I_2) + I_2$$

$$= (S+1)V_2 + I_2(1-S-1)$$

$$= (S+1)V_2 - I_2 S$$

$$T_b = \begin{bmatrix} s+1 & -s \\ 1 & -1 \end{bmatrix}$$

$$T = T_a T_b = \begin{bmatrix} s^2 + 2s + 2 & s^2 + s + 1 \\ s^2 + s + 1 & s^2 + 1 \end{bmatrix}$$

THIRD SEMESTER (B.TECH)
END TERM EXAMINATION [2014]
CIRCUITS AND SYSTEMS [ETEE-207]

M.M.

Time : 3 hrs.

Note: Attempt any five questions including Q.No. 1 which is compulsory. Assume missing data if any.

Q.1. (a) Show that voltage across a capacitor & current through an inductor cannot change instantaneously.

Ans. For Modulator

$$L_1(t) = \frac{1}{L} \int_{-\infty}^t v_L dt$$

$$L_2 = (0-) t = 0_-$$

$$L_2(0_+) t = 0_+$$

therefore

$$i_L(0_+) = \frac{1}{L} \int_{-\infty}^{0_+} V_L dt$$

$$= i_L(0) + \frac{T}{L} \int_0^{0_+} V_L dt$$

Interval 0_- to 0_+ is almost zero.

$$\text{So } \frac{1}{L} \int_{0_-}^{0_+} V_L dt = 0$$

$$i_L(0_+) = i_L(0-)$$

Similarly for Capacitor

$$V(0-) = V(0_+)$$

This shows the voltage across a capacitor is constant & current across inductor constant for instantaneous change

Q.1. (b) A resistor of 10Ω has a current $i = 6 \sin 500\pi t$. Find the instantaneous voltage, power & energy over one cycle.

Ans. Instantaneous voltage = $IR = 60 \sin 500\pi t$

$$\text{Power} = I_{rms}^2 R$$

$$= \left(\frac{6}{\sqrt{2}}\right)^2 \times 10 = \frac{360}{2} \times 10 = 1800 \text{ W}$$

$$E = PT$$


$$= P \times \frac{1}{f} = 1800 \times \frac{1}{250} = 72$$

I.P. University-(B.Tech)-Akash Books

2014-15

Q.1. (c) Show that the output of an LTI system is simply its impulse response convolved with the excitation.

Ans.

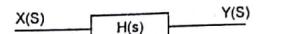

Let a LTI system with transfer function $H(s)$ and input $X(s)$

Then output of the system is

$$y(s) = H(s) \times (s)$$

Applying convolution theorem

$$H(s) X(s) \xrightarrow{\text{ILT}} h(t) \times x(t)$$

Q.1. (d) State significance of impulse, unit step, ramp & exponential signals why are they used?

Ans. Impulse

$$\delta(t) = \begin{cases} 1 & t=0 \\ 0 & \text{ow} \end{cases}$$

Unit step

$$u(t) = \begin{cases} t & t \geq 0 \\ 0 & \text{ow} \end{cases}$$

$$\text{ramp } r(t) = \begin{cases} t & t \geq 0 \\ 0 & \text{ow} \end{cases}$$

$$\text{exponential function} = \begin{cases} e^{at} & t \geq 0 \\ 0 & \text{ow} \end{cases}$$

These all basic signals are used to know the basic input response of the system.

Q.1. (e) Check the system $y(t) = x(t) \cos \omega_0 t$ for time invariance $y(t) = Ax(t) + B$ for linearity. (3 x 5 = 15)

Ans.

1st to Apply Shifted input $x(t-T)$ then output is

$$x(t-T) \cos \omega_0 t$$

and time shifted output is

$$c(t-T) \cos \omega_0 (t-T)$$

both are not equal so system is time variant

$$y(t) = A x(t) + B$$

for input $x_1(t) \rightarrow y_1(t)$

$$y_1(t) = Ax_1(t) + B$$

for input $ax_1(t) + b$

$$y(t) = A(ax_1(t) + b) + B$$

for input $x_2(t) \rightarrow y_2(t)$

$$y_2(t) = Ax_2(t) + B$$

linear combination of output

$$a(Ax_1(t) + b) + b(Ax_2(t) + B)$$

$$y(t) = Aax_1(t) + ab + bAx_2(t) + Bb$$

$$y(t) \neq y'(t)$$

So system is non linear.

16-2014

Third Semester, Circuit & System

Q.2. (a) A 2 element series circuit has an average power 940 W & power factor 0.707 lagging. Determine the circuits elements if the expressed voltage is $v = 99 \sin(6000t + 30^\circ) V$.

Ans. (RL) An ac circuit in which the current lags behind the voltage is said to have a lagging power factor. (RC) An ac circuit in which current leads the voltage is said to have a leading power factor.

Lagging power factor mean current lags behind voltage means RL circuit.

$$\cos \phi = .707$$

$$\phi = 45^\circ$$

$$\text{Power} = VI \cos \phi$$

$$940 = 99 \times I \times .707$$

$$I = \frac{940}{99 \times .707} = 13.42$$

$$I = 13.42 \sin(6000t + 30 - 45) \\ = 13.42 \sin(6000t - 15)$$

Q.2. (b) Derive the "Q" for a parallel RLC circuit. (10)

Ans. $\theta = \text{factor for parallel RLC}$

$$\text{Let } V = V_m \sin \omega t$$

$$\text{current through } i_L = \frac{V_m \sin(\omega_0 t - 90)}{XL_0}$$

$$\text{inductor where } \omega_0 = \frac{1}{\sqrt{LC}}$$

Instantaneous energy in circuit is

$$w(t) = \frac{1}{2} L i_L^2 + \frac{1}{2} C V^2 \\ = \frac{1}{2} C V_m^2$$

Average power loss in circuit is

$$P = \frac{V^2}{R} = \frac{(V_m / \sqrt{2})^2}{R} = \frac{V_m^2}{2R}$$

Energy loss per cycle

$$P \frac{2\pi}{\omega_0} = \frac{\pi V_m^2}{\omega_0 R}$$

Quality factor $Q_{OP} = \frac{2\pi (\text{maximum energy stored in ckt})}{(\text{total energy loss frequency})}$

$$= \frac{2\pi \frac{1}{2} C V_m^2}{\pi V^2 / \omega_0 R}$$

$$Q_{OP} = \omega_0 C R$$

I.P. University-(B.Tech)-Akash Books

2014-17


Q.3. (a) Find the rms value of $v = (10 + 14.4 \cos \omega t + 3.55 \sin 3\omega t) V$. (5)

$$\text{Ans. } V^2 = \frac{1}{2\pi} \int v^2 dt = \frac{1}{2\pi} \int (10 + 14.4 \cos \omega t + 3.55 \sin 3\omega t)^2 dt$$

$$V_{rms}^2 = \left(10^2 + \frac{(14.4)^2}{2} + \frac{(3.55)^2}{2} \right)$$

$$V_{rms} = \sqrt{10^2 + \frac{(14.4)^2}{2} + \frac{(3.55)^2}{2}}$$

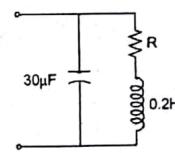Q.3. (b) Compare the resonant frequency of the circuit shown for $R = 0$ & $R = 50 \Omega$.



LC parallel tank circuit.

Ans.

if

$$R = 0$$

$$Y = j\omega C + \frac{1}{j\omega L}$$

$$Y = j\omega C - j\frac{1}{\omega L}$$

for resonance

$$\text{Im}(Y) = 0$$

$$\omega C - \frac{1}{\omega L} = 0$$

$$\omega C = \frac{1}{\omega L} \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

If

$$R = 50$$

$$Y = j\omega C + \frac{1}{R+j\omega L} : j\omega C + \frac{R-j\omega L}{R^2 + \omega^2 L^2}$$

$$Y = \frac{R}{R^2 + \omega^2 L^2} - j\omega \left(C - \frac{L}{R^2 + \omega^2 L^2} \right)$$

$$\text{Im}(Y) = 0$$

$$j\omega \left(C - \frac{L}{R^2 + \omega^2 L^2} \right) = 0$$

$$C = \frac{L}{R^2 + \omega^2 L^2}$$

$$\omega^2 L^2 C = L - CR^2$$

$$\omega^2 = \frac{L - CR^2}{L^2 C} \Rightarrow \omega = \sqrt{\frac{L - CR^2}{L^2 C}}$$

Putting the value of R , L & C

$$\omega = \sqrt{\frac{.2 - 30 \times 10^{-6} \times 2500}{(.2)^2 \times 3 \times 10^{-6}}}$$

Q.4. (a) A CT function has $H(s) = \frac{1}{s+5}$. If it is excited by a sinusoidal input $x(t) = 10 \cos 200\pi t$. Find the steady state output function amplitude and frequency of the output waveform.

Ans.

$$H(s) = \frac{1}{s+5}$$

$$x(t) = 10 \cos 200\pi t$$

$$X(s) = \frac{10s}{s^2 + (200\pi)^2}$$

$$y(s) = \frac{1}{s+5} \times \frac{10s}{s^2 + (200\pi)^2} \Rightarrow \frac{A}{s+5} + \frac{B}{s+200\pi j} + \frac{C}{s-200j}$$

$$A = \left. \frac{10s}{s^2 + (200\pi)^2} \right|_{s=-5} = \frac{-50}{25 + 200^2 \pi^2}$$

$$B = \left. \frac{10s}{(s+5)(s-200\pi)} \right|_{s=200\pi j}$$

$$C = \left. \frac{10s}{(s+5)(s+200j)} \right|_{s=200\pi j}$$

Steady state output $s \rightarrow 0$ or $t \rightarrow \infty$

Apply final value theorem

$$\lim_{s \rightarrow 0} sy(s) = \lim_{s \rightarrow 0} \frac{10s^2}{(s+5)(s^2 + (200\pi)^2)} = 0$$

Q.4. (b) A CTS is described by $\ddot{y} + 3\dot{y} + 2y = 3r$. Find.

(i) Transfer function $H(s)$.

(ii) Impulse response $h(t)$.

(iii) Step response

(iv) Frequency response

(v) Block diagram representation of this system.

$$\text{Ans. (i)} \quad \dot{y} + 3\dot{y} + 2y = 3r$$

taking LT

$$s^2 y(s) + 3s y(s) + 2y(s) = 3R(s)$$

$$H \frac{y(s)}{R(s)} = \frac{3}{s^2 + 3s + 2} = \frac{3}{(s+1)(s+2)}$$

$$(ii) \quad \frac{A}{s+1} + \frac{B}{s+2} \Rightarrow A = 3, B = -3$$

$$H(s) = 3 \left[\frac{1}{s+1} - \frac{1}{s+2} \right]$$

on taking iLT

$$h(t) = 3e^{-t} - 3e^{-2t}$$

$$(iii) \quad y(s) = H(s) \times (s)$$

For unit step input $x(t) = u(t)$

$$x(s) = \frac{1}{s}$$

$$= \frac{3}{(s+1)(s+2)} \times \frac{1}{s} = \frac{3}{s(s+1)(s+2)}$$

$$\frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2}$$

$$A = \left. \frac{3}{(s+1)(s+2)} \right|_{s=0} = \frac{3}{2}$$

$$B = \left. \frac{3}{s(s+2)} \right|_{s=-1} = \frac{3}{-1(-1+2)} = -3$$

$$C = \left. \frac{3}{s(s+1)} \right|_{s=-2} = 3/2$$

$$y(s) = \frac{3}{2} \times \frac{1}{s} - \frac{3}{s+1} + \frac{3}{2} \frac{1}{s+2}$$

$$y(t) = \frac{3}{2} u(t) - 3e^{-t} + \frac{3}{2} e^{-2t}$$

$$(iv) \frac{3}{(s+1)(s+2)} \text{ putting } s = j\omega$$

$$H(j\omega) = \frac{3}{(j\omega+1)(j\omega+2)} \Rightarrow \frac{3}{-\omega^2 + 3j\omega + 2} = \frac{3}{(2-\omega^2) + 3j\omega}$$


$$\text{on rationalizing } \frac{3((2-\omega^2) - 3j\omega)}{(2-\omega^2)^2 + (3\omega)^2} = \frac{3(2-\omega^2) - 9j\omega}{4 + \omega^4 + 3\omega^2}$$

$$(v) \frac{3}{s^2 + 3s + 2}$$

$$\frac{\frac{3}{s^2}}{1 + \frac{3}{s} + \frac{2}{s^2}} = \frac{y(s)}{x(s)}$$

$$\frac{3}{s^2} x(s) = y(s) + \frac{3}{s} x(s) + \frac{2}{s^2} y(s)$$
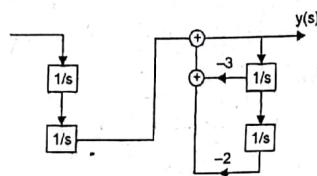
$$y(s) = \frac{3}{s^2} x(s) - \frac{3}{s} y(s) - \frac{2}{s^2} y(s)$$



Q.5. (a) Given $F(S) = \frac{2s+5}{(s+2)(s+5)}$. Find $f(t)$ if the ROC is

- (i) $s > -2$
- (ii) $-5 < s < -2$
- (iii) $s < -5$

$$\text{Ans. (a)} F(s) \frac{2s+5}{(s+2)(s+5)}$$

$$= \frac{A}{s+2} + \frac{B}{s+5}$$

$$A = \frac{2s+5}{s+5} \Big|_{s=-2} = \frac{-4+5}{-2+5} = \frac{1}{3}$$

$$B = \frac{2s+5}{5+2} \Big|_{s=-5} = \frac{-10+5}{-5+2} = \frac{5}{3}$$

$$F(s) = \frac{1}{3} \frac{1}{s+2} + \frac{5}{3} \frac{1}{s+5}$$

1. If ROC $s > -2$

$$\frac{1}{2} e^{-2t} u(t) + \frac{5}{3} e^{-5t}$$

(ii)

$$-5 < s < -2$$

$$\frac{1}{2} e^{-2t} u(-t) + \frac{5}{3} e^{-5t} u(t)$$

$$(iii) s < -5$$

$$\frac{1}{2} e^{-2t} u(t) + \frac{5}{3} e^{-5t} u(-t)$$

Q.5. (b) Show that $LT[f(t)] = s \cdot F(s) - f(0)$.

$$L(f(t)) = F(s)$$

$$\text{then } L\left[\frac{df(t)}{dt}\right] = sF(s) - f(0^-)$$

$$\text{Proof } L\left[\frac{d}{dt}f(t)\right] = \int_0^\infty \frac{df(t)}{dt} e^{-st} dt$$

on integrating by parts

$$u = e^{-st} \text{ and } dv = df(t)$$

$$du = -se^{-st} \text{ and } v = f(t)$$

$$\int u dv = vu - \int v du$$

$$= e^{-st} f(t) \Big|_0^\infty - \int_0^\infty f(t) (-se^{-st}) dt$$


$$= e^{-st} f(t) \Big|_0^\infty + s \int_0^\infty f(t) e^{-st} dt$$

$$= -f(0^-) + sF(s)$$

$$L\left[\frac{df(t)}{dt}\right] = sF(s) - f(0^-)$$

Q.5. (c) Find Laplace transform (LT) of the saw tooth wave form shown in figure:

Ans.

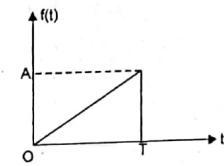

$$f(t) = \frac{A}{T} t [u(t) - u(t-T)]$$

$$= \frac{A}{T} t u(t) - \frac{A}{T} u(t-T)$$

$$= \frac{A}{T} t u(t) - \frac{A}{T} [(t-T) - u(t-T) + Tu(t-T)]$$


on taking LT

$$FS = \frac{A}{T} \frac{1}{s^2} - \frac{A}{T} \left[\frac{e^{-Ts}}{s^2} + T e^{-Ts} \right]$$

22-2014

Third Semester, Circuit & System

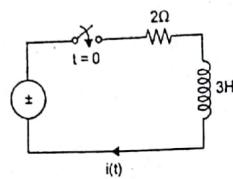
Q.6. (a) Switch is closed at $t = 0$. Find $i(t)$ for $t \geq 0$ using Laplace transform. (8)



Ans.

$$\Delta t \quad t = 0$$

$$i = \frac{10 \sin 10(0)}{2}$$

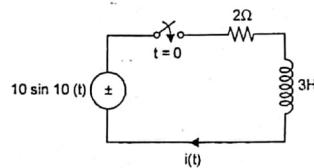

Apply KVL

$$10 \sin 10t = 2i(t) + 3 \frac{di(t)}{dt}$$

$$\text{taking } (LT) = \frac{10 \times 10}{s^2 + 10^2} = 2I(s) + 3sI(s)$$

$$I(s) = \frac{100}{s^2 + 100} \times \frac{1}{(2+3s)} \Rightarrow \frac{A}{3s+2} + \frac{B}{(s+10i)} + \frac{C}{(s-10j)}$$

$$A = \frac{100}{s^2 + 100} \Big|_{s=-2} = \frac{100}{4+100} = \frac{900}{904}$$

$$B = \frac{100}{(2+3s)(s-10j)} \Big|_{s=-10j} = \frac{100}{(2-30j)(-20j)}$$

$$= \frac{5}{(-2j-30)}$$

$$C = \frac{100}{(2+3s)(s+10j)} \Big|_{s=10j} = \frac{100}{(2+30j)(20j)} = \frac{5}{(2j-30)}$$

$$I(s) = \frac{900}{904 \times 3} \left(\frac{2}{s+2} \right) + \frac{5}{(-2j-30)} \frac{1}{s+10j} + \frac{s}{(2j-30)} \frac{1}{s-10j}$$

I.P. University-(B.Tech)-Akash Books

2014-23

Q.6. (b) Find the transient steady state response of a causal system having $h(t) = e^{-t}$ & $x(t) = 10 \sin 4t u(t)$. (7)

Ans. $h(t) = e^{-t}$

$$x(t) = 10 \sin 4t u(t)$$

taking LT

$$H(s) = \frac{1}{s+1} x(s) = \frac{10 \times 4}{s+j^2}$$

$$y(s) = \frac{1}{s+1} \times \frac{40}{s^2 + 4^2}$$

$$= \frac{A}{s+1} + \frac{B}{s+j4} + \frac{C}{s-j4}$$

$$A = \frac{40}{s^2 + 4^2} \Big|_{s=-1} = \frac{40}{17}$$

$$B = \frac{40}{(s+1)(s-4j)} \Big|_{s=j4} = \frac{40}{(-4j+1)(-8j)} = \frac{5}{(-4-j)}$$

$$C = \frac{40}{(s+1)(s+4j)} \Big|_{s=4j} = \frac{40}{(4j+1)(8j)} = \frac{5}{(-4+j)}$$

$$y(s) = \frac{40}{17} \frac{1}{s+1} + \frac{5}{(-4-j)} \frac{1}{(s+j4)} + \frac{5}{(-4+j)} \frac{1}{(s-j4)}$$

$$= \frac{40}{17} e^{-t} + \frac{5}{(-4-j)} e^{-j4t} + \frac{5}{(-4+j)} e^{+j4t}$$

Q.7. (a) What are ABCD parameters? Show that $AD-BC = 1$ for a bilateral network. (7)

Ans. In terms of T-parameters

$$V_1 = AV_2 + B(-I_2)$$

$$I_1 = CV_2 + D(-I_2)$$

$$V_1 = V_s I_1, V_2 = 0, I_2 = -I'_2$$

$$I'_2 = \frac{V_s}{B}$$

As in figure (b);

$$V_2 = V_s I_2 = I'_2 V_1 = 0, I_1 = -I'_1$$

$$I'_1 = V_s \left(\frac{AD-BC}{B} \right)$$

Above discussion leads to the condition of reciprocity,


24-2014

Third Semester, Circuit & System


$$AD - BC = 1 \text{ or } \Delta T = 1$$

or
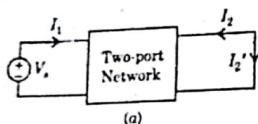
$$\begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$$



(a)

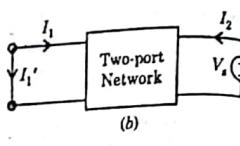

(b)

Q.7. (b) Show that $Z_{11} = Z_{22}$ for a symmetric network & $Z_{12} = Z_{21}$ for a reciprocal network.

Ans. In terms of Z-parameters.

$$\text{As in (a); } V_1 = V_2, I_1 = I_2, I_1 = 0, V_2 = V_1 \\ V_s = Z_{11} I_1$$


$$\left. \frac{V_s}{I_1} \right|_{I_1=0} = Z_{11}$$

$$\text{As in figure 8.14 (b); } V_2 = V_s, I_2 = I_1, I_2 = 0, V_1 = V_1 \\ V_s = Z_{22} I_2$$


$$\left. \frac{V_s}{I_2} \right|_{I_2=0} = Z_{22}$$

from the definition of symmetry,

$$\left. \frac{V_s}{I_1} \right|_{I_2=0} = \left. \frac{V_s}{I_2} \right|_{I_1=0} \text{ leads to} \\ Z_{11} = Z_{22}$$

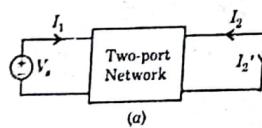

(a)

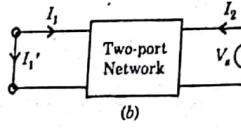

(b)

In terms of Z-parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2$$

As in figure (a):

$$V_1 = V_s, I_1 = I_1, V_2 = 0, I_2 = -I'_2$$

Therefore,

$$V_s = Z_{11} I_1 - Z_{12} I'_2$$

and

$$0 = Z_{21} I_1 - Z_{22} I'_2$$

Hence

$$I'_2 = \frac{V_s Z_{21}}{Z_{11} Z_{22} - Z_{21} Z_{12}}$$

I.P. University-(B.Tech)-Akash Books

2014-25

$$\text{As in figure 8.13 (b); } V_2 = V_s, I_2 = I'_2, V_1 = 0, I_1 = -I'_1.$$

Therefore,

$$0 = -Z_{11} I'_1 + Z_{12} I_2$$

and


$$V_s = -Z_{21} I'_1 + Z_{22} I_2$$

Hence


$$I'_1 = \frac{V_s Z_{12}}{Z_{11} Z_{22} - Z_{21} Z_{12}}$$

Comparing I'_2 and I'_1 , we get

$$Z_{12} = Z_{21}$$

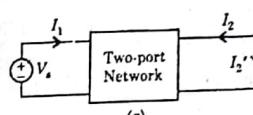

(a)

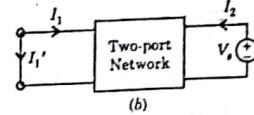

(b)

Q.8. (a) List the difference between tree & cotree. What is meant by the terms Tie set & Cut set?

Ans. The concept of a tree is now introduced. Consider a connected graph G with n nodes and b branches. A tree is defined as a connected graph which has no closed path. Alternatively, a tree graph is a connected graph in which there is a unique path between every pair of nodes. A tree is an important concept in linear graph theory.

A tree is defined as any set of branches in the original graph that is just sufficient to connect all the nodes. This number (of branches) is $n - 1$.

For a given graph it is possible to draw numerous trees. The tree branches are $(n - 1)$, which are called twigs. The remaining branches are called links. The branches of the graph which are not in the tree form the co-tree or complement of the tree. Link is any branch belonging to the co-tree. It is obvious that for each tree there exists a particular co-tree corresponding to that particular tree.

A graph, is then, the union of tree and its co-tree. This decomposition of a graph into tree and co-tree or its branches into twigs and links is not unique.

Number of twigs; $nt = n - 1$

Number of links; $nl = b - nt = b - n + 1$

A tree and its co-tree of graph.

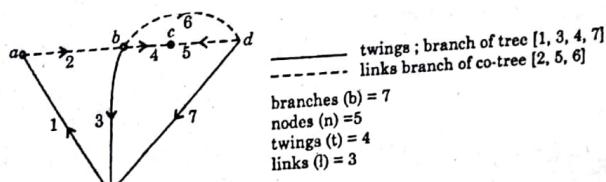


Fig. Tree and co-tree of the oriented linear graph

branches (b) = 7
nodes (n) = 5
twigs (t) = 4
links (l) = 3

twigs ; branch of tree [1, 3, 4, 7]
links branch of co-tree [2, 5, 6]

- The tree of a graph has the following properties.
1. In a tree, there exists one and only one path between any pair of nodes.
 2. Every connected graph has at least one tree.
 3. A connected subgraph of a connected graph is a tree if there exist all the nodes in the graph.
 4. Each tree has $(n - 1)$ branches
 5. The rank of a tree is $(n - 1)$; this is also the rank of the graph to which it belongs.

Q.8. (b) List the necessary & sufficient condition for +ve real function.

Ans. The necessary and sufficient conditions for a rational function $T(s)$ with real coefficients to be p.r. are:

Condition (1): $T(s)$ must have no poles in the right half of s -plane, i.e., Denominator $D(s)$ of $T(s)$ has a factor of the type $s^2 + a$, where a is positive real constant, imaginary axis ($j\omega$ -axis) with real and positive residues. This condition is tested by making partial fraction expansion of $T(s)$ and checking whether the residues of the poles on the $j\omega$ -axis are positive and real.

Condition (3): $\operatorname{Re}[T(j\omega)] \geq 0$, for all ω

or

$$A(\omega^2) = M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega) \geq 0; \text{ for all } \omega$$

Q.8. (c) Realize $F(s) = \frac{(s+2)(s+5)}{s(s+4)(s+6)}$ using Foster-I & Foster-II representation.

Ans. Foster - I form: Since we know that the residues of poles of $Z_{R-L}(s)$ are real and negative. So determine the residues of

$\frac{Z(s)}{s}$ as:

$$\begin{aligned} \frac{Z(s)}{s} &= \frac{(s+2)(s+5)}{(s+1)(s+4)} \\ &= \frac{s^2 + 5s + 4}{s^2 + 5s + 4} \left(\frac{s^2 + 7s + 10}{s^2 + 5s + 4} \right) \\ &= 1 + \frac{2s + 6}{(s+1)(s+4)} \end{aligned} \quad (6)$$

Using partial fraction expansion.

$$\frac{Z(s)}{s} = 1 + \frac{\frac{4}{3}}{s+1} + \frac{\frac{2}{3}}{s+4}$$

or,

$$Z(s) = s + \frac{\frac{4}{3}s}{s+1} + \frac{\frac{2}{3}s}{s+4}$$

Therefore, synthesized networks is shown in figure (a)

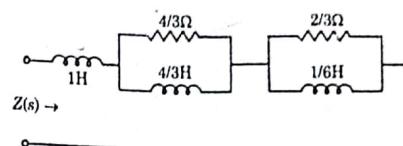


Fig. (a)

Foster-II form:
$$Y(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

Using partial fraction expansion, we have

$$Y(s) = \frac{2}{s} + \frac{1}{s+2} + \frac{4}{s+5}$$

Therefore, synthesized network is shown in figure (b).

(b) Cauer-I form:

$$Z(s) = \frac{s^3 + 7s^2 + 10s}{s^2 + 5s + 4}$$

As found in previous example.

$$Z_1 = s, Y_2 = \frac{1}{2}$$

$$Z_3 = s, Y_4 = 1, Z_5 = \frac{1}{2}s$$

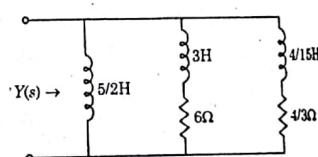


Fig. (b)

Therefore, the synthesized network shown in figure (c).

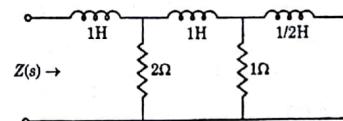


Fig. (c).

28-2014

Third Semester, Circuit & System

Cause-II form:

$$Z(s) = \frac{s^3 + 7s^2 + 10s}{s^2 + 5s + 4} = \frac{10s + 7s^2 + s^3}{4 + 5s + s^2}$$

or $Y(s) = \frac{4 + 5s + s^2}{10s + 7s^2 + s^3}$

As found in previous example,

$$Y_1 = \frac{2}{5s}, Z_2 = \frac{50}{11}, Y_3 = \frac{121}{235s}, Z_4 = \frac{2209}{44}, Y_5 = \frac{4}{47s}$$

Therefore, the synthesized network is shown in figure (d).

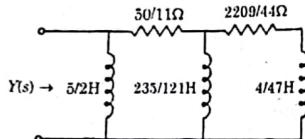
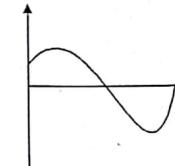



Fig. (d)

FIRST TERM EXAMINATION [SEPT. 2015]
THIRD SEMESTER [B.TECH]
CIRCUIT AND SYSTEMS

M.M. : 30

*Note: Question No.1 is compulsory and attempt any two from the rest.***Q.1. (i) What are Continuous-time and Discrete-time Signals? (10 × 1 = 0)****Ans.** Signal which has value for all instant of time is called continuous time signal and represented by $x(t)$. Eg:

$$x(t) = \sin t$$

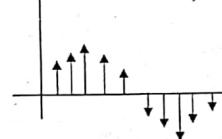Signal which has value for some particular instant of time is known as discrete time signal $x[n]$ **Q.1. (ii) What is a Gate Signal?****Ans.** Gate Signal

$$g_{t_0 t_1}(t) = \begin{cases} 1 & t_0 < t < t_1 \\ 0 & \text{otherwise} \end{cases} = u(t - t_0) - u(t - t_1)$$

Q.1. (iii) What is a Linear System?**Ans.** If $x_1(t)$ is an input of a signal and $y_1(t)$ is the output corresponding to input $x_1(t)$ and $x_2(t)$ is the output corresponding to input $x_2(t)$ and output corresponding to linear combination of $x_1(t)$ and $x_2(t)$ is equal to the linear combination of $y_1(t)$ and $y_2(t)$ then system is known as linear system.**Q.1. (iv) What are Singularity Functions?****Ans.** $\text{sign}(t) = \begin{cases} 1 & t > 0 \\ -1 & t < 0 \end{cases}$ **Q.1. (v) What do you understand by Waveform Synthesis?****Ans.** To express any deterministic signal into mathematical expression is known as waveform synthesis.**Q.1. (vi) Define the Time Constant of a series R-L Circuit.**


$$\text{Ans. } T = \frac{L}{R}$$

Q.1. (vii) What are the advantages of Laplace Transform technique?**Ans.** (i) The homogeneous equation and the particular integral of the solution are obtained in one operation.

(ii) It converts the integro-differential equation onto an algebraic equation in S

Q.1. (viii) Represent the following functions by suitable Waveforms:
 $u(-t-a)$ and $-r(-t+a)$

Ans.

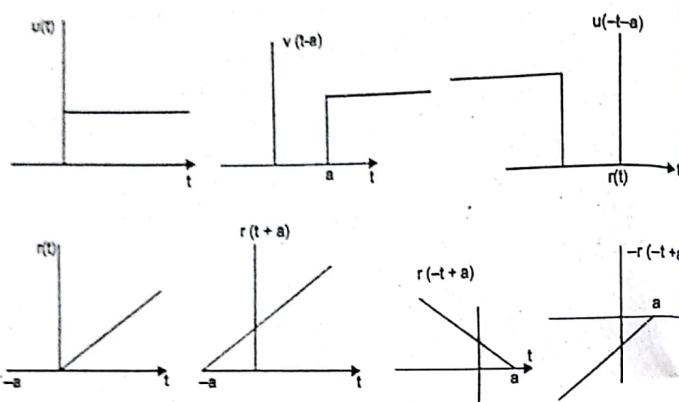

Q.1. (ix) What are Single Energy and Double Energy Transients?


Ans. If the systems contain only resistance Induction or capacitance for C than system is known as single energy transient. If the system contain L and C both then system is known as double energy transient.

Q.1. (x) Write down the expression for the current in an initially relaxed series R-C Circuit energized by a Step voltage.


Ans.

$$i(t) = \frac{1}{R} e^{-\frac{t}{RC}}$$

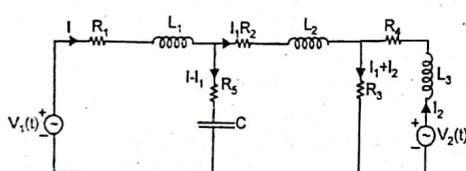Q.2. (a) Write down the Integro-Differential Equations for the electrical circuit shown in Fig (1) using KVL.



Ans.

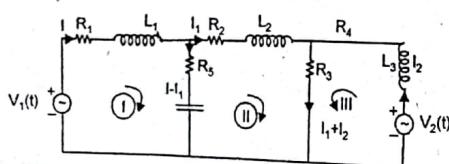

On Applying KVL in loop I

$$V_1(t) = IR_1 + L_1 \frac{dI}{dt} + (I - I_1)R_3 + \frac{1}{C} \int (I - I_1) dt$$

On Applying KVL in loop II

$$I_1 R_2 + L_2 \frac{dI_1}{dt} + (I_1 + I_2) R_3 = (I - I_1) R_5 + \frac{1}{C} \int (I - I_1) dt$$

On Applying KVL in loop III

$$V_2(t) = L_3 \frac{dI_3}{dt} + I_2 R_4 + (I_1 + I_2) R_5$$

Q.2. (b) A series circuit consisting of a resistance of 10Ω and an inductance of $2H$ is energized with a ramp function of 5 occurring at $t = 5$ seconds. Find the current $i(t)$ for any time $t \leq 0$ seconds, assuming the initial current through the inductance to be zero.

Ans.

$$t(u(t) - u(t-5))$$

Applying KVL


$$t(u(t) - u(t-5)) = 10I + 2 \frac{dI}{dt}$$

taking LT


$$= 10I(s) + 2sI(s) = \frac{1}{s^2} - LT((t-5)u(t-5) + 5u(t-5))$$

$$\frac{1}{s^2} - \frac{e^{-5s}}{s^2} - \frac{5e^{-5s}}{s} = I(s)(10 + 2s)$$
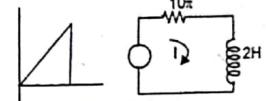
$$I(s) = \frac{1 - e^{-5s} - 5se^{-5s}}{s^2(10 + 2s)}$$



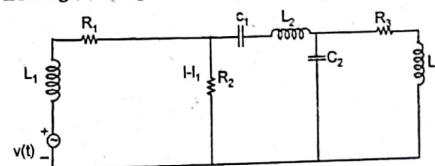Q.3. (a) Frame the performance equations in time domain for the electrical circuit shown in Fig (2) using KCL.




Ans.

Applying KCL at node 1.

$$\frac{1}{L_1} \int [V(t) - V_1(t)] = \frac{V_1 - V_2}{R_1}$$

Applying KCL at node 2
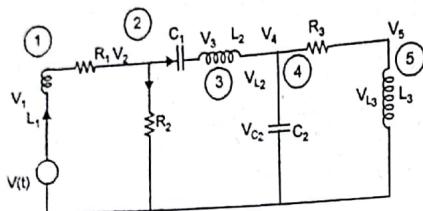
$$\frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} + C_1 \frac{d(V_2 - V_3)}{dt}$$



Applying KCL at node 3

$$C_1 \frac{d(V_2 - V_3)}{dt} = \frac{1}{L_2} \int (V_3 - V_4) dt$$

At node 4


$$\frac{1}{L_2} \int (V_3 - V_4) dt = C_2 \frac{dV_4}{dt} + \frac{V_4 - V_5}{R_3}$$

At node 5

$$\frac{V_4 - V_5}{R_3} = \frac{1}{L_3} \int V_5 dt$$

Q.3. (b) A voltage pulse of 20 volts magnitude and $10\mu s$ duration is applied to a series R-C Circuit. Determine the current in the circuit. Assume that the circuit is initially relaxed. The value of $R=10\Omega$ and $C=10\mu F$. (5)

Ans.

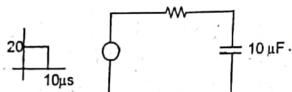 $20[u(t) - u(t-10)]$

Applying KVL

$$20[u(t) - u(t-10\mu s)] = I \times 10 + \frac{1}{10\mu F} \int I dt$$

taking LT


$$20 \left(\frac{1}{s} - \frac{e^{-10s}}{s} \right) = 10I(s) + 10^5 \frac{I(s)}{s}$$

$$I(s) = \frac{20(1 - e^{-10s})}{10s + 10^5}$$

$$= \frac{2(1 - e^{-10s})}{s + 10^4}$$

$$= 2e^{-10t} - 2e^{-10(t-10)}$$

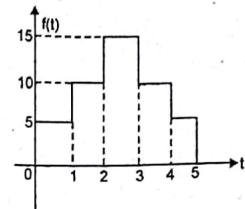Q.4. (a) Synthesize the following function into its component signals and hence find the mathematical equation for it. (5)




$$\text{Ans. } f(t) = 5(u(t) - u(t-1)) + 10[u(t-1) - u(t-2)] + 15[u(t-2) - u(t-3)] + 10[u(t-3) - u(t-4)] + 5[u(t-4) - u(t-5)]$$

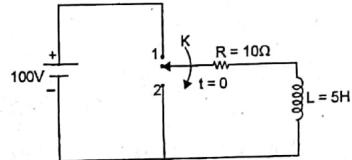Q.4. (b) The Switch in the circuit shown in Fig (3) is kept in position-1 for a sufficiently long time so that the Steady State Conditions are attained by the circuit. The switch 'K' is moved to position-2 at $t = 0$ sec. Obtain an expression for the circuit for any time, $t \geq 0$. Use Laplace transform Method.

Ans. When K at position 1 and steady state reach inductor behave as short circuit

$$L = \frac{V}{R} = \frac{100}{10} = 10A$$



when K at 2

$$5 \frac{dI}{dt} + I \times 10 = 0$$

$$\frac{dI}{dt} + 2I = 0$$

$$\begin{aligned} I &= Ae^{-2t} \\ t &= 0 \\ i &= 10A \end{aligned}$$

Putting this values en above equation $10 = Ae^0$

$$I = 10e^{-2t} \rightarrow A = 10$$

$$I = 10e^{-2t}$$

SECOND TERM EXAMINATION [NOV. 2015]
THIRD SEMESTER [B.TECH]
CIRCUITS AND SYSTEMS


M.M.:

Time. 1.30 Hours

Note: Question No. 1 is compulsory and attempt any two from the rest.

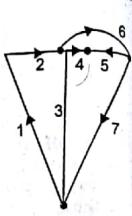
Q.1. (i) What is an Oriented Graph? Explain with an example. (10x1 = 10)

Ans. In a graph each branch carries an arrow to indicate its orientation of graph is known as oriented graph.



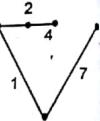Q.1. (ii) With reference to an Oriented Network Graph define (i) Tree and (ii) Co-tree

Ans. If three is this the 1,2,4,7 is twing and 3, 5, 6 is the co turg and 3, 5, 6 is the co tree or link



Q.1. (iii) What is a Tie-set Schedule?

Ans. Loop which contain only one link are independent are called basic fundamental loops or tie sets.

Q.1. (iv) Define h-Parameters for a two-port network.

Ans.

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \left. \frac{V_1}{V_2} \right|_{V_2=0}$$

$$h_{21} = \left. \frac{V_2}{V_1} \right|_{V_1=0}$$

$$h_{12} = \left. \frac{I_1}{V_2} \right|_{I_1=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

Q.1. (v) Define the Network Functions of a Single Port Network.

Ans. In single port network Network function is Impedance and transform admittance

$$Z(s) = \frac{V(s)}{I(s)}$$

$$Y(s) = \frac{I(s)}{V(s)}$$

Q.1. (vi) Write down the relationships between the Z-parameters and Y-parameters.

Ans.

$$Z_{11} = \frac{\Delta h}{h_{22}}$$

$$Z_{12} = \frac{h_{12}}{h_{22}}$$

$$Z_{21} = \frac{-h_{21}}{h_{22}}$$

$$Z_{22} = \frac{1}{h_{22}}$$

where $\Delta h = h_{11}h_{22} - h_{12}h_{21}$

I.P. University-(B.Tech)-Akash Books

2015-7

Q.1. (vii) What is the difference between the network analysis and network synthesis?

Ans. To Analysis any circuit is network analysis or to know all parameter of circuit is called network analysis.

Q.1. (viii) What are Hurwitz polynomials?

Ans. Hurwitz polynomial: Polynomial whose all roots lies in left side of imaginary axis.

Q.1. (ix) What do you mean by a Positive Real Function?

Ans. A Transfer function $T(s) = \frac{N(s)}{D(s)}$ is prf if

(1) $T(s)$ is real for all real value of s

(2) $D(s)$ is Hurwitz polynomial


(3) $T(s)$ may have pole on Jw axis

(4) Real part of $T(s)$ is greater than or equal to zero for the real part of s is greater than or equal to zero

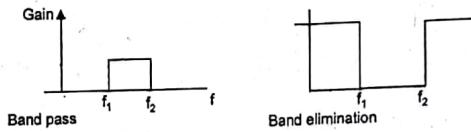Q.1. (x) What are Band pass and Band Elimination Filters?

Ans. A filter which pass a certain range frequency and reject other all frequency is called Band pass filter.

→ A filter which pass a certain range of frequency is known as Band elimination filter.



Q.2. (a) For the network Graph shown in Fig.1, identify the tie-sets and write the tie-set schedule on the basis of current variables. (5)


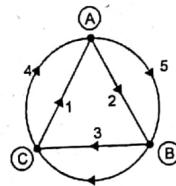
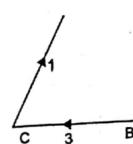


Fig. 1

Ans.

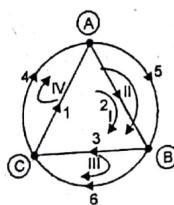

	1	2	3	4	5	6
loop 1	1	1	1	0	0	0
loop 2	1	0	1	0	1	0
loop 3	0	0	-1	0	0	1
loop 4	-1	0	0	1	0	0

Q.2. (b) Determine the Y-Parameters of the two-Port network shown in Fig.2.

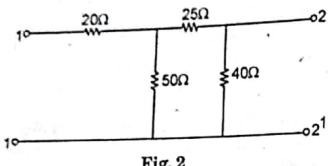


Fig. 2

Ans.


$$\begin{aligned} \frac{V_1 - V}{20} &= \frac{V}{50} + \frac{V - V_2}{25} \\ I_1 &= \frac{V}{50} + \frac{V - V_2}{25} \\ I_2 &= \frac{V_2 - V}{25} + \frac{V_2}{40} \\ I_1 &= \frac{V_1 - V}{20} \Rightarrow -20I_1 + V_1 = V \\ I_1 &= \frac{V_1 - 20I_1 + V_1 - 20I_1 - V_2}{50} \\ I_1 + \frac{20I_1}{50} + \frac{20I_1}{25} &= \frac{V_1}{50} + \frac{V_1 - V_2}{25} \\ \frac{110I_1}{50} &= \frac{3V_1 - V_2}{50} \\ I_1 &= \frac{3V_1 - V_2}{110 - 55} \end{aligned}$$

Putting the value of I_1 in equation (3)

$$I_2 = V_2 \left(\frac{1}{25} + \frac{1}{40} \right) - \frac{1}{25} \left(\frac{20V_2 - 60V_1}{55} \right)$$

Q.3. (a) Find $G_{21}(S)$ for the circuit shown in Fig.3.

(5)

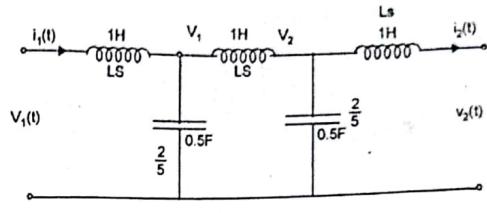

(Fig.3)

Ans.

$$\begin{aligned} G_{21}(s) &= \frac{V_2(s)}{V_1(s)} \text{ at } I_2 = 0 \\ Z_{eq}(s) &= \frac{\left(\frac{s+2}{s} \right) \frac{2}{s}}{\left(\frac{s+2}{s} + \frac{2}{s} \right)} + s \\ &= \frac{2(s^2+2)}{\frac{s^2+4}{s}} + s \\ &= \frac{2(s^2+2)s}{s(s^2+4)} + s \\ &= \frac{2s^2 + 4 + s^4 + 4s^2}{s(s^2+4)} \\ I_1 &= \frac{V_1}{\frac{s^4 + 6s^2 + 4}{s(s^2+4)}} = \frac{s(s^2+4)}{s^4 + 6s^2 + 4} V_1 \\ I &= \frac{\frac{2}{s} \times I_1}{\left(\frac{s+4}{s} \right)} = \frac{\frac{2}{s} \left(\frac{s(s^2+4)}{s^4 + 6s^2 + 4} \right) V_1}{\left(\frac{s+4}{s} \right)} \\ V_2 &= \frac{2}{s} \times I = \frac{2}{s} \times \frac{\frac{2}{s} \left(\frac{s(s^2+4)}{s^4 + 6s^2 + 4} \right) V_1}{\left(\frac{s+4}{s} \right)} V_1 \\ \frac{V_2}{V_1} &= \frac{4(s^2+4)}{(s^4 + 6s^2 + 4)(s^2+4)} \end{aligned}$$

10-2015

Third Semester, Circuit and Systems

Q.3. (b) Test the polynomial $Q(s) = s^6 + 2s^5 + 6s^4 + 10s^3 + 8s^2 + 8s + 4$ for Hurwitz property.

$$\text{Ans. } s^6 + 2s^5 + 6s^4 + 10s^3 + 9s^2 + 8s + 4$$

$$\begin{array}{r} 2s^5 + 10s^3 + 8s \\ \underline{-s^6 + 5s^4 + 4s^2} \\ \hline s^4 + 5s^2 + 4 \end{array} \left(\begin{array}{l} s^6 + 6s^4 + 9s^2 + 4 \\ \underline{-s^6 + 5s^4 + 4s^2} \\ \hline 2s^4 + 5s^2 + 4 \end{array} \right) \begin{array}{r} 2s^5 + 10s^3 + 8s \\ \underline{2s^5 + 10s^3 + 8s} \\ \hline X \end{array}$$

$$\begin{array}{l} 2s^5 + s^4 + 5s^2 + 4 + 10s^3 + 8s \\ (2s + 1)(s^4 + 5s^2 + 4) \\ (2s + 1) \text{ is Hurwitz} \end{array}$$

$$\begin{array}{r} 4s^3 + 10s \\ \underline{-s^4 \pm 10s^2} \\ \hline \frac{4}{2}s^2 + 4 \end{array} \left(\begin{array}{l} s^4 + 5s^2 + 4 \\ \underline{-s^4 \pm 10s^2} \\ \hline 4s^3 + 10s \end{array} \right) \begin{array}{l} \frac{8}{5}s \\ \underline{-4s^3 + 32s} \\ \hline \frac{18}{5}s \end{array} \left(\begin{array}{l} \frac{5}{2}s^2 + 4 \\ \underline{\frac{5}{2}s^2} \\ \hline 4 \end{array} \right) \begin{array}{l} \frac{25}{36} \\ \underline{\frac{5}{2}s^2} \\ \hline 4 \end{array} \left(\begin{array}{l} \frac{18}{5}s \\ \underline{\frac{5}{2}s^2} \\ \hline 4 \end{array} \right) \begin{array}{l} \frac{20}{18}s \\ \underline{\frac{15}{2}s} \\ \hline X \end{array}$$

all coefficient is the Positive So function is Hurwitz.

Q.4. (a) Realize the following driving point impedance function (i) as a first Foster Form and (ii) as a Second Foster of LC Networks.

$$Z(s) = \frac{s^3 + 4s}{2s^4 + 20s^2 + 18}$$

Ans. From the pole zero diagram

$$Z(s) = \frac{K(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

By putting

$$Z(-2) = \frac{130}{16} = \frac{K \cdot 5 \cdot 13}{-2 \cdot 8} \text{ gives } K = 2$$

Therefore,

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

(a) Foster -I Form:

$$\begin{array}{r} s^3 + 4s \\ \underline{2s^4 + 20s^2 + 18} \\ \hline 2s^4 + 8s^2 \\ \hline 12s^2 + 18 \end{array}$$

I.P. University-(B.Tech)-Akash Books

2015-11

$$Z(s) = 2s + \frac{12s^2 + 18}{s(s^2 + 4)}$$

Using partial fraction expansion,

$$\begin{array}{l} \frac{12s^2 + 18}{s(s^2 + 4)} = \frac{A}{s} + \frac{Bs + C}{s^2 + 4} \\ A = 9/2, C = 0 \text{ and } B = \frac{15}{2} \end{array}$$

Therefore,

$$Z(s) = 2s + \frac{\frac{9}{2}}{s} + \frac{\frac{15}{2}s}{s^2 + 4}$$

We then obtain the synthesized network in figure 1(a).

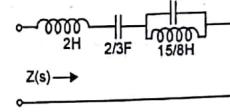


Fig. 1.(a)

Foster-II form:

$$Y(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$$

Using partial fraction expansion,

$$\begin{array}{l} \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)} = \frac{1}{2} \left[\frac{As + B}{s^2 + 1} + \frac{Cs + D}{s^2 + 9} \right] \\ A = \frac{3}{8}, B = D = 0, C = \frac{5}{8} \end{array}$$

Therefore,

$$\begin{aligned} Y(s) &= \frac{1}{2} \left[\frac{\frac{3}{8}s}{s^2 + 1} + \frac{\frac{5}{8}s}{s^2 + 9} \right] \\ &= \frac{\frac{3}{16}s}{s^2 + 1} + \frac{\frac{5}{16}s}{s^2 + 9} \end{aligned}$$

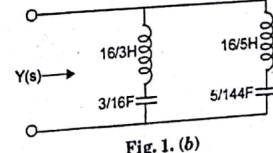


Fig. 1.(b)

12-2015

Third Semester, Circuit and Systems

Hence, synthesized network is shown in figure 1 (b).

(b) Cauer-I form:

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} = \frac{2s^4 + 20s^2 + 18}{s^3 + 4s}$$


The continued fraction expansion is

$$\begin{aligned} & \frac{s^3 + 4s}{2s^4 + 6s^2} \cdot \frac{2s^4 + 20s^2 + 18}{2s^4 + 8s^2} \leftrightarrow Z_1 \\ & \frac{12s^2 + 18}{12s^2 + 18s^3 + 4s} \cdot \frac{12s^2 + 18s^3 + 4s}{12s^2 + 18} \leftrightarrow Y_2 \\ & \frac{s^3 + 3s}{s^3 + 3s} \cdot \frac{12s^2 + 18}{12s^2} \leftrightarrow Z_2 \\ & \frac{\frac{5}{2}}{\frac{5}{2}} \cdot \frac{12s^2 + 18}{12s^2} \cdot \frac{\frac{2}{5} \times 12s}{5} = \frac{24}{5} s \leftrightarrow Z_3 \\ & \frac{18}{18} \cdot \frac{\frac{5}{2} s}{\frac{5}{2} s} \cdot \left(\frac{1}{18} - \frac{1}{18}s \right) = \frac{1}{18} s \leftrightarrow Y_4 \\ & \frac{5}{2} s \xrightarrow{x} \end{aligned}$$

Therefore, the final synthesized network is shown in figure 1. (c).

Cauer-II form:
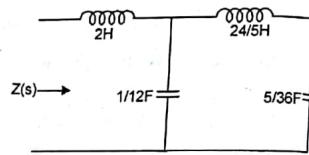
$$\begin{aligned} Z(s) &= \frac{2s^4 + 20s^2 + 18}{s^3 + 4s} \\ &= \frac{18 + 20s^2 + 2s^4}{4s + s^3} \end{aligned}$$



The Continued fraction expansion is

Fig. 1(c)

$$\begin{aligned} & \frac{4s + s^3}{18 + \frac{9}{2}s^2} \cdot \frac{18 + 20s^2 + 2s^4}{4s + s^3} \left(\frac{18}{4s} = \frac{9}{2s} \right) \leftrightarrow Z_1 \\ & \frac{\frac{31}{2}s^2 + 2s^4}{\frac{31}{2}s^2 + 2s^4} \cdot \frac{4s + s^3}{\frac{31}{2}s^2 + 2s^4} \left(\frac{2}{31} \cdot \frac{4}{S} = \frac{8}{31s} \right) \leftrightarrow Y_2 \\ & \frac{4s \cdot \frac{16}{13}s^3}{\frac{15}{2}s^2} \cdot \frac{\frac{31}{2}s^2 + 2s^4}{\frac{31}{2}s^2 + 2s^4} \left(\frac{31}{15} \cdot \frac{31}{2s} = \frac{961}{30s} \right) \leftrightarrow Z_3 \\ & \frac{\frac{31}{2}s^2}{2s^4} \cdot \frac{\frac{15}{2}s^2}{\frac{15}{2}s^2} \left(\frac{1}{2} \cdot \frac{15}{31s} = \frac{15}{62s} \right) \leftrightarrow Y_4 \\ & \frac{15}{31}s^3 \xrightarrow{x} \end{aligned}$$

Therefore, the final synthesized network is shown in figure 1 (d).

I.P. University-(B.Tech)-Akash Books

2015-13


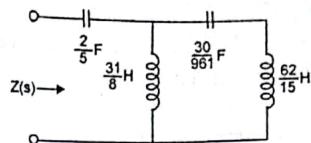


Fig. 1 (d)

Q.4. (b) Design a Band Pass Filter having a Design impedance of 400Ω and cut off frequencies of 2 KHz and 8 KHz.

Ans.

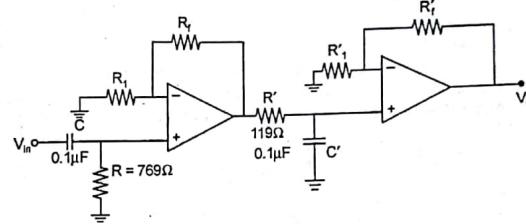

Given that

and

we know that

$$f = 2 \text{ KHz for HPF}$$

$$f = 8 \text{ KHz for LPF}$$

Let

$$f = \frac{1}{2\pi RC}$$

$$C = 0.1 \mu\text{F} \text{ then}$$

$$2 \times 10^3 = \frac{1}{2\pi \times R \times 0.1 \mu\text{F}}$$

$$R = \frac{1}{2 \times 3.14 \times 2 \times 10^3 \times 0.1 \times 10^{-6}} = 796 \Omega$$

Also

$$8 \text{ KHz} = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2 \times 3.14 \times 8 \times 10^3 \times 0.1 \times 10^{-6}}$$

$$R = 199 \Omega$$

∴

∴

∴

∴

END TERM EXAMINATION [DEC. 2015]
THIRD SEMESTER [B. TECH]
CIRCUIT AND SYSTEM

MM : 75

Time: 3 Hrs.

Note: Attempt any five question including Q no. 1, which is compulsory. Select one question from each unit.

Q.1. (a) Determine the following systems are LT1, causal or not. (5)

$$(i) y(t) = t^2 x(t-1)$$

$$(ii) y(n) = \sum_{k=n_0}^{n+n_0} x(k)$$


Ans.

$$y(t) = t^2 x(t-1)$$


(i) Present output depends on only past input so system is causal.

(ii) Present output depends on past and future input so system is non causal.

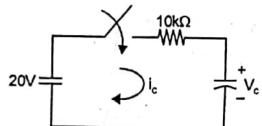Q.1. (b) The switch in the following circuit is closed at $t = 0$, determine the equations for capacitor voltage and current. Compute v_c and i_c at $t = 50$ ms. (5)



Ans.

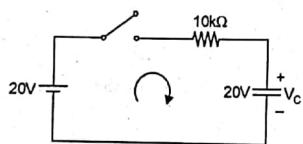

$$20 = 10^4 I + \frac{1}{C} \int I dt$$

On differentiating we get

$$\frac{1}{C} I + 10^4 \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} + \frac{1}{10^4 C} I = 0$$

$$I = A e^{-\frac{t}{10^4 C}}$$

... (1)

at

$$t = 0 \quad I = \frac{20}{10^4} = 2 \times 10^{-3} A$$

$$V = \frac{1}{C} \int I dt = \frac{1}{C} \int A e^{-t/10^4 C} dt$$

... (2)

I.P. University-[B. Tech]-Akash Books

2015-15

Putting the value of initial condition we get

$$A = 2 \times 10^{-3} A$$

$$I = 2 \times 10^{-3} e^{-\frac{t}{10^4 C}}$$

Q.1. (c) Find Laplace transform of $\frac{1}{4} t \sin(2t) u(t)$. (5)


$$\text{Ans. LT } \sin 2t \rightarrow \frac{2}{s^2 + 2^2}$$

Applying differentiation property we get

$$\text{LT of } t \sin 2t \rightarrow \frac{d \left(\frac{2}{s^2 + 2^2} \right)}{ds} = \frac{2s \times 2}{(s^2 + 4)^2} = \frac{4s}{(s^2 + 4)^2}$$


$$\text{So LT of } \frac{1}{4} t \sin 2t = \frac{s}{(s^2 + 4)^2}$$

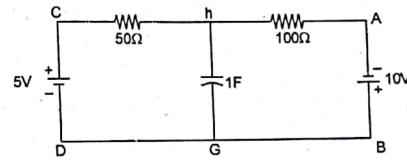Q.1. (d) For the following circuit draw directed graph and write incidence matrix. (5)




Ans.
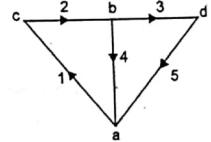
$$\begin{matrix} 1 & 2 & 3 & 4 & 5 \\ a & 1 & 0 & 0 & -1 & -1 \\ b & 0 & -1 & 1 & 1 & 0 \\ c & -1 & 1 & 0 & 0 & 0 \\ d & 0 & 0 & -1 & 0 & 1 \end{matrix}$$





Q.1. (e) Write down Foster I, II and Caur I, II forms of circuit synthesis. (5)

Ans. Foster I.

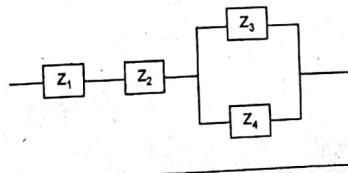

16-2015

Third Semester, Circuit and Systems

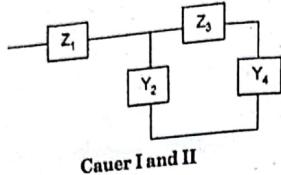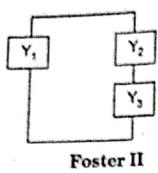


UNIT-I

Q.2. (a) Find E_x for the signal $x(t) = \delta(t+2) - \delta(t-2)$.
Ans. $x(t) = \delta(t+2) - \delta(t-2)$

$$E_x = \int |x(t)|^2 dt = \int (\delta^2(2t+2) + \delta^2(t-2) - 2\delta(t+2)\delta(t-2))dt = 1 + 1 = 2$$

Q.2. (b) Switch of the following circuit is opened at $t = 0$ after a long time.
Write expression for $v(t)$ at $t > 0$. (6.5)

Ans.

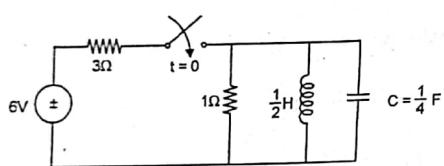

$t < 0$ inductor work as short circuit and capacitor as open circuit then current through conductor is $I = \frac{6}{3} = 2A$ and

$$c \frac{dV_c}{dt} = \frac{1}{L} \int V_c dt + \frac{v_c}{1}$$

$$\frac{1}{4} \frac{dv_c}{dt} = 2 \int v_c dt + v_c$$

On differentiating the above eqn.

$$\frac{1}{4} \frac{d^2v_c}{dt^2} = 2v_c + \frac{dv_c}{dt}$$

$$\frac{d^2v_c}{dt^2} - 4 \frac{dv_c}{dt} - 8v_c = 0$$

$$v_c = Ae^{-(2+2\sqrt{3})t} + Be^{-(2-2\sqrt{3})t}$$

$$\alpha, \beta = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{4 \pm \sqrt{16 - 4 \times 1 \times -8}}{2}$$


$$= \frac{4 \pm \sqrt{48}}{2} = 2(1 \pm \sqrt{3}).$$

(6)



I.P. University-[B. Tech]-Akash Books

2015-17

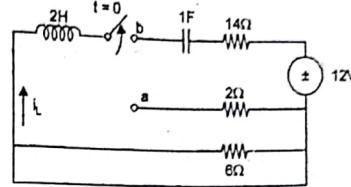Q.3. For the following circuit switch is moved from position (a) to (b) at $t = 0$. Then find $i_1(t)$ for $t > 0$. (12.5)



Ans.

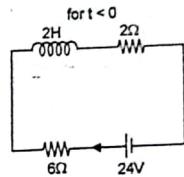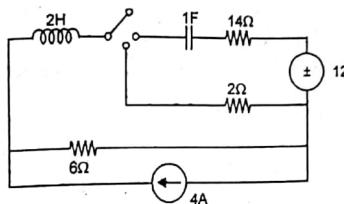


Inductor work as short circuit

$$I = \frac{24}{8} = 3A$$

$$24 - 12 = 20I + 2 \frac{dI}{dt} + \frac{1}{1} \int I dt$$
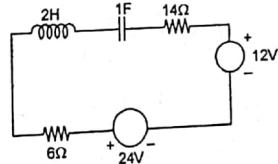
$$12 = 20I + 2 \frac{dI}{dt} + \int I dt$$



On differentiating both side we get

$$2 \frac{d^2I}{dt^2} + 20 \frac{dI}{dt} + I = 0$$

$$\frac{d^2I}{dt^2} + 10 \frac{dI}{dt} + .5I = 0$$

$$I = A e^{-0.36t} + B e^{-9.97t}$$

$$\alpha, \beta = \frac{-10 + \sqrt{100 - 4 \times 5}}{2}$$

$$= \frac{-10 \pm \sqrt{98}}{2} = -5 \pm \frac{7}{2}\sqrt{2} = .036 - 9.97$$

UNIT-II

Q.4. Consider the following circuits, the two switches are closed simultaneously at $t = 0$. The voltage on capacitor C_1 and C_2 before the switches are closed are 1 and 2V respectively.

(a) Find the currents $i_1(t)$ and $i_2(t)$.

Ans. Applying KVL in Loop 1

$$4 = (I_1 + I_2)2 + \int I_1 dt$$

$$2 = (I_1 + I_2)2 + \int I_2 dt$$

Applying LT on both equation we get

$$\frac{4}{s} = 2I_1(s) + \frac{I_1(s)}{s} + 2I_2(s)$$

$$\frac{2}{s} = 2I_1(s) + 2I_2(s) + \frac{I_2(s)}{s}$$

or

$$\left[I_1(s) \left(2 + \frac{1}{s} \right) + 2I_2(s) = \frac{4}{s} \right] \times 2$$

$$\left[I_1(s) 2 \pm \left(2 + \frac{1}{s} \right) I_2(s) = \frac{2}{s} \right] \left(2 + \frac{1}{s} \right)$$


$$\left[4 - \left(2 + \frac{1}{s} \right)^2 \right] I_2(s) = \frac{8}{s} - \frac{4}{s} - \frac{2}{s^2}$$

$$I_2(s) = \frac{\frac{4s-2}{s^2}}{4 - 4 - \frac{2}{s} - \frac{1}{s^2}} = \frac{\frac{12s+2}{s^2}}{\frac{8s^2+2s+1}{s^2}} = \frac{12s+2}{8s^2+2s+1}$$


$$= \frac{2(s-1)}{-(2s+1)}$$

$$I_1(s) = \frac{8}{5} +$$

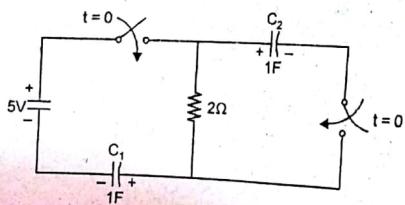Q.4. (b) Find capacitor voltages at $t = 0$.



Ans.

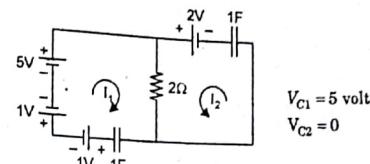

Q.5. (a) For the LTI system described by the following differential equation determine system function $H(s)$.

$$y''(t) + y'(t) - 2y(t) = x(t)$$

Ans.

$$y''(t) + y'(t) - 2y(t) = x(t)$$

Taking LT $s^2 Y(s) + s Y(s) - 2 Y(s) = X(s)$

$$\frac{Y(s)}{X(s)} = \frac{1}{s^2 + s - 2}$$

$$H(s) = \frac{1}{s^2 + s - 2}$$

Q.5. (b) Find Inverse Laplace transform of

$$X(s) = \frac{2 + 2s e^{-2s} + 4 e^{-4s}}{s^2 + 4s + 3} \quad \text{Re } S > -1$$

$$\text{Ans. } X(s) = \frac{2 + 2s e^{-2s} + 4 e^{-4s}}{s^2 + 4s + 3} = \frac{2}{s^2 + 4s + 3} + \frac{2s e^{-2s}}{s^2 + 4s + 3} + \frac{4 e^{-4s}}{s^2 + 4s + 3}$$

$$\text{LT of } \frac{2}{(s+3)(s+1)} = \frac{A}{s+3} + \frac{B}{s+1}$$

$$A = \frac{2}{(s+3)(s+1)}(s+3) \Big|_{s=-3} = \frac{2}{-2} = -1$$

$$B = \frac{2}{(s+3)(s+1)}(s+1) \Big|_{s=-1} = 1$$

$$X(s) = \frac{-1}{s+3} + \frac{1}{s+1} + \frac{-se^{-2s}}{s+3} + \frac{se^{-2s}}{s+1} - \frac{2e^{-4s}}{s+3} + \frac{2e^{-4s}}{s+1}$$

taking ILT


$$r(t) = -e^{-3t} + e^{-t} - e^{-3t}$$

UNIT-III


Q.6. Determine the fundamental cut set and fundamental loop matrix for the following graph. Where solid lines are twigs and dotted lines are links.

20-2015

Third Semester, Circuit and Systems

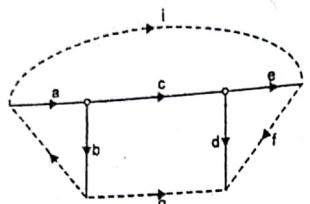


Ans.

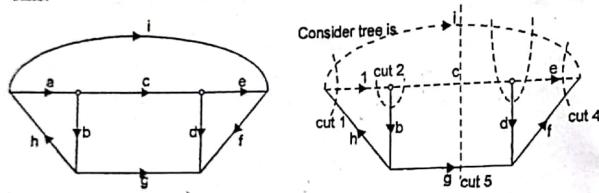

Twig are h, b, g, d, f
Link are a, c, e, i

	a	b	c	d	e	f	g	h	i
cut 1	-1	0	0	0	0	0	0	1	-1
cut 2	-1	1	1	0	0	0	0	0	0
cut 3	0	0	-1	1	1	0	0	0	0
cut 4	0	0	0	0	1	1	0	0	1
cut 5	0	0	1	0	0	0	1	0	1

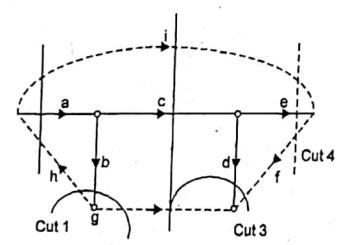


Fundamental cutset Matrix

	a	b	c	d	e	f	g	h	i
cut 1	1	0	0	0	0	0	0	-1	1
cut 2	0	1	0	0	0	0	-1	-1	0
cut 3	0	0	1	0	-1	1	0	0	0
cut 4	0	0	0	1	1	0	0	0	1
cut 5	0	0	1	0	0	1	0	0	1


I.P. University-(B. Tech)-Akash Books

2015-21

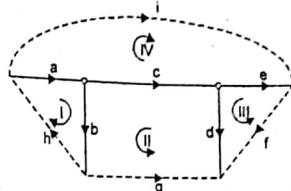

Fundamental loop matrix

	a	b	c	d	e	f	g	h	i
loop 1	1	1	0	0	0	0	0	0	1
loop 2	0	1	-1	-1	0	0	1	0	0
loop 3	0	0	0	1	-1	1	0	0	0
loop 4	-1	0	-1	0	-1	0	0	0	1

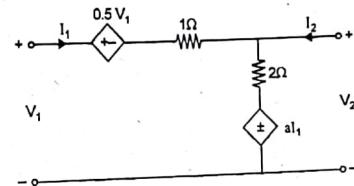Q.7. (a) For what value of a is the following circuit reciprocal. (6)


Ans.

On applying KVL in loop I

$$V_1 - 0.5V_1 - al_1 = I_1 + 2(I_1 + I_2)$$

$$.5V_1 = (3+a)I_1 + 2I_2$$
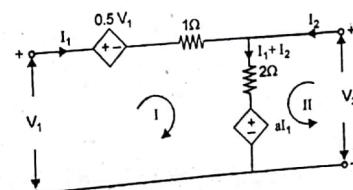
$$V_1 = (6+2a)I_1 + 4I_2 \quad \dots(1)$$




Applying KVL in loop 2


$$\begin{aligned} V_2 &= 2(I_1 + I_2) + aI_1 \\ V_2 &= (2+a)I_1 + 2I_2 \\ z_{11} &= (6+2a) \quad z_{12}=4 \\ z_{21} &= 2+a \quad z_{22}=2 \end{aligned}$$

for Reciprocity

$$\begin{aligned} z_{12} &= z_{21} \\ 2+a &= 4 \Rightarrow a=2 \end{aligned}$$

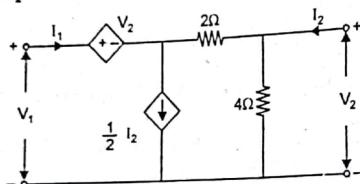Q.7. (b) Find h parameters of the following circuit.

Ans.

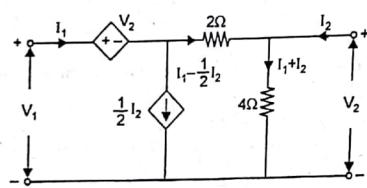

$$\begin{aligned} V_1 - V_2 &= 2\left(I_1 - \frac{1}{2}I_2\right) + 4\left(I_1 + \frac{I_2}{2}\right) \\ V_2 &= 4\left(I_1 + \frac{I_2}{2}\right) \\ V_1 - V_2 &= 6I_1 + I_2 \\ V_2 &= 4I_1 + 2I_2 \\ V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

Putting the value of I_2 from equation 2 to equation 1.

$$V_1 - V_2 = 6I_1 + \frac{V_2}{2} - 2I_1$$

$$V_1 = 4I_1 + \frac{3}{2}V_2$$

$$I_2 = \frac{-4I_1 + V_2}{2}$$

$$h_{11} = 4 \quad h_{21} = -2$$

$$h_{12} = \frac{3}{2} \quad h_{22} = \frac{1}{2}$$

Q.8. (a) What are the properties of Hurwitz Polynomial.

Ans. Properties of Hurwitz Polynomial.

Hurwitz polynomial $P(s)$ have the following properties:(i) If the polynomial $P(s)$ can be written as

$$P(s) = a_n s^n + a_{n-1}s^{n-1} + \dots + a_1 s + a_0$$

Then, All the coefficients a_i must be positive. A corollary is that between the highest order term in s and the lowest order term, none of the coefficients may be zero unless the polynomial is even or odd. In other words, $a_{n-1}, a_{n-2}, \dots, a_2, a_1$ must not be zero if the polynomial is neither even nor odd.

(ii) Both the odd and even parts of a Hurwitz polynomial $P(s)$ have roots on the $j\omega$ -axis only. If we denote the even part of $P(s)$ as $M(s)$ and the odd part as $N(s)$, so that

$$P(s) = M(s) + N(s) \dots$$

then $M(s)$ and $N(s)$ both have roots on the $j\omega$ -axis only.

(iii) As a result of property (ii), if $P(s)$ is either even or odd, all its roots are on the $j\omega$ -axis (including origin).

(iv) The continued fraction expansion of the ratio ($\psi(s)$) of the odd to even parts ($N(s)/M(s)$) or the even to odd parts ($M(s)/N(s)$) of a Hurwitz polynomial yields all positive quotient terms. As,

$$\begin{aligned} \psi(s) &= \frac{N(s)}{M(s)} \text{ or } \frac{M(s)}{N(s)} = q_1 s + \frac{1}{q_2 s + \frac{1}{\dots}} \\ &\quad + \frac{1}{q_n s} \end{aligned}$$

Where the quotients q_1, q_2, \dots, q_n must be positive if the polynomial $P(s) = M(s) + N(s)$ is Hurwitz.

(v) If $P(s)$ is Hurwitz polynomial and $W(s)$ is a multiplicative factor. Then $P_1(s) = P(s), W(s)$ is also Hurwitz polynomial, if $W(s)$ is Hurwitz polynomial.

(vi) In case the polynomial is either only even or only odd, it is not possible to obtain the continued fraction expansion in such cases, the polynomial $P(s)$ is Hurwitz if the ratio of $P(s)$ and its derivative $P'(s)$ gives a continued fraction expansion.

Q.8. (b) $F(s) = \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$ check whether the function is positive real or not.

$$(6.5)$$

$$F(s) = \frac{s^2 + 4s + 3}{s^2 + 6s + 8} = \frac{(s+3)(s+1)}{(s+2)(s+4)} = \frac{N(s)}{D(s)}$$

Ans.

1. All pole of the $D(s)$ lies on the $-ve$ side of real axis.

2. No any pole on imaginary axis.

3. $M_1 M_2 - N_1 N_2 \geq 0$ for all value of ω

$$M_1 = s^2 + 3 \quad M_2 = s^2 + 8$$

$$N_1 = 4s \quad N_2 = 6s$$

$$(s^2 + 3)(s^2 + 8) - 4s \cdot 6s = s^4 - 13s^2 + 24$$

24-2015

Third Semester, Circuit and Systems

Putting

$$\begin{aligned} s &\rightarrow j\omega \\ &= \omega^4 + 13\omega^2 + 24 \end{aligned}$$

this is always +ve for any value of ω

So function is P.R.F

Q.9. Realize $Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$ by cauer-I form.**Ans.**

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

$$\begin{aligned} s^2 + s + 1 &\left| \begin{array}{l} s^2 + 2s + 2 \\ -s^2 - s - 1 \\ \hline s + 1 \end{array} \right. \quad (s \leftrightarrow z_1) \\ &\underline{-} \quad \underline{-} \\ s + 1 &\left| \begin{array}{l} s^2 + s + 1 \\ -s^2 - s - 1 \\ \hline 0 \end{array} \right. \quad (s \leftrightarrow y_2) \\ &\underline{\underline{-}} \quad \underline{\underline{-}} \\ 1 &\left| \begin{array}{l} s + 1 \\ -s \\ \hline 1 \end{array} \right. \quad (s \leftrightarrow z_3) \\ &\underline{\underline{\underline{-}}} \quad \underline{\underline{\underline{-}}} \\ 1 &\left| \begin{array}{l} 1 \\ -1 \\ \hline X \end{array} \right. \quad (s \leftrightarrow y_4) \end{aligned}$$

MID TERM EXAMINATION [SEPT. 2016]
THIRD SEMESTER [B.TECH]
CIRCUITS AND SYSTEMS [ETEE-207]

M.M.: 30

Time: 1½ Hrs.

(12.5) Note: Answer any three questions. All questions carry equal marks.

Q.1. (a) Define a signal and also describe the different types of the signals. (4)

Ans. A signal may be considered to be a function of time that represents a physical variable of interest associated with a system.

Types of Signal

1. Continuous time signal
2. Discrete time signal

On the basis of symmetry

1. Even signal
2. Odd-signal

On the basis of periodicity

1. Periodic signal
2. Non periodic signal

On the basis of power and energy

1. Power signal
2. Energy signal

Basic Signal


1. Step Signal: $f_s(t)$ is defined by

$$f_s(t) = \begin{cases} 0; t < 0 \\ K; t \geq 0 \end{cases}$$

where K is the amplitude of step signal


2. Ramp Signal: $f_r(t)$ is defined by

$$f_r(t) = \begin{cases} 0; t < 0 \\ Kt; t \geq 0 \end{cases}$$

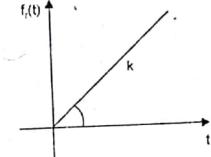 K is the slope of ramp signal.

3. Impulse Signal: $f_\delta(t)$ is defined by

$$f_\delta(t) = \begin{cases} 0; t \neq 0 \\ A; t = 0 \end{cases}$$

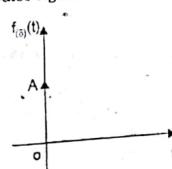
where A is the area of impulse signal.

Other Basic Signals

1. Unit Doublet Signal: If a unit impulse signal $\delta(t)$ is differentiated w.r.t t , we get


2-2016

Third Semester, Circuits and Systems

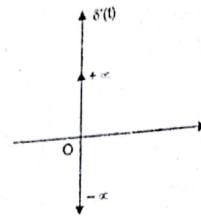

$$\delta(t) = \frac{d}{dt}[(\delta t)] = +\infty \text{ and } -\infty; t=0 \\ = 0; t \neq 0$$


2. Exponential Signal

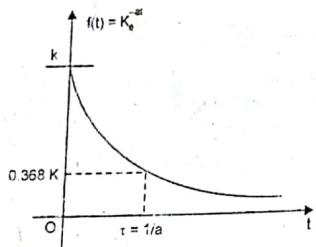

$$f(t) = \begin{cases} 0 & ; t \leq 0 \\ K_0 e^{-at} & ; t \geq 0 \end{cases}$$

where a and K_0 are real constants.

3. Sinusoidal Signal

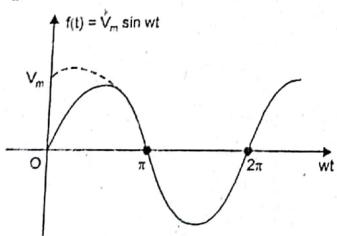

$$f(t) = \begin{cases} 0 & ; t < 0 \\ V_m \sin wt & ; t \geq 0 \end{cases}$$

Q.1. (b) Draw the waveform of the signal represented by the mathematical equation $V(t) = 2tu(t) - 2(t-1)u(t-1) - 2u(t-3)$ and find its Laplace Transformation.

Ans. $V(t) = 2tu(t) - 2(t-1)u(t-1) - 2u(t-3)$

I.P. University-[B.Tech]-Akash Books

2016-3

If $0 < t < 1$

Only

Then

If

$$= 2[tu(t) - (t-1)u(t-1) - u(t-3)]$$

$$u(t) = 1 \text{ and } u(t-1) = u(t-3) = 0$$

$$V(t) = 2t - 2t + 2 = 2$$

When

$$1 < t < 3$$

$$u(t) = u(t-1) = 1 \text{ and } u(t-3) = 0$$


$$V(t) = 2t - 2t + 2 = 2$$

$$t > 3$$

$$u(t) = u(t-1) = u(t-3) = 1$$

$$V(t) = 2t - 2t + 2 - 2 = 0$$

The final wave.

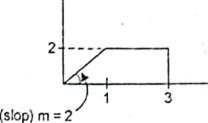

Q.2. (a) What is LTI System and describe its properties in detail? (6)

Ans. LTI Systems

A system is instantaneous (or memoryless or zero memory or without memory) if its output at any time depends only on the value of the input at the same time, otherwise dynamic i.e., a dynamic system or system with memory is one whose output depends on past or future values of the input or past values of output in addition to the present input.

A without memory continuous-time LTI system has the form

$$y(t) = Kx(t) \quad (\text{where } K \text{ is any constant})$$

Its impulse response

$$h(t) = K\delta(t)$$

Similarly, the form of a without memory discrete-time LTI system and its corresponding impulse response we $y[n] = Kx[n]$ and $h[n] = K\delta[n]$, respectively.

Note that if $K = 1$, then these systems become identity systems, with outputs equal to the inputs and with unit impulse responses equal to the unit impulse signals, i.e.,

$$h(t) = 0; \text{ for } t \neq 0 \text{ and } h[n] = 0; \text{ for } n \neq 0$$

In this case, the convolution integral and sum formulas imply that

$$x(t) = x(t) * \delta(t) \text{ and } x[n] = x[n] * \delta[n]$$

If an LTI system has an impulse response $h(t)$ or $h[n]$ that is not identically zero for $t \neq 0$ or $n \neq 0$, respectively, then the system is with memory or dynamic.

2. Causality of LTI Systems: A system is causal or non-anticipative if the output of the system at any time depends only on values of the input at the present time and in the past otherwise non-causal i.e., a non-causal system is the system whose output depends (or anticipate) future values of the input.

A continuous-time LTI system to be causal, output $y(t)$ must not depend on input $x(\tau)$ for $\tau > t$. This results

$$h(t) = 0 \quad \text{for } t < 0$$

Similarly, for a causal discrete-time LTI system the output $y[n]$ depends on input $x[k]$ for $k < n$. This results $h[n] = 0$ for $n < 0$.

That is the impulse response of a causal LTI system must be zero before the impulse occurs.

More generally, causality for an LTI system is equivalent to the condition of initial rest. And the system output is

$$y(t) = \int_{-\infty}^t x(\tau) h(t-\tau) d\tau \quad \text{or} \quad y[n] = \sum_{k=-\infty}^n x[k] h[n-k]$$

In other words, the causality of an LTI system is equivalent to its impulse response being a causal signal.

3. Invertibility of LTI Systems: A system is invertible only if an inverse system exists that, when cascaded with the original system, yields an output equal to the input to the first system. Here, if an LTI system is invertible, then it has an LTI inverse.

If we have an LTI system with impulse response $h(t)$ or $h[n]$, then inverse system with impulse response $g(t)$ or $g[n]$, must satisfy

$$h(t) * g(t) = \delta(t)$$

$$\text{or} \quad h[n] * g[n] = \delta[n]$$

4. Stability of LTI Systems: An LTI system is said to stable if the impulse response is absolutely integrable in case of continuous-time or absolutely summable in case of discrete-time systems, i.e.,

$$\int_{-\infty}^{\infty} |h(\tau)| d\tau < \infty \quad \text{or} \quad \sum_{k=-\infty}^{\infty} |h[k]|$$

More general, an LTI system is said to be stable if the impulse response approaches zero as $t \rightarrow \infty$ or $n \rightarrow \infty$ for continuous-time or discrete-time system, respectively.

5. Commutative Property: The output of an LTI system with impulse response $h(t)$ or $h[n]$ to input $x(t)$ or $x[n]$ is equal to the output of the system with impulse response $x(t)$ or $x[n]$ to input $h(t)$ or $h[n]$, i.e.,

$$y(t) = x(t) * h(t) = h(t) * x(t)$$

$$\text{or} \quad y[n] = x[n] * h[n] = h[n] * x[n]$$

This leads to $y(t) = \int_{-\infty}^t x(\tau) h(t-\tau) d\tau = \int_{-\infty}^t x(t-\tau) h(\tau) d\tau$

$$\text{or} \quad y[n] = \sum_{k=-\infty}^{\infty} x[k] h[n-k] = \sum_{k=-\infty}^{\infty} x[n-k] h[k]$$

which may at times be easier to evaluate than equation.

6. Distributive Property: The output of an LTI system with impulse response $h_1(t) + h_2(t)$ or $h_1[n] + h_2[n]$ to input $x(t)$ or $x[n]$ is equal to the sum of the output of system with impulse response $h_1(t)$ or $h_1[n]$ to input $x(t)$ or $x[n]$ and system with impulse response $h_2(t)$ or $h_2[n]$ to input $x(t)$ or $x[n]$, i.e.,

$$y(t) = x(t) * [h_1(t) + h_2(t)] = x(t) * h_1(t) + x(t) * h_2(t)$$

$$\text{or} \quad y[n] = x[n] * [h_1[n] + h_2[n]] = x[n] * h_1[n] + x[n] * h_2[n]$$

The distributive property is useful when two or more systems are connected in parallel.

Also, as a consequence of both commutative and distributive properties, we have

$$y(t) = [x_1(t) + x_2(t)] * h(t) = x_1(t) * h(t) + x_2(t) * h(t)$$

$$\text{or} \quad y[n] = [x_1[n] + x_2[n]] * h[n] = x_1[n] * h[n] + x_2[n] * h[n]$$

Which simply state that the response of an LTI system to the sum of two inputs must equal the sum of the responses to these inputs individually.

7. Associative Property: The output of an LTI system with impulse response $[h_1(t) + h_2(t)]$ or $[h_1[n] + h_2[n]]$ to input $x(t)$ or $x[n]$ is equal to the output of the system with impulse response $h_2(t)$ or $h_2[n]$ to input $[x(t) * h_1(t)]$ or $x_1[n] * h_1[n]$, i.e.,

$$y(t) = x(t) * [h_1(t) * h_2(t)] = [x(t) * h_1(t)] * h_2(t)$$

$$\text{or} \quad y[n] = x[n] * [h_1[n] + h_2[n]] = [x[n] * h_1[n]] * h_2[n]$$

The associative property is useful when two or more systems are connected in series or in cascade.

Also, as a consequence of this property, we can say that the overall system response does not depend upon the order of the systems in the series or in cascade.

Q.2. (b) Find the Laplace Transform of the following functions: (4)

$$(i) e^{at} \sin(wt) \quad (ii) 10u(t-1) - 5\delta(t-2) - 5\delta(t-3).$$

Ans. Laplace Transform

(i) $e^{at} (\sin wt)$

$$\text{As we know the LT of } \sin wt = \frac{w}{s^2 + w^2}$$

Property

$$e^{at} \sin wt \xrightarrow{\text{LT}} \frac{w}{(s-a)^2 + w^2} \quad \begin{bmatrix} f(t) \xrightarrow{\text{LT}} F(s) \\ e^{at} f(t) \xrightarrow{\text{LT}} F(s-a) \end{bmatrix}$$

$$(ii) f(t) = 10u(t-1) - 5\delta(t-2) - 5\delta(t-3)$$

$$u(t-1) \xrightarrow{\text{LT}} \frac{e^{-s}}{s} \quad \text{Property}$$

$$\begin{bmatrix} f(t) \longrightarrow F(s) \\ f(t-a) \longrightarrow e^{-as} F(s) \end{bmatrix}$$

$$\delta(t-2) \xrightarrow{\text{LT}} e^{-2s}$$

$$\delta(t-3) \xrightarrow{\text{LT}} e^{-3s}$$

$$f(t) \xrightarrow{\text{LT}} 10 \frac{e^{-s}}{s} - e^{-2s} - 5e^{-3s}$$

Q.3. (a) Write the mathematical equation for the waveform shown in Fig. using Signal Synthesis Concept and find its Laplace Transformation. (4)


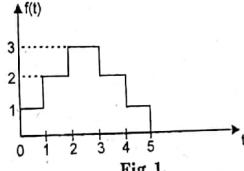


Fig. 1.

Ans.

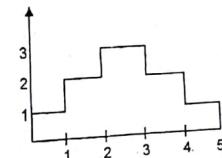

$$f(t) = u(t) + u(t-1) + u(t-2) - u(t-3) - u(t-4) - u(t-5)$$

$$f(t) \xrightarrow{\text{LT}} \frac{1}{s} + \frac{e^{-s}}{s} + \frac{e^{-2s}}{s} - \frac{e^{-3s}}{s} - \frac{e^{-4s}}{s} - \frac{e^{-5s}}{s}$$

As we know $u(t) \xrightarrow{\text{LT}} \frac{1}{s}$


$$f(t-a) \longrightarrow e^{-as} F(s)$$

6-2016


Third Semester, Circuits and Systems

So $u(t-\sigma) \rightarrow \frac{e^{-\sigma s}}{s}$

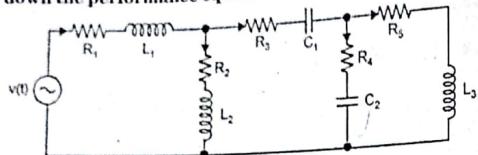Q.3. (b) Draw the s -domain equivalent circuit for the circuit shown in Fig. 2 and write down the performance equations using KVL. (6)



Ans.

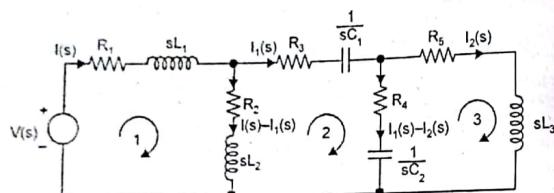

Applying KVL in loop 1, 2 and 3

$$\text{In loop 1: } V(s) = R_1 I + sL_1 I + (R_2 + sL_2)(I - I_1)$$

$$\text{In loop 2: } (R_2 + L_2 s)(I - I_1) = \left(R_3 + \frac{1}{sC_1} \right) I_1 + \left(R_4 + \frac{1}{sC_2} \right) (I_1 - I_2)$$

$$\text{In loop 3: } \left(R_4 + \frac{1}{sC_2} \right) (I_1 - I_2) = (R_5 + sL_3) I_2.$$

Q.4. (a) Obtain an expression for the current in the inductor for any time $t \geq 0$, in the circuit shown in Fig. 3 using Laplace Transformation. Assume the circuit to be initially relaxed. (5)


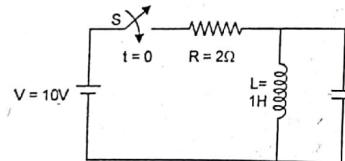


Fig. 3

Ans.

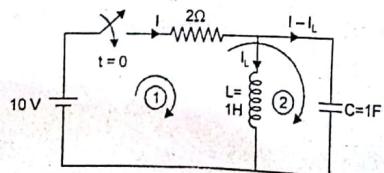

I.P. University-[B.Tech]-Akash Books
Applying KVL in loop 1 and 2

2016-7

$$\text{Taking LT: } 10 = 2I + \frac{dI_L}{dt} \quad \dots(1)$$

$$\frac{10}{s} = 2I(s) + sI_L(s)I_L(O^+) \quad \dots(1a)$$

$$\frac{10}{s} = 2I + \frac{1}{C} \int (I - I_L) dt \quad \dots(2)$$

$$\text{Taking LT: } \frac{10}{s} = 2I + \frac{I - I_L}{s} \quad \dots(2a)$$

$$\begin{aligned} \frac{10}{s} &= \left(2 + \frac{1}{s} \right) I - \frac{I_L}{s} \\ &= \left(sI_L + 2I = \frac{10}{s} \right) \times \left(2 + \frac{1}{s} \right) \\ &\quad \left(-\frac{I_L}{s} + \left(2 + \frac{1}{s} \right) I + \frac{10}{s} \right) \times 2 \end{aligned}$$

$$\left[\left(2 + \frac{1}{s} \right) s + \frac{2}{s} \right] I_L = \frac{20}{s} + \frac{10}{s^2} - \frac{20}{s}$$

$$\left(2s + 1 - \frac{2}{s} \right) I_L = \frac{10}{s^2}$$

$$I_L = \frac{10}{s(2s^2 + s + 2)}.$$

Q.4. (b) Determine the current $i(t)$ in the circuit shown in Fig. 4 using Laplace Transformation. (5)


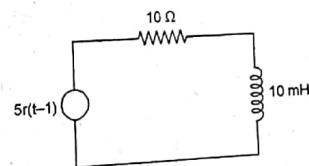


Fig. 4

Ans.

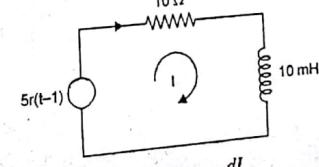

$$5r(t-1) = 10I + 10 \times 10^{-3} \frac{di}{dt}$$

8-2016

Third Semester, Circuits and Systems

Taking LT:

$$\frac{5e^{-s}}{s^2} = 10I(s) + 10^{-2}sI(s)$$

$$\Rightarrow I(s) = \frac{5e^{-s}}{s^2(10^{-2}s + 10)} = \frac{500e^{-s}}{s^2(s + 1000)}$$

Now ILT:

$$\frac{1}{s^2(s + 1000)} = \frac{A}{s} + \frac{B}{s^2} + \frac{C}{s + 1000}$$

$$B = \frac{1}{1000} \quad C = \frac{1}{10^6}$$

$$\frac{1}{s^2(s + 1000)} \xrightarrow{\text{LT}} Au(t) + Btu(t) + Ce^{-1000t}$$

Finally: $\frac{500e^{-s}}{s^2(s + 1000)} \xrightarrow{\text{LT}} 500Au(t-1) + 500B(t-1)u(t-1) + 500Ce^{-1000(t-1)}$

Put the value of A, B, C , we get I .

END TERM EXAMINATION [DEC. 2016] THIRD SEMESTER [B.TECH] CIRCUIT AND SYSTEM [ETEC-207]

Time : 3 Hrs.


M.M.: 75

Note: Attempt any five questions including Q. no. 1 which is compulsory. Select one question from each unit. Assume suitable missing data if any.


Q.1. (a) What is LTI system and describe their properties in brief.

Ans. Refer Q.2. (a) Mid Term Examination 2016. (5×5=25)

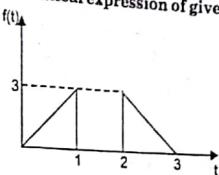Q.1. (b) Write the mathematical expression of given waveform.




Ans.

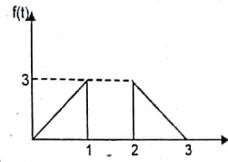

$$f(t) = 3[u(t) - u(t-1)] + (9-3t)[u(t-2) - u(t-3)]$$

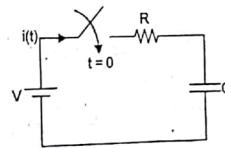Q.1. (c) Find the current $i(t)$ in the given network using Laplace technique.




Ans.

$$V = IR + \frac{1}{C} \int i dt$$

$$\frac{V}{s} = IR + \frac{1}{C} \left[\frac{I(s)}{s} - \frac{I'(0)}{s} \right]$$

$$\frac{V}{s} = IR + \frac{I}{Cs}$$
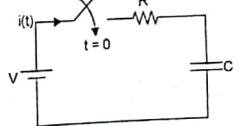
$$\Rightarrow I = \frac{V}{s \left(\frac{1}{Cs} + R \right)} = \frac{CV}{CRs + 1} = \frac{V}{R} \left(\frac{1}{s + \frac{1}{RC}} \right)$$



$$I(t) = \frac{V}{R} e^{-\frac{1}{RC}t}$$

Q.1. (d) Find T parameter in terms of g parameter.

Ans.

$$\begin{aligned} V_1 &= AV_2 + B(-I_2) \\ I_1 &= CV_2 + D(-I_2) \end{aligned}$$

...(1)

...(2)

$$V_2 = \frac{1}{A}V_1 + \frac{B}{A}I_2$$

$$g_{21} = \frac{1}{A} \text{ and } g_{22} = \frac{B}{A}$$


Putting the value of V_2 in equation (2)

$$I_1 = C\left[\frac{1}{A}V_1 + \frac{B}{A}I_2\right] + D(-I_2) = \frac{C}{A}V_1 + \left(\frac{BC}{A} - D\right)I_2$$

$$g_{11} = \frac{C}{A} \text{ and } g_{12} = \frac{B}{A}$$


UNIT-I

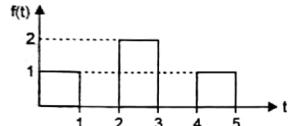Q.2. (a) Synthesis the given waveform using gate signal. (6)



$$\begin{aligned} \text{Ans. } f(t) &= [u(t) - u(t-1)] + 2[u(t-2) - u(t-3)] + [u(t-4) - u(t-5)] \\ &= g_{(0,1)}^{(t)} + 2g_{(2,3)}^{(t)} + g_{(4,5)}^{(t)} \end{aligned}$$

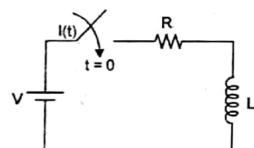Q.2. (b) Find the step transient response of series RL network using differential equation method. (6.5)




Ans.

$$\text{Applying KVL} \quad V = IR + L \frac{dI}{dt} \quad \frac{dI}{dt} + \frac{R}{L} I = \frac{V}{L}$$

$$\text{C.F.} \quad D + \frac{R}{L} = 0$$

$$I_{cf}(t) = Ae^{\frac{R}{L}t}$$

$$\text{PI} = \left. \frac{V}{D + \frac{R}{L}} \right|_{D=0} = \frac{V}{R}$$

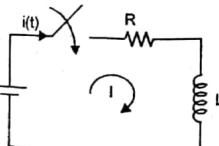

$$i(t) = Ae^{\frac{R}{L}t} + \frac{V}{R}$$

at

$$t = 0 \quad i = 0$$

$$A = -\frac{V}{R}$$

$$i(t) = \frac{V}{R} \left(1 - e^{\frac{R}{L}t} \right).$$

Q.3. (a) Define different type of test signals with their mathematical and graphical representation and Laplace.


Ans. Refer Q. 1(a) of Mid Term 2016.

Q.3. (b) Draw the waveform of given expression $f(t) = 2tu(t) - 2(t-1)u(t-1) - 2u(t-3)$. (6.5)

Ans. Refer Q. 1(b) of Mid Term 2016.

UNIT-II

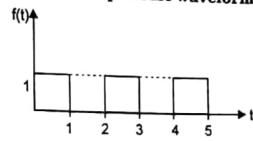Q.4. (a) Find the Laplace of given periodic waveform. (6)




Ans.

$$f(t) = [u(t) - u(t-1)] + [u(t-2) - u(t-3)] + [u(t-4) - u(t-5)] + \dots$$

$$\text{Taking LT: } F(s) = \frac{1}{s} - \frac{e^{-s}}{s} + \frac{e^{-2s}}{s} - \frac{e^{-3s}}{s} + \frac{e^{-4s}}{s} - \frac{e^{-5s}}{s} + \dots$$

$$= \frac{1}{s} [1 - e^{-s} + e^{-2s} - e^{-3s} + e^{-4s} - e^{-5s} + \dots]$$
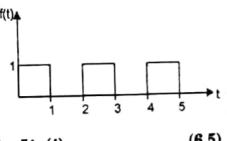
$$F(s) = \frac{1}{s} \times \frac{1}{1 + e^{-s}}.$$




Q.4. (b) Find the Laplace of given function $f(t) = 5tu(t)$. (6.5)

Ans. $f(t) = 5tu(t)$

$$\begin{aligned} &= 5 \int_0^\infty t e^{-st} dt = 5 \left[\frac{te^{-st}}{-s} - \frac{1}{-s} \int_0^\infty e^{-st} dt \right]_0^\infty = 5 \left[-\frac{e^{-st}}{s^2} \right]_0^\infty = \frac{5}{s^2} \end{aligned}$$

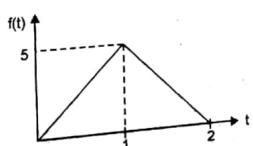Q.5. (a) Find the Laplace of given waveform.



12-2016


Ans.

$$\begin{aligned}
 f(t) &= 5[t(u(t) - u(t-1)) + (2-t)[u(t-1) - u(t-2)] \\
 f(t) &= 5[tu(t) - tu(t-1) + 2u(t-1) - 2u(t-2) - tu(t-1) + tu(t-2)] \\
 f(t) &= 5[tu(t) - 2tu(t-1) + 2u(t-1) + (t-2)u(t-2)] \\
 f(t) &= 5[r(t) - 2r(t-1) + r(t-2)]
 \end{aligned}$$

$$F(s) = 5 \left[\frac{1}{s^2} - \frac{2e^{-s}}{s^2} + \frac{e^{-2s}}{s^2} \right]$$

$$= \frac{5}{s^2} [1 - 2e^{-s} + e^{-2s}]$$

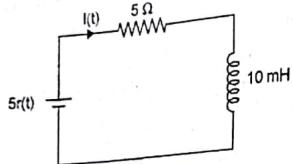Q.5. (b) Find the current in given network using laplace transform technique (6.5)



Ans.

$$5r(t) = 5I + 10^{-2} \frac{dI}{dt}$$

Taking LT: $\frac{5}{s^2} = 5I + 10^{-2}sI$

$$\Rightarrow I = \frac{5}{s^2(5 + 10^{-2}s)} = \frac{500}{(5 + 500)s^2}$$


$$I(s) = \frac{A}{s} + \frac{B}{s^2} + \frac{C}{s + 500}$$

$$B = 1 \quad C = \frac{1}{500} \quad A = \text{Find}$$

$$I(t) = Au(t) + tu(t) + \frac{1}{500} e^{-500t}$$

UNIT-II

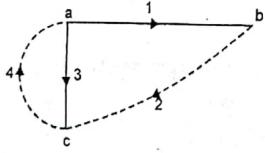Q.6. (a) Determine f-tie set matrix for given graph.



Ans.


$$B_f = 2 \begin{bmatrix} 1 & 2 & 3 & 4 \\ 1 & 1 & -1 & 0 \\ 4 & 0 & 0 & 1 \end{bmatrix} \rightarrow \text{for loop 1}$$

$$4 \begin{bmatrix} 0 & 1 & 1 & 1 \end{bmatrix} \rightarrow \text{for loop 2}$$


Third Semester, Circuits and Systems

I.P. University-[B.Tech]-Akash Books

2016-13

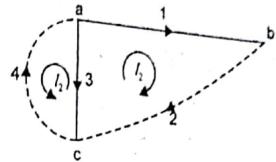

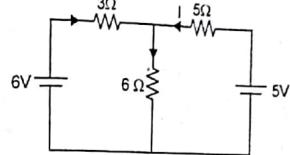Q.6. (b) Find the current in given network using super position theorem. (6.5)



Ans. 1st consider 6 V and replace 5 V with short circuit.


$$R_{eq} = (6 || 5) + 3$$

$$= 3 + \frac{6 \times 5}{6 + 5} = 3 + \frac{30}{11} = \frac{63}{11}$$

$$I = \frac{6}{63} = \frac{66}{63}$$

$$I_1 = \frac{5}{11} \times I$$
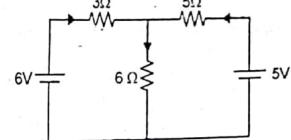
$$= \frac{5}{11} \times \frac{66}{63} = \frac{30}{63}$$




Consider 5 V and replace 6 V by short circuit

$$I = \frac{5}{7}$$


$$R_{th} = (6 || 3) + 5 = 5 + \frac{6 \times 3}{9} = 7$$

$$I'_1 = \frac{3}{9} \times \frac{5}{7} = \frac{15}{63}$$
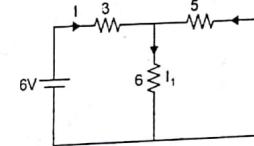
$$\text{Total } I = I_1 + I'_1 = \frac{30}{63} + \frac{15}{63} = \frac{45}{63}$$



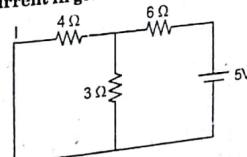Q.6. (b) Find the current in given network using Norton's theorem. (6)






Q.7. (a) Find the current in given network using Norton's theorem.

Ans.

$$\begin{aligned}\text{Total current} &= \frac{5}{(4+13)+6} \\ &= \frac{5}{12+6} \\ &= \frac{35}{54}\end{aligned}$$

$$\text{Current through } (AB) = \frac{3}{7} \times I$$

$$\begin{aligned}I_N &= \frac{3}{7} \times \frac{35}{54} = \frac{15}{54} \\ R_{th} &= 4 + (6+13) \\ &= 4 + \frac{18}{9} = 6.\end{aligned}$$

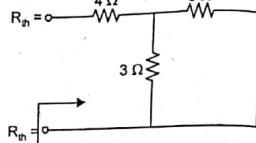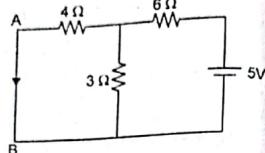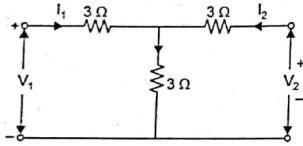**Q.7. (b) Find transmission parameter of given two port network. (6.5)****Ans.**

$$\begin{aligned}V_1 &= AV_2 + B(-I_2) \\ I_1 &= CV_2 + D(-I_2) \\ V_1 &= 6I_1 + 3I_2 \quad \dots(1) \\ V_2 &= 3I_1 + 6I_2 \quad \dots(2)\end{aligned}$$

From equation (2),

$$I_1 = \frac{V_2}{3} - 2I_2$$

Putting the value of I_1 in equation (1)

$$V_1 = 6\left(\frac{V_2}{3} - 2I_2\right) + 3I_2$$

$$V_1 = 2V_2 - 9I_2$$


On comparing, we get

$$A = 2, B = 9$$

$$V_2 = 3I_1 + 6I_2$$

$$I_1 = \frac{V_2}{3} - \frac{6I_2}{3}$$

$$I_1 = \frac{V_2}{3} - 2I_2$$

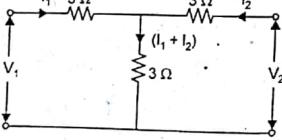

On comparing, we get

$$C = \frac{1}{3}, D = 2$$

Q.8. (a) Realize the function in Foster-1 and Foster-2 form. (12.5)

$$Z(s) = \frac{s(s+2)s(s+5)}{s(s+1)(s+4)}$$

$$\text{Ans. } Z(s) = \frac{s(s+2)s(s+5)}{s(s+1)(s+4)} = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$$

$$\begin{aligned}\text{Foster 1: } \frac{Z(s)}{s} &= \frac{(s+2)(s+5)}{(s+1)(s+4)} = \frac{s^2 + 7s + 10}{s^2 + 5s + 4} \\ &\quad s^2 + 5s + 4 \sqrt{s^2 + 7s + 10} (1) \\ &\quad \frac{s^2 + 5s + 4}{2s + 6}\end{aligned}$$


$$\frac{Z(s)}{s} = 1 + \frac{2s + 6}{(s+1)(s+4)}$$

Using partial fraction

$$\frac{Z(s)}{s} = 1 + \frac{A}{s+1} + \frac{B}{s+4}$$

$$A = \frac{4}{3}, B = \frac{2}{3}$$
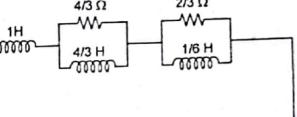
$$Z(s) = s + \frac{\frac{4}{3}s}{s+1} + \frac{\frac{2}{3}s}{s+4}$$




$$\text{Foster II: } Y(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

$$Y(s) = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+5}$$

$$A = \frac{2}{5}, B = \frac{1}{3}, C = \frac{4}{15}$$

$$Y(s) = \frac{\frac{2}{5}}{s} + \frac{\frac{1}{3}}{s+2} + \frac{\frac{4}{15}}{s+5}$$

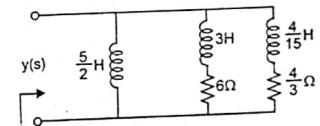**Q.9. Realize the function in Caur-1 and Caur-2 form. (12.5)**

$$Z(S) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$


$$\text{Ans. } Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

$$\text{Caur-1: } Y(s) = \frac{s^3 + 7s^2 + 10s}{s^2 + 5s + 4}$$

16-2016


Third Semester, Circuits and Systems

$$\begin{aligned}
 & s^2 + 5s + 4 \xrightarrow{s^3 + 7s^2 + 10s} (s \longleftrightarrow Y_1) \\
 & \frac{s^3 + 5s^2 + 4s}{2s^2 + 6s} s^2 + 5s + 4 \left(\frac{1}{2} \longleftrightarrow Z_2 \right) \\
 & \frac{s^2 + 3s}{2s + 4} \xrightarrow{s^2 + 6s} (s \longleftrightarrow Y_3) \\
 & \frac{2s^2 + 4s}{2s} 2s + 4 \left(1 \longleftrightarrow Z_4 \right) \\
 & \frac{2s}{+4} \xrightarrow{2s} \left(\frac{1}{2}s \longleftrightarrow Y_5 \right) \\
 & \underline{x}
 \end{aligned}$$

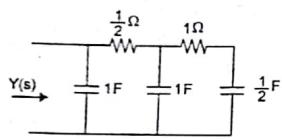

Caur-II: $Z(s) = \frac{s^2 + 5s + 4}{s^3 + 7s^2 + 10s} = \frac{4 + 5s + s^2}{10s + 7s^2 + s^3}$

$$\begin{aligned}
 & 10s + 7s^2 + s^3 \xrightarrow{4 + 5s + s^2} \left(\frac{4}{10s} \longleftrightarrow Z_1 \right) \\
 & 4 + \frac{14}{5}s + \frac{2}{5}s^2 \xrightarrow{10s + 7s^2 + s^3} \left(\frac{5}{11} \cdot 10 \longleftrightarrow Y_2 \right) \\
 & \frac{11}{5}s + \frac{3}{5}s^2 \xrightarrow{10s + \frac{30}{11}s^2} \left(\frac{11}{47}s^2 + s^3 \longleftrightarrow Z_3 \right) \\
 & \frac{20}{235}s^2 \xrightarrow{\frac{11}{47}s^2 + s^3} \left(\frac{235}{20} \times \frac{47}{11} \longleftrightarrow Y_4 \right) \\
 & \frac{47}{11}s^2 \xrightarrow{+s^3} \left(\frac{20}{235}s^2 \longleftrightarrow Z_5 \right) \\
 & \underline{x}
 \end{aligned}$$

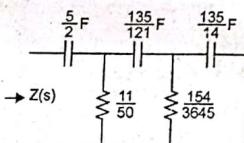

FIRST TERM EXAMINATION [SEPT. 2017]
THIRD SEMESTER [B.TECH]
CIRCUITS AND SYSTEMS
[ETEE-207]



time : 1½ hrs.

M.M.: 30

Note: Attempt any three questions including Q.No 1 which is compulsory.

Q.1. Attempt all of the following:

Q.1. (a) Draw the waveform of

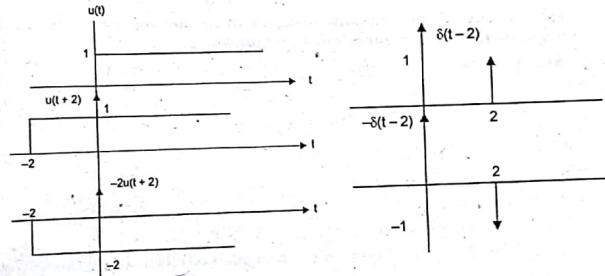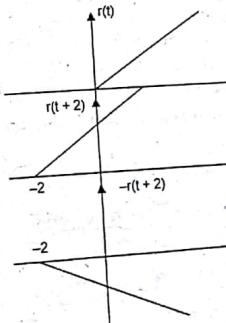(i) $-2u(t+2)$ (ii) $\delta(t-2)$ (iii) $-r(t+2)$ Ans. (i) $u(t)$ (ii) $\delta(t-2)$ (iii) $-r(t+2)$ 

2-2017

Third Semester, Circuits and Systems

Q.1. (b) Write the equation for the waveform shown in the figure 1 using shifted step function. (2)

Ans.

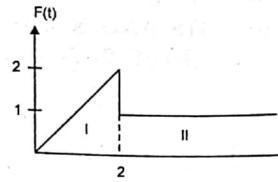


Fig. 1

Section I $t[u(t) - u(t-2)]$ Section II $u(t-2)$

$$F(t) = t(u(t) - u(t-2)) + u(t-2)$$

Q.1. (c) Prove that the impulse response of any network is inverse Laplace transform of the transfer function of that network. (2)

Ans. As we know the transfer function is the ratio of $Y(S)$ and $X(S)$

$$T(S) = H(S) = \frac{Y(S)}{X(S)}$$

Where $Y(S)$ is the LT of $y(t)$ i.e. outputand $X(S)$ is the LT of $x(t)$ i.e., inputif input is $x(t) = \delta(t)$ then $X(s) = 1$ On putting this value in eqn 1 we get $H(S) = Y(S)$ On taking ILT $h(t) = y(t)$ that means if the input is $\delta(t)$ then $h(t) = y(t)$.and Impulse response of a system is the response if input is $\delta(t)$.**Q.1. (d)** What are the advantages of Laplace Transform techniques. (2)

Ans. Advantage of LT

1. It gives complete solution
2. Initial conditions are automatically considered in the transformed equation
3. Easy to solve differential equation using LT
4. It gives systematic solution of differential eqn.

Q.1. (e) Find even and odd component of the signal $x(t) = e^{-2t} \cos 2t$. (2)Ans. $x(t) = e^{-2t} \cos 2t$

$$x(-t) = e^{+2t} \cos(-2t) = e^{+2t} \cos 2t$$

$$x_{\text{even}}(t) = \frac{e^{-2t} \cos 2t + e^{+2t} \cos 2t}{2}$$


$$x_{\text{odd}}(t) = \frac{e^{-2t} \cos 2t - e^{+2t} \cos 2t}{2}$$

I.P. University-[B.Tech.]-Akash Books

2017-3

Q.2. (a) Find out the response $i(t)$ for $t > 0$ for the series R-C circuit excited by a pulse excitation of 10 magnitudes voltage for one second duration. Explain $i(t)$ with graph. Assuming initial conditions zero. $R = 1\Omega$, $C = 1F$. (5)

Ans.

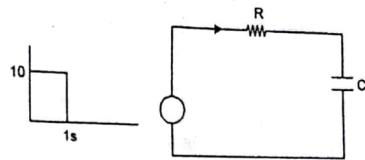

$$V = iR + \frac{1}{C} \int i dt$$

$$10[u(t) - u(t-1)] = iR + \frac{1}{C} \int i dt$$

taking LT

$$\frac{10}{s} - \frac{10}{s} e^{-s} = I(s)R + \frac{1}{C} \frac{I(s)}{s}$$

$$R = 1\Omega \quad C = 1F$$

$$\frac{10}{s} - \frac{10}{s} e^{-s} = I(s) \left(1 + \frac{1}{s}\right) = I(s) \left(\frac{s+1}{s}\right)$$

$$I(s) = \frac{10(1 - e^{-s})}{(1+s)} = \frac{10}{s+1} - \frac{10e^{-s}}{s+1}$$

taking ILT

$$i(t) = 10e^{-t} - 10e^{-(t-1)}$$

$$= 10e^{-t}(1-e)$$

Q.2. (b) Given $F(s) = \frac{s+1}{(s+2)(s+3)}$. Find Initial value and Final Value of the function. (5)

Ans. Initial Value Theorem $\lim_{s \rightarrow \infty} sF(s)$

$$= \frac{s(s+1)}{(s+2)(s+3)}$$

$$= \lim_{s \rightarrow \infty} \frac{\cancel{s} \left(1 + \frac{1}{s}\right)}{\cancel{s} \left(1 + \frac{2}{s}\right) \left(1 + \frac{3}{s}\right)} = \frac{1}{1 \times 1} = 1$$

Final Value Theorem $= \lim_{s \rightarrow 0} sF(s)$

$$= \lim_{s \rightarrow 0} \frac{s(s+1)}{(s+2)(s+3)} = 0$$

Q.3. (a) Calculate Laplace Transform of periodic function as shown in figure 2. (5)


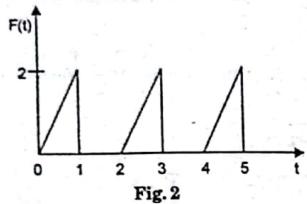


Fig. 2

Ans.

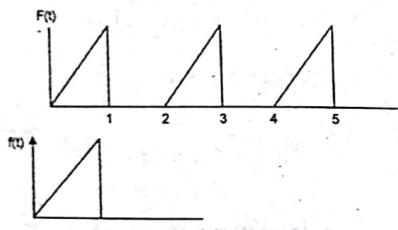

$$f(t) = t[u(t) - u(t-1)] = t u(t) - t u(t-1)$$

taking LT

$$\begin{aligned} F(s) &= \frac{1}{s^2} - LT[(t-1)u(t-1)] - LT[u(t-1)] \\ &= \frac{1}{s^2} - \frac{e^{-s}}{s^2} - \frac{e^{-s}}{s} \\ LT \text{ of } F(t) &= \frac{1}{1-e^{-2s}} \left(\frac{1}{s^2} - \frac{e^{-s}}{s^2} - \frac{e^{-s}}{s} \right) \end{aligned}$$

Q.3. (b) In the circuit of figure 3 switch S_1 is closed at $t = 0$ and switch S_2 is open at $t = 0.2$ second. Find the expression for the transient current for two intervals. (5)


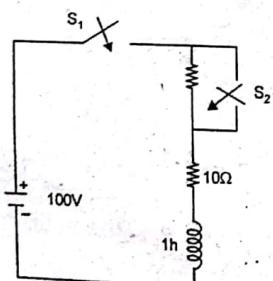


Fig. 3

Ans.

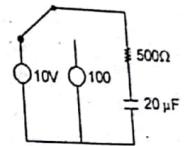

$$100 = 20i + L \frac{di}{dt}$$

$$100 = 20i + \frac{di}{dt}$$

$$Cf = Ae^{-\alpha t}$$

$$PI = \frac{100}{D+20} = \frac{100}{20} = 5$$

$$i(t) = Ae^{-2t} + 5$$

at $t = 0$ $i = 0$ because inductor work as open chkt

$$A = -5$$

$$i(t) = 5(1 - e^{-2t})$$

$$t = .2s \text{ at } i = 5(1 - e^{-2 \times 0.2}) = 5(1 - e^{-0.4})$$

When S_2 is open

$$100 = 10i + L \frac{di}{dt}$$

$$CF = Be^{-\alpha t}$$

$$PI = \frac{100}{D+10} = 10$$


$$i(t) = Be^{-10t} + 10$$

$$t = 0, i = 5(1 - e^{-4})$$

$$5(1 - e^{-4}) = B + 10 \Rightarrow B = -10 + 5 - 5e^{-4}$$

$$= -4.9$$

$$i(t) = -4.9e^{-10t} + 10$$

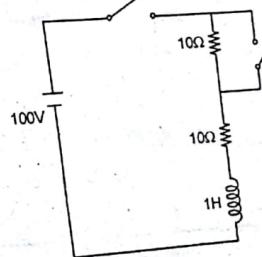

When both switch is on 1st 10Ω is bypassed

So KVL eqn is

$$100 = 10i + \frac{di}{dt}$$

$$CF = Ae^{-10t}$$

$$PI = \frac{100}{10} = 10$$

$$i(t) = Ae^{-10t} + 10$$

at $t = 0; i = 0$

$$0 = Ae^{-10 \times 0} + 10 \Rightarrow A = -10$$

$$i(t) = 10(1 - e^{-10t})$$

at $t = .2S$

$$i = 10(1 - e^{-10 \times .2})$$

$$= 10(1 - e^{-2})$$

$$= 8.64$$

When S_1 is off

then Applying on KVL on loop we get

$$100 = 20i + \frac{di}{dt}$$

$$CF = Be^{-20t}$$

$$PI = \frac{100}{20} = 5$$

$$i(t) = 5 + Be^{-20t}$$

$$t = 0.05 \quad i(t) = 8.64$$

$$8.64 = 5 + Be^0 \Rightarrow B = 8.64 - 5 = 3.64$$

$$i(t) = 5 + 3.64e^{-20t}$$

$$t = 0.05 \quad i(t) = 8.64 - 5 = 3.64$$

$$i(t) = 5 + 3.64e^{-20t}$$

Q.4. (a) Find the time at which D.C. Source deliver a current of 500 Amp in below circuit as shown in figure 4 after closing the switch K at $t = 0$ sec. (5)

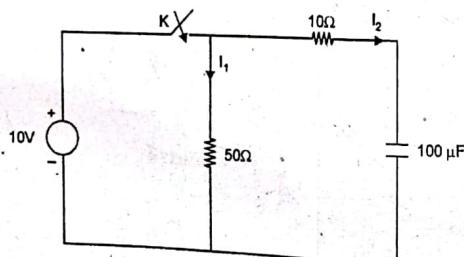


Fig. 4

Ans.

$$I = I_1 + I_2$$

$$I_1 = \frac{10}{50} = .2A = 200 \text{ mA}$$

$$I = 500 \text{ mA}$$

$$\Rightarrow 500 = 200 + I_2$$

$$I_2 = 300 \text{ mA}$$

$$I_2 = \frac{V}{R} e^{-t/T}$$

$$0.3 = \frac{10}{70} e^{-\frac{t}{RC}} = \frac{10}{70} e^{-\frac{t}{.007}}$$

$$-\frac{t}{0.007} = \log_e(2.1) = t = 5.2 \text{ ms.}$$

Q.4. (b) In the circuit of figure 5 the switch S is closed on position 1 in $t \approx 0$ and after one time constant is moved to position 2. Find the current before and after moving to position 2. Assuming all initial conditions are zero. (5)

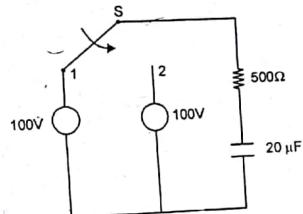


Fig. 5

Ans. Applying KVL $100 = 500i + \frac{1}{20\mu F} \int i dt$

On differentiating above eqn

$$0 = 500 \frac{di}{dt} + \frac{1}{20 \times 10^{-6}} i$$

$$\frac{di}{dt} + 100i = 0$$

$$i(t) = Ke^{-100t}$$

$$\text{at } t = 0 \quad i = \frac{100}{500} = .2A$$

$$K = .2$$

$$i(t) = 0.2e^{-100t}$$

$$\text{time constant } T = RC = 500 \times 20 \times 10^{-6}$$

$$= 10^{-2}$$

$$i(t) = 2e^{-100t} \times 10^{-2} = \frac{2}{e} = .074 A$$

$$V_C = 100(1 - e^{-1}) = 63.7 V$$

When switch move to position 2

$$100 = 500i + \frac{1}{20 \times 10^{-6}} \int i dt$$

On differentiating we get

$$\frac{di}{dt} + 100i = 0$$

$$i(t) = Ke^{-100t}$$

$$V = \frac{1}{C} \int i dt = \frac{1}{20 \times 10^{-6}} \int Ke^{-100t} dt$$

$$= -\frac{K}{20 \times 10^{-6} \times 100} e^{-100t}$$

$$V_C = -500Ke^{-100t}$$

$$t = 0 \quad V_C = 63.7 V$$

$$63.7 = 500Ke^0 \Rightarrow K = -\frac{63.7}{500}$$

$$i(t) = -\frac{63.7}{500} e^{-100t}$$

at

END TERM EXAMINATION [DEC. 2017] THIRD SEMESTER [B.TECH] CIRCUITS AND SYSTEMS [ETEE-207]

Time : 3 hrs.

M.M. : 75

Note: Attempt any five questions including Q.No. 1 which is compulsory.

Q.1. (a) What are even and odd signals? Give examples. (2)

Ans. If $x(-t) = x(t)$ then signal is even
 $x(-t) = -x(t)$ then signal is odd

Q.1. (b) What are energy and power signal? Discuss. (2)

Ans. A signal is power signal if Average power of a system is finite and energy is infinite.

A signal is energy signal if total energy of the signal is finite and power is zero.

Q.1. (c) What is the relation between unit step function and ramp function? (4)

Ans. $r(t) = t[u(t)]$

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases} \rightarrow r(t)$$

Q.1. (d) Give the classification of filters. (4)

Ans. Classification of filter:

1. Low pass filter
2. High pass filter
3. Band pass filter
4. Band stop filter

Q.1. (e) What are the characteristics of Hurwitz polynomial? Discuss. (4)

Ans. 1. The coefficients of the s terms must be +ve.
 2. Both odd and even part of the polynomial have roots on the imaginary axis.
 3. The continued fraction expansion of the ratio of even to odd parts of hurwitz polynomial gives all +ve quotient terms.

4. If $P(s)$ is a Hurwitz polynomial and $W(S)$ is a even multiplicative factor the $P_1(s) = W(S)P(S)$ is also a Hurwitz polynomial. (4)

Q.1. (f) Define tree, twigs, links and loop. (5)

Ans. Tree: It is an inter connected open set of branches which include all the nodes of the given graph. In a Tree of the graph there cannot be any closed loop.

Twig: The branch involved in tree is known as Twig.

Link: It is that branch of graph that does not belongs to the particular tree.

Loop: This is closed contour selected in a graph.

Q.1. (g) Write a short note on h-parameters. (5)

Ans. $V_1 = h_{11}I_1 + h_{12}V_2$
 $I_2 = h_{21}I_1 + h_{22}V_2$

$$h_{11} = \left. \frac{V_1}{V_2} \right|_{V_2=0}, \quad h_{21} = \left. \frac{V_2}{V_1} \right|_{V_1=0}, \quad h_{12} = \left. \frac{I_1}{V_2} \right|_{I_1=0}, \quad h_{22} = \left. \frac{I_2}{V_1} \right|_{I_1=0}$$

Q.2. (a) Determine whether the system described by the differential equation $\frac{dy(t)}{dt} + y(t) + 4 = x(t)$ is linear. (6)

Ans. $\frac{dy(t)}{dt} + y(t) + 4 = x(t)$

Let a input $x_1(t)$ and corresponding output is $y_1(t)$.

$$\frac{dy_1(t)}{dt} + y_1(t) + 4 = x_1(t)$$

Similarly Input $x_2(t)$ and output $y_2(t)$.

$$\frac{dy_2(t)}{dt} + y_2(t) + 4 = x_2(t)$$

Linear combination of them

$$a \frac{dy_1(t)}{dt} + ay_1(t) + 4a + b \frac{dy_2(t)}{dt} + by_2(t) + 4b \\ = ax_1(t) + bx_2(t)$$

$\frac{d}{dt} [ay_1(t) + by_2(t)] + [ay_1(t) + by_2(t)] + 4[a + b] = ax_1(t) + bx_2(t)$ is not in the linear combination

So system is non linear.

Q.2. (b) A Cosine wave $\cos \omega t$ is applied as input to the series RL circuit as shown in fig-1. Find the resultant current $I(t)$ if the switch "S" is closed at $t = 0$. (6.5)

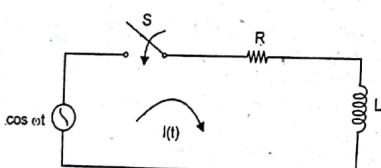


Fig. 1

Ans. $\cos \omega t = IR + L \frac{dI}{dt}$

$$\frac{1}{L} \cos \omega t = \frac{R}{L} I + \frac{dI}{dt}$$

$$D + \frac{R}{L} = 0 \Rightarrow D = -\frac{R}{L}$$

$$CF = e^{-Rt/L}$$

$$PI = \frac{1}{L} \left(\frac{\cos \omega t}{D + \frac{R}{L}} \right) \left(\frac{(D - R/L)}{D - \frac{R}{L}} \right)$$

$$= \frac{1}{L} \frac{D \cos \omega t - \frac{R}{L} \cos \omega t}{D^2 - \left(\frac{R}{L} \right)^2}$$

$$= \frac{1}{L} \times \frac{1}{-\omega^2 - \left(\frac{R}{L} \right)^2} \left[-\omega \sin \omega t + \frac{R}{L} \cos \omega t \right]$$

$$i(t) = Ae^{-\frac{R}{L}t} - \frac{1}{L \left(\omega^2 + \frac{R^2}{L^2} \right)} \left[-\omega \sin \omega t + \frac{R}{L} \cos \omega t \right]$$

Initially inductor work as open circuit. So at $t = 0$ $i = 0$

$$0 = A - \frac{R}{L} \frac{1}{L \left(\omega^2 + \frac{R^2}{L^2} \right)} \Rightarrow A = \frac{R}{L^2 \omega^2 + R^2} = 0$$

$$A = \frac{R}{L^2 \omega^2 + R^2}$$

Q.3. (a) A system has a transfer function given by $H(s) = \frac{1}{(s+1)(s^2+s+1)}$. Find the response of the system when the excitation is $x(t) = (1 + e^{-3t} - e^{-t})u(t)$. (6.5)

Ans. $x(t) = (1 + e^{-3t} - e^{-t})u(t)$

taking LT

$$X(s) = \frac{1}{s} + \frac{1}{s+3} - \frac{1}{s+1} = \frac{s^2 + 4s + 3 + s^2 + s - s^2 - 3s}{s(s+3)(s+1)} \\ = \frac{s^2 + 2s + 3}{s(s+3)(s+1)}$$

$$Y(s) = \frac{1}{(s+1)(s^2+s+1)} \times \frac{s^2 + 2s + 3}{s(s+3)(s+1)}$$

$$Y(s) = \frac{s^2 + 2s + 3}{s(s+1)^2(s+3)(s^2+s+1)}$$

Using partial fraction we can write it

$$\frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+1} + \frac{D}{(s+1)^2} + \frac{Ps}{s^2+s+1}$$

$$A = \frac{s^2 + 2s + 3}{s(s+1)^2(s+3)(s^2+s+1)} \times \left. s \right|_{s=0} = \frac{3}{3} = 1$$

$$B = \frac{s^2 + 2s + 3}{s(s+1)^2(s+3)(s^2+s+1)} \times \left. s+3 \right|_{s=-3} = \frac{9 - 6 + 3}{-3 \times 4 \times (9 - 3 + 1)} = \frac{6}{-12 \times 7} = -\frac{1}{14}$$

$$D = \frac{s^2 + 2s + 3}{s(s+1)^2(s+3)(s^2+s+1)} \times \left. (s+1)^2 \right|_{s=-1} = \frac{2}{-1 \times 2 \times 1} = -1$$

C and also find P

$$\begin{aligned} & \frac{Ps}{s^2+s+1} \\ &= P \frac{s}{s^2 + 2 \frac{1}{2}s + \left(\frac{1}{2}\right)^2 + \frac{5}{4}} \\ &= \frac{P \left(s + \frac{1}{2}\right)}{\left(s + \frac{1}{2}\right)^2 + \frac{5}{4}} - P \frac{e^{\frac{1}{2}t}}{\left(s + \frac{1}{2}\right)^2 + \frac{5}{4}} \\ &= P \left[e^{-\frac{1}{2}t} \cos \frac{\sqrt{5}}{2}t - \frac{1}{2} e^{-\frac{1}{2}t} \sin \frac{\sqrt{5}}{2}t \right] \end{aligned}$$

$$\frac{1}{s} + -\frac{1}{14(s+3)} + \frac{-1}{(s+1)^2} + \frac{C}{s+1} + \frac{Ps}{s^2+s+1}$$

$$u(t) = \frac{1}{14} e^{-3t} - t e^{-t} + c e^{-t} + P \left[e^{-\frac{1}{2}t} \cos \frac{\sqrt{5}}{2}t - \frac{1}{2} e^{-\frac{1}{2}t} \sin \frac{\sqrt{5}}{2}t \right]$$

Q.3. (b) Determine the frequency response, magnitude response, and phase response and time delay of the system given by $y(n) + \frac{1}{2}y(n-1) = x(n) - x(n-1)$. (6)

$$\text{Ans. } Y(n) + \frac{1}{2}y(n-1) = x[n] - x[n-1]$$

Taking FT

$$Y(jw) + \frac{1}{2}(jw)Y(jw) = X(jw) - jwX(jw)$$

$$H(jw) = \frac{Y(jw)}{X(jw)} = \frac{1-jw}{1+\frac{1}{2}jw}$$

$$= \frac{2(1-jw) \times (2-jw)}{(2+jw) \times (2-jw)}$$

$$= \frac{2\{2-3jw-w^2\}}{4+w^2} = \frac{2(2-w^2)}{4+w^2} - \frac{6jw}{4+w^2}$$

$$|H(jw)| = \sqrt{\left(\frac{2(2-w^2)}{4+w^2}\right)^2 + \left(\frac{6jw}{4+w^2}\right)^2} = \frac{1}{(4+w^2)} \sqrt{4(4+w^4-4w^2)+36j^2w^2}$$

$$= \frac{1}{4+w^2} \sqrt{16+4w^4-16w^2-36w^2} = \frac{4}{4+w^2} \sqrt{4+w^4-13w^2}$$

$$\angle H(jw) = \tan^{-1} \frac{-6w}{2(2-w^2)} = \tan^{-1} \left(\frac{-3w}{2-w^2} \right)$$

Q.4. (a) A sine wave $\sin \omega t$ is applied as the input to the series RC circuit shown in fig.2. Find the resultant current $i(t)$ if switch S is closed at $t=0$. (6.5)

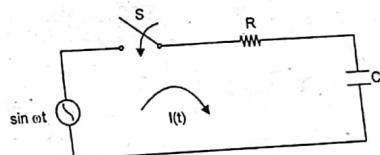


Fig.2

Ans.

$$IR + \frac{1}{C} \int i dt = \sin \omega t$$

$$R \frac{di}{dt} + \frac{i}{C} = \omega \cos \omega t$$

$$\frac{di}{dt} + \frac{i}{RC} = \frac{\omega}{R} \cos \omega t$$

$$D + \frac{1}{RC} = 0 \Rightarrow D = -\frac{1}{RC}$$

$$CF = A e^{-\frac{1}{RC}t}$$

$$PI = \frac{\frac{\omega \cos \omega t}{R} \left(D - \frac{1}{RC} \right)}{\left(D + \frac{1}{RC} \right) \left(D - \frac{1}{RC} \right)} = \frac{\frac{\omega}{R} \left[D(\cos \omega t) - \frac{1}{C} \cos \omega t \right]}{D^2 - \left(\frac{1}{RC} \right)^2}$$

$$= \frac{\frac{\omega}{R} \left[-\omega \sin \omega t - \frac{1}{RC} \cos \omega t \right]}{-\omega^2 - \left(\frac{1}{RC} \right)^2}$$

$$= \frac{\left(\frac{\omega^2}{R} \sin \omega t + \frac{\omega^2}{R^2 C} \cos \omega t \right)}{\omega^2 + \left(\frac{1}{RC} \right)^2}$$

$$i(t) = A e^{-\frac{1}{RC}t} + \frac{\omega}{R \left[\omega^2 + \left(\frac{1}{RC} \right)^2 \right]} \times \left[\omega \sin \omega t + \frac{1}{RC} \cos \omega t \right]$$

Q. 4. (b) Find the laplace transform of the triangular pulse shown. (6)

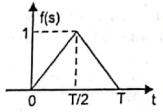


Fig. 3

$$\text{Ans. } f(t) = \frac{2}{T} t \left[u(t) - u\left(t - \frac{T}{2}\right) \right] + 2 \left(1 - \frac{t}{T} \right) \left[u\left(t - \frac{T}{2}\right) - u(t - T) \right]$$

$$= \frac{2}{T} \left[t u(t) - t u\left(t - \frac{T}{2}\right) \right] + \frac{2}{T} (T-t) \left[4 \left(t - \frac{T}{2} \right) - u(t-T) \right]$$

$$t u(t) \rightarrow \frac{1}{s^2}$$

$$t u\left(t - \frac{T}{2}\right) = \left(t - \frac{T}{2} \right) u\left(t - \frac{T}{2}\right) + \frac{T}{2} u(t-T/2)$$

$$\xrightarrow{LT} \frac{e^{-\frac{T}{2}s}}{s^2} + \frac{T}{2} \frac{e^{-Ts}}{s}$$

$$(t-T) u(t-T) \rightarrow \frac{e^{-Ts}}{s^2}$$

$$(t-T) u(t-\frac{T}{2})$$

$$\left(t - \frac{T}{2} \right) u\left(t - \frac{T}{2}\right) - \frac{T}{2} u\left(t - \frac{T}{2}\right)$$

$$\Rightarrow \frac{e^{-T/2s}}{s^2} - \frac{T}{2} \frac{e^{-1/2s}}{s}$$

$$f(t) \xrightarrow{LT} \frac{2}{T} \left[\frac{1}{s^2} - \frac{e^{-T/2}}{s^2} - \frac{T}{2} \frac{e^{-sT/2}}{s} \right]$$

$$= \frac{2}{T} \left[\frac{e^{-T/2}}{s} - \frac{T}{2} \frac{e^{-T/2}}{s} - \frac{e^{-sT}}{s^2} \right]$$

Q.5.(a) Consider R-L circuit with $R = 4\Omega$ $L = 1H$ excited by 20 V dc source as shown in fig 4. Assume the initial value of current in inductor is 2A. Using Laplace Transform determine the current $I(t)$. Also draw the s-domain representation of the circuit.

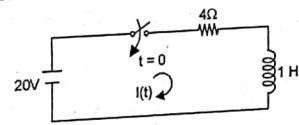


Fig. 4

Ans. Applying KVL in loop

$$I \times 4 + 1 \frac{dI}{dt} = 20$$

taking LT we get

$$4I(s) + sI(s) - i(0^+) = \frac{20}{s}$$

$$4I(s) + sI(s) = \frac{20}{s} + i(0^+)$$

$$I(s)(4+s) = \frac{20}{s} + 2 = \frac{20+2s}{20}$$

$$I(s) = \frac{s+10}{10(s+4)} = \frac{1}{10} \frac{s+4+6}{s+4} \text{ given } i(0) = 2A$$

$$= \frac{1}{10} \left[1 + \frac{6}{s+4} \right]$$

taking ILT

$$L(t) = \frac{1}{10} \delta(t) + \frac{6}{10} e^{-4t}$$

Q. 5. (b) State and explain the laplace transform and its inverse transform. (6)

Ans. LT is a mathematical tool which transform a time domain signal into frequency (s) domain signal.

$$X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$$

Inverse LT is just inverse process of laplace transform

$$x(t) = \frac{1}{2\pi} \int X(s) e^{+st} ds$$

To represent the laplace and inverse transform we use following notation

$$x(t) \rightarrow X(s)$$


$$L[x(t)] = X(s)$$

and


$$L^{-1}[X(s)] = x(t)$$

Where $X(s)$ is Laplace transform of $x(t)$ and $x(t)$ is inverse laplace transform of $X(s)$.

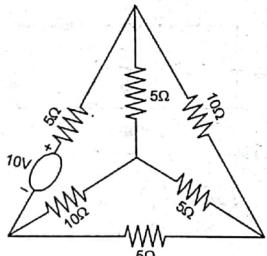Q.6. (a) For the network shown write the tieset matrix and determine the loop current and branch currents. (6.5)




Ans.

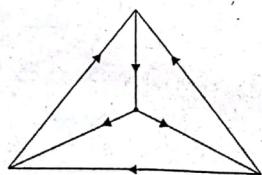

Oriented graph of the given circuit.

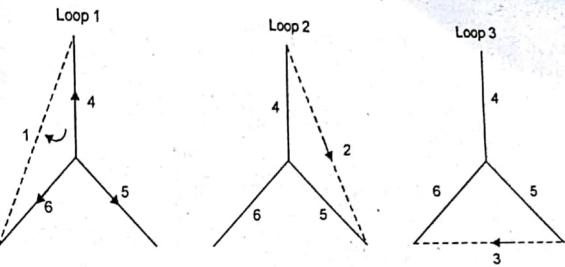We select tree (4, 5, 6) and link (1, 2, 3)



$$B_f = \begin{vmatrix} 4 & 5 & 6 & 1 & 2 & 3 \\ 1 & -1 & 0 & 1 & 1 & 0 \\ 2 & 1 & -1 & 0 & 0 & 1 \\ 3 & 0 & 1 & -1 & 0 & 0 \end{vmatrix}$$

$$Z_b = \begin{vmatrix} 5 & 0 & 0 & 0 & 0 & 0 \\ 0 & 10 & 0 & 0 & 0 & 0 \\ 0 & 0 & 5 & 0 & 0 & 0 \\ 0 & 0 & 0 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0 & 5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 10 \end{vmatrix}$$

$$Z_i = B_f Z_b B_f^T \quad \& \quad V_i = Z_i T_i$$

$$I_b = [B_f]^T I_i - I_s$$

$$B_f Z_b = \begin{bmatrix} -5 & 0 & 5 & 5 & 0 & 0 \\ 5 & -10 & 0 & 0 & 5 & 0 \\ 0 & 10 & -5 & 0 & 0 & 10 \end{bmatrix}$$

$$B_f Z_b B_f^T = \begin{bmatrix} -5 & 0 & 5 & 5 & 0 & 0 \\ 5 & -10 & 0 & 0 & 5 & 0 \\ 0 & 10 & -5 & 0 & 0 & 10 \end{bmatrix} \begin{bmatrix} -1 & 1 & 0 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

Q.6. (b) Find the transmission parameter in terms of y and z parameters. (6)

Ans.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 = \frac{1}{Z_{21}} V_2 + \frac{Z_{22}}{Z_{21}} (-I_2)$$

$$C = \frac{1}{Z_{21}} \text{ and } D = \frac{Z_{22}}{Z_{21}}$$

$$\begin{aligned} V_1 &= Z_{11} \left[\frac{1}{Z_{21}} V_2 + \frac{Z_{22}}{Z_{21}} \right] (-I_2) + Z_{12} I_2 \\ &= \frac{(Z_{11})}{Z_{21}} V_2 + \left(\frac{Z_{11} Z_{22}}{Z_{21}} - Z_{12} \right) (-I_2) \end{aligned}$$


$$A = \begin{pmatrix} Z_{11} \\ Z_{21} \end{pmatrix}, B = \frac{\Delta Z}{Z_{21}}$$

$$\text{Similarly } A = -\frac{Y_{22}}{Y_{21}}, B = -\frac{1}{Y_{21}}$$


$$C = -\frac{\Delta Y}{Y_{21}}, D = -\frac{Y_{11}}{Y_{21}}$$

Q.7. (a) Determine z parameter of the networks shown.

(6.5)

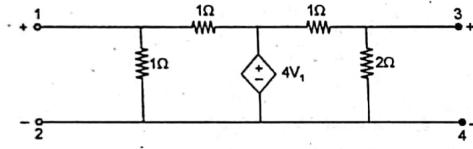

Ans.

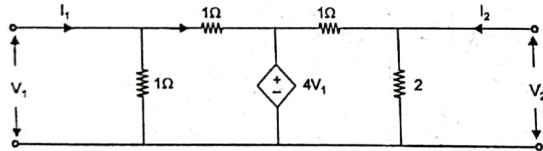

$$I_1 = \frac{V_1}{1} + \frac{V_1 - 4V_1}{1}$$

$$I_2 = \frac{V_2}{2} + \frac{V_2 - 4V_1}{1}$$

$$I_1 = -2V_1 \Rightarrow V_1 = -\frac{I_1}{2}$$

$$I_2 = -4V_1 + \frac{3V_2}{2}$$

Putting the value of V_1 in above equation

$$\frac{3}{2}V_2 = I_2 - \frac{4I_1}{2}$$

$$V_2 = -\frac{2}{3} \times \frac{4}{2} I_1 + \frac{2}{3} I_2$$

$$V_2 = -\frac{4}{3} I_1 + \frac{2}{3} I_2$$

$$Z_{11} = -\frac{1}{2}, Z_{12} = 0$$

$$Z_{21} = \frac{-4}{3}, Z_{22} = \frac{2}{3}$$

Q.7. (b) Discuss the necessary conditions for transfer functions. (6)

Ans.

1. The coefficients in the polynomials $N(s)$ and $D(s)$ of $T = N/D$ must be real and those for $D(s)$ must be positive.

2. Poles and zeroes must be conjugate if imaginary or complex.

3. The real part of poles must be negative or zero, if the real part is zero, then that pole must be simple. This includes the origin.

4. The polynomial $D(s)$ may not have any missing term between that of highest and lowest degrees, unless all even or all odd terms are missing.

5. The polynomial $N(s)$ may have terms missing, and some of the coefficients may be negative.

6. The degree of $N(s)$ may be as small as zero independent of the degree of $D(s)$.

7. (a) for G and a : The maximum degree of $N(s)$ is equal to the degree of $D(s)$. (b) For Z and Y : The maximum degree of $N(s)$ is equal to the degree of $D(s)$ plus one.

Q.8. (a) Using the foster I Form synthesize the impedance function. (6.5)

$$z(s) = \frac{8(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$$

$$Z(s) = \frac{8(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$$

$$\frac{A_0}{s} + \frac{2A_1 s}{s^2 + 2} + \frac{2A_2 s}{s^2 + 4}$$

$$A_0 = \frac{8(s^2 + 1)(s^2 + 3)}{(s^2 + 2)(s^2 + 4)} \Big|_{s=0} = 3$$

$$A_1 = \frac{8(s^2 + 1)(s^2 + 3)}{(s^2 - j\sqrt{2})(s^2 + 4)} \Big|_{s=-j\sqrt{2}} = 1$$

$$A_2 = \frac{8(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s - j\sqrt{2})} \Big|_{s=j\sqrt{2}}$$

$$\frac{3}{5} + \frac{2s}{s^2 + 2} + \frac{3s}{s^2 + 4}$$

$$C_o = \frac{1}{3} F$$

$$C_1 = \frac{1}{2 \times 1} = \frac{1}{2} F$$

$$L_1 = \frac{2}{(\sqrt{2})^2} = 1H$$

$$C_2 = \frac{1}{2 \times 1.5} = \frac{1}{3} F$$

$$L_2 = \frac{2 \times 1.5}{4} = \frac{3}{4} H$$

Q. 8. (b) Using the foster II form synthesize the function

(6)

$$Y(s) = \frac{s(s^2 + 4)(s^2 + 6)}{(s^2 + 3)(s^2 + 5)}$$

Ans. Foster II

$$Y(s) = \frac{s(s^2 + 2)(s^2 + 4)}{8(s^2 + 1)(s^2 + 3)}$$

$$= \frac{2B_1 s + 2B_2 s}{s^2 + 1} + C_3$$

$$B_1 = \frac{1}{8} \left. \frac{s(s^2 + 2)(s^2 + 4)}{(s - 1)(s^2 + 3)} \right|_{s=-j1} = \frac{3}{32}$$

$$B_2 = \frac{1}{8} \left. \frac{(s^2 + 2)(s^2 + 4)}{(s^2 + 1)(s - 1\sqrt{3})} \right|_{s=j\sqrt{3}} = \frac{1}{32}$$


$$L_1 = \frac{1}{2} \times \frac{32}{3} = \frac{16}{3}$$

$$L_2 = \frac{1}{2} \times 32 = 16 H$$

$$C_1 = \frac{2 \times \frac{3}{32}}{1} = \frac{3}{16} F$$

$$C_2 = \frac{2 \times \frac{1}{32}}{3} = \frac{1}{48} F$$

$$C_3 = \frac{1}{8} F$$

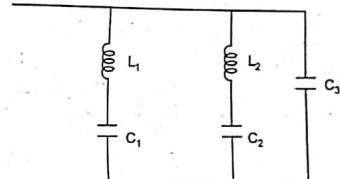

Q.9. (a) A series LCR type band pass filter has $L = 50 \text{ mH}$, $C = 130 \text{ nF}$ and $RF = 80\Omega$. (6.5)

Determine

- (i) frequency of resonance
- (ii) bandwidth
- (iii) cutoff frequency

Ans. (a) For RLC Band pass filter

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{50 \times 10^{-3} \times 130 \times 10^{-9}}} = 1.97 \times 10^3$$

$$Q = \frac{W_r L}{R} = \frac{\frac{1}{2\pi f_r} \times L}{R} = \frac{\sqrt{L/C}}{R} = \frac{\sqrt{50 \times 10^{-3}}}{80}$$

$$\frac{620}{80} = 7.75$$

$$BW = \frac{f_r}{Q} = \frac{1.97 \times 10^3}{7.75} = 254.2$$


$$f_1 = f_r - \frac{BW}{2} = 1970 - 147$$

$$= 1823$$

$$f_2 = f_r + \frac{BW}{2} = 1970 + 147$$

$$= 2117$$

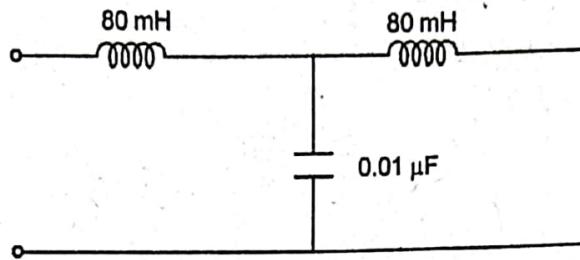Q. 9. (b) For the T-section find cutoff frequency and nominal characteristics impedance R_o . (6)



Ans.

$$\begin{aligned}
 W_C &= \sqrt{\frac{4}{LC}} \\
 &= \sqrt{\frac{4}{80 \times 2 \times 10^{-3} \times 0.01 \times 10^{-6}}} \\
 &= \sqrt{\frac{4}{1.6 \times 10^{-9}}} \\
 &= 50000 = 50 \text{ KHz}
 \end{aligned}$$

$$\begin{aligned}
 R_o &= \sqrt{\frac{L}{C}} = \sqrt{\frac{160 \times 10^{-3+1}}{.1 \times 10^{-6-2}}} = 4 \times 10^3 \\
 &= 4000
 \end{aligned}$$

$$Z_{OT} = R_o \sqrt{1 - \left(\frac{f_e}{f_c}\right)^2}$$