

UNIT-I

Book : Anand Kumar ✓  
P. Rayia

Number Systems

- ① Binary (2) → 0, 1
- ② Decimal (10) → 0, to 9
- ③ Octal (8) → 0 to 7
- ④ Hexadecimal (16) → 0 to 9, A to F

i. BINARY to

## a) Decimal

$$(11010)_2 = (?)_{10}$$

$$= 16 + 8 + 0 + 2 + 0$$

$$= \underline{\underline{(26)}}_{10}$$

## b) Octal

4 2 1

0 0 0 → 0

0 0 1 → 1

0 1 0 → 2

0 1 1 → 3

1 0 0 → 4

1 0 1 → 5

1 1 0 → 6

1 1 1 → 7

$$\begin{array}{r} (10101101)_2 = (?)_8 \\ \hline 1010 \end{array}$$

$$= (255)_8$$

c) Hexadecimal

8 4 2 1

0 0 0 0 → 0

0 0 0 1 → 1

0 0 1 0 → 2

0 0 1 1 → 3

0 1 0 0 → 4

0 1 0 1 → 5

0 1 1 0 → 6

0 1 1 1 → 7

1 0 0 0 → 8

1 0 0 1 → 9

1 0 1 0 → A

1 0 1 1 → B

1 1 0 0 → C

1 1 0 1 → D

1 1 1 0 → E

1 1 1 1 → F

$$(01010110)_2 = (?)_{16}$$

$$= (\text{B} \text{D})_{16}$$

$$= (\text{AD})_{16}$$

2. DECIMAL to

a) Binary

$$(23)_{10} = (?)_2$$

|   |    |   |
|---|----|---|
| 2 | 23 | 1 |
| 2 | 11 | 1 |
| 2 | 5  | 1 |
| 2 | 2  | 0 |
|   | 1  |   |

$$= (10111)_2$$

4)  $(0.625)_{10} = (?)_2$

$$\begin{array}{r}
 0.625 \\
 \times 2 \\
 \hline
 1.250 \\
 \times 2 \\
 \hline
 0.500 \\
 \times 2 \\
 \hline
 1.00
 \end{array}
 \quad \downarrow \quad (0.101)_2$$

b) Octal

$$(172)_{10} \rightarrow (?)_8$$

$$\begin{array}{r}
 8 | 172 | 4 \\
 8 | 21 | 5 \\
 2
 \end{array} \quad (254)_8$$

$$(0.878)_{10} \rightarrow (?)_8$$

$$\begin{array}{r}
 0.878 \\
 \times 8 \\
 \hline
 0.024 \\
 \times 8 \\
 \hline
 0.192 \\
 \times 8 \\
 \hline
 0.536 \\
 \times 8 \\
 \hline
 0.288
 \end{array}
 \quad \downarrow \quad (0.7014)_8$$

4)  $(0.625)_{10} = (?)_2$

$$\begin{array}{r}
 0.625 \\
 \times 2 \\
 \hline
 1.250 \\
 \times 2 \\
 \hline
 0.500 \\
 \times 2 \\
 \hline
 1.00
 \end{array}$$



$$(0.101)_2$$

b) Octal

$$(172)_{10} \rightarrow (?)_8$$

$$\begin{array}{r}
 8 | 172 | 4 \\
 8 | 21 | 5 \\
 2
 \end{array}$$

$$(254)_8$$

$$(0.878)_{10} \rightarrow (?)_8$$

$$\begin{array}{r}
 0.878 \\
 \times 8 \\
 \hline
 0.024 \\
 \times 8 \\
 \hline
 0.192 \\
 \times 8 \\
 \hline
 0.536 \\
 \times 8 \\
 \hline
 0.288
 \end{array}$$



$$(0.7014)_8$$

### 3. OCTAL TO

a) Binary

$$(127)_8 = (?)_2$$

$$7 = 111$$

$$2 = 010$$

$$1 = 001$$

$$\therefore (1010111)_2$$

b) Decimal

$$(42)_8 = (?)_{10}$$

$$\begin{array}{r} 4 \\ \times 8^1 \\ + 2 \\ \hline 34 \end{array}$$

$$2 = 010$$

$$\begin{aligned} 4 \times 8^1 + 2 \times 8^0 &= 32 + 2 \\ &= (34)_{10} \end{aligned}$$

c) Hexadecimal

Octal  $\rightarrow$  Binary  $\rightarrow$  Hexa

$$(127)_8 = (?)_{16}$$

$$1 = 001$$

$$2 = 010$$

$$7 = 111$$

$$\begin{array}{r} 1 \\ \times 8^2 \\ + 0 \\ \hline 1010111 \end{array}$$

$$(57)_{16}$$

$$\begin{array}{r} (3134)_5 \\ + \underline{(3133)_5} \\ \hline \end{array}$$

### ADDITION

$$\begin{array}{r} 3 1 \quad | \quad 1 \\ 3 1 \quad 3 \quad 4 \\ \hline \end{array} \quad \leftarrow \text{Remainder}$$

Valid inputs = 0, 1, 2, 3, 4

$$\begin{array}{r} 3 1 \quad 3 \quad 3 \\ \hline 1 \underline{1} \quad 3 \quad 2 \quad 2 \end{array} \quad \leftarrow \text{Quotient}$$

$$4+3=7 \qquad 5 \overline{)7} \qquad \begin{array}{r} 1 \\ 5 \\ \hline 2. \end{array}$$

$$\begin{array}{r} 1 \left( \begin{array}{r} 7 \quad F \\ B \quad A \end{array} \right)_{16} \\ + \underline{\left( \begin{array}{r} 3 \quad 9 \end{array} \right)_{16}} \\ \hline \end{array}$$

$$\begin{array}{r} F=15 \\ A=10 \end{array}$$

$$\begin{array}{r} 8 \\ - 11 \\ \hline 19 \end{array}$$

$$16 \overline{)25} \qquad \begin{array}{r} 1 \\ 16 \\ \hline 9 \end{array}$$

$$\begin{array}{r} (7342)_8 \\ - \underline{(564)}_8 \\ \hline \end{array}$$

### SUBTRACTION

Borrow the base

$$\begin{array}{r} 6 \rightarrow 2 \quad 8 \quad 3 \quad 8+2 \\ 7 \quad 3 \quad 4 \quad 2 \\ - 5 \quad 1 \quad 6 \quad 4 \\ \hline 2 \quad 1 \quad 5 \quad 6 \end{array} \quad \begin{array}{r} 1 \\ 1 \\ \hline 1 \end{array} \quad \begin{array}{r} 1 \\ 1 \\ \hline 1 \end{array} \quad \begin{array}{r} 1 \\ 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} \text{1111} \\ \text{1010} \\ \text{0100} \\ - \\ \hline \text{(1)_{16}} \end{array}$$

$$(\text{FFFF})_{16}$$

~~K-Maps~~ : Karnaugh Maps

$\boxed{2^n} \rightarrow$  no. of variables  
 ↳ No. of cells

$m \rightarrow$  minterms  $\rightarrow$  Product terms  $\sum m(\dots)$   
 $M \rightarrow$  Maxterms  $\rightarrow$  Sum terms  $\prod M(\dots)$   
 single, pair, quart, octet

Gray code: one transition at a time

| AB | C     | 0     | 1 |
|----|-------|-------|---|
| 00 | $m_0$ | $m_1$ |   |
| 01 | $m_2$ | $m_3$ |   |
| 11 | $m_6$ | $m_7$ |   |
| 10 | $m_4$ | $m_5$ |   |

$$m(0, 1, 2, 4, 7)$$

| A | B | C | 00    | 01    | 11    | 10 |
|---|---|---|-------|-------|-------|----|
| 0 | 0 | 0 | $m_0$ | $m_1$ |       |    |
| 1 | 0 | 1 | $m_4$ |       | $m_2$ |    |

$$\bar{A}\bar{B} + A\bar{B}\bar{C} + \bar{B}\bar{C} + ABC + \bar{A}\bar{C}$$

$m(0, 1, 3, 5, 7)$

|  |  | BC | 00  | 01  | 11  | 10 |
|--|--|----|-----|-----|-----|----|
|  |  | 0  | (1) | (1) | (1) |    |
|  |  | 1  |     | (1) | (1) |    |
|  |  |    |     |     |     |    |

$$\bar{A}\bar{B} + C$$

$m(3, 4, 5, 7, \cancel{12}, 13, 15, 14, 9, .)$

$AB \setminus CD$  00 01 11 10

| 00 | ..0 | ..1 | 1   | ..2 |
|----|-----|-----|-----|-----|
| 01 | (1) | (1) | (1) | ..3 |
| 11 | ..4 | (1) | (1) | ..5 |
| 10 | ..6 | 1   | ..7 | ..8 |

$$\cancel{ACD} + \bar{ABC} + ABC.$$

$$\bar{ABC} + \bar{ACD} + ABC + \bar{ACD}$$

Redundancy

## 5 Variables

|  |  | DE | 00 | 01 | 11 | 10 |
|--|--|----|----|----|----|----|
|  |  | 00 | 0  | 1  | 3  | 2  |
|  |  | 01 | 4  | 5  | 7  | 6  |
|  |  | 11 | 12 | 13 | 15 | 14 |
|  |  | 10 | 8  | 9  | 11 | 10 |

|  |  | DE | 00 | 01 | 11 | 10 |
|--|--|----|----|----|----|----|
|  |  | 00 | 16 | 17 | 19 | 18 |
|  |  | 01 | 20 | 21 | 23 | 22 |
|  |  | 11 | 26 | 29 | 31 | 30 |
|  |  | 10 | 24 | 25 | 27 | 26 |

$A = 0$

$A = 1$

$m(0, 1, 3, 5, 7, 9, 11, 17, 19, 21, 23, 30)$

|  |  | DE | 00  | 01  | 11  | 10 |
|--|--|----|-----|-----|-----|----|
|  |  | 00 | (1) | (1) | (1) |    |
|  |  | 01 | 15  | 17  |     |    |
|  |  | 11 |     |     |     |    |
|  |  | 10 |     |     |     |    |

|  |  | DE | 00 | 01 | 11  | 10  |
|--|--|----|----|----|-----|-----|
|  |  | 00 |    |    | (1) | (1) |
|  |  | 01 |    |    | 21  | 23  |
|  |  | 11 |    |    |     |     |
|  |  | 10 |    |    |     |     |

$A = 1$

Superimpose both the maps

∴ An octet is formed

$m_1 m_3 m_5 m_7 m_{17} m_{19} m_{21} m_{23}$

$$Y = \bar{B}E + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{C}E + ABCD\bar{E}$$

Q Design a logic ckt with 4 inputs A, B, C, D  
The output will produce 1 if the input is greater than 1000

A B C D

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1

0 1 1 0

0 1 1 1

1 0 0 0

1 0 0 1

1 0 1 1

1 1 0 0

1 1 0 1

1 1 1 0

1 1 1 1

| AB | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | 00 | 0  | 1  | 3  | 2  |
| 01 | 01 | 4  | 5  | 7  | 6  |
| 11 | 11 | 12 | 13 | 15 | 14 |
| 10 | 10 | 8  | 9  | 11 | 10 |

$$Y = AB\bar{C} + AD + AC$$

Quine-McClusky Method / Q.M. Method

simplify  $Y = \sum m(0, 1, 3, 7, 8, 9, 11, 15)$  using Q.M. method

|           | Group | Minterms | Variable        |
|-----------|-------|----------|-----------------|
| 0 → 0000  | 0     | 0        | A B C D<br>0000 |
| 1 → 0001  | 0     | 0        | 0001            |
| 3 → 0011  | 1     | 1        | 1000            |
| 7 → 0111  |       | 8        | 0011            |
| 8 → 1000  | 2     | 3        | 1001            |
| 9 → 1001  |       | 9        | 1001            |
| 11 → 1011 | 3     | 7        | 0111            |
| 15 → 1111 |       | 11       | 1011            |
|           | 4     | 15       | 1111            |

Adjacent groups are checked, and only one transition is acceptable

|  | Group | Minterm | Variable |
|--|-------|---------|----------|
|  | 0     | 0, 1    | 000-     |
|  |       | 0, 8    | -000     |
|  | 1     | 1, 3    | 00-1     |
|  |       | 1, 9    | -001     |
|  |       | 8, 9    | 100-     |
|  | 2     | 3, 7    | 0-11     |
|  |       | 3, 11   | -011     |
|  |       | 9, 11   | 10-1     |
|  | 3     | 7, 15   | -111     |
|  |       | 11, 15  | 1-11     |

Similarly

|  | Group | Minterm      | Variable |
|--|-------|--------------|----------|
|  | 0     | 0, 1, 8, 9   | -00-     |
|  |       | 0, 8, 1, 9   | -00-     |
|  | 1     | 1, 3, 9, 11  | -0-1     |
|  |       | 1, 9, 3, 11  | -0-1     |
|  | 2     | 3, 7, 11, 15 | --11     |
|  |       | 3, 11, 7, 15 | --11     |

Now check the variables

Group: 0  $\rightarrow \bar{B}\bar{C}$   
 1  $\rightarrow \bar{B}D$   
 2  $\rightarrow CD$

prime implicants

| No. of tables = no. of variables - 1 |

| Prime implicant terms | Primary Value | Minterms    |
|-----------------------|---------------|-------------|
| $\bar{B}\bar{C}$      | 0, 1, 8, 9    | (X) X X X   |
| $\bar{B}D$            | 1, 3, 9, 11   | X X X X     |
| $CD$                  | 3, 7, 11, 15  | X (X) X (X) |

$$Y = \bar{B}\bar{C} + CD$$

$\therefore \bar{B}D$  is redundant

Q Simplify using Q.M. method

$$0 - 0000$$

$$8 - 1000$$

$$1 - 0001$$

$$9 - 1001$$

$$2 - 0010$$

$$11 - 1011$$

$$3 - 0011$$

$$14 - 1110$$

$$5 - 0101$$

$$7 - 0111$$

~~3, 11, 7, 15~~

Now check the variables

Group: 0 →  $\bar{B}\bar{C}$   
 1 →  $\bar{B}D$   
 2 →  $CD$

$\Rightarrow$  prime implicants

| No. of tables = no. of variables - 1 |

| Prime Implicant terms | Primary Value | Miu terms               |
|-----------------------|---------------|-------------------------|
| $\bar{B}\bar{C}$      | 0, 1, 8, 9    | (X) . X      (X) X      |
| $\bar{B}D$            | 1, 3, 9, 11   | . X X      X X          |
| $CD$                  | 3, 7, 11, 15  | 1      X (X)      X (X) |

$$Y = \bar{B}\bar{C} + CD$$

∴  $\bar{B}D$  is redundant

Simplify  $\Sigma(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$  using  
Q.M. method

0 - 0 0 0 0

8 - 1 0 0 0

1 - 0 0 0 1

9 - 1 0 0 1

2 - 0 0 1 0

11 - 1 0 1 1

3 - 0 0 1 1

14 - 1 1 1 0

5 - 0 1 0 1

7 - 0 1 1 1

| Group | Minterms | Variable |
|-------|----------|----------|
| 0     | 0        | 0000     |
| 1     | 1, 2     | 0001     |
|       | 3        | 0010     |
|       | 8        | 1000     |
| 2     | 3, 8     | 0011     |
|       | 9        | 0101     |
| 3     | 7        | 1001     |
|       | 14       | 1110     |
|       | 11       | 1011     |

| Group | Minterms   | Variable |
|-------|------------|----------|
| 0     | 0, 8       | 0000     |
| 1     | 0, 1, 2, 3 | 000-     |
|       | 1, 8       | 00-0     |
|       | 1, 9       | 00-1     |
|       | 2, 3       | 001-     |
|       | 8, 9       | 100-     |
| 2     | 3, 7       | 0-11     |
|       | 3, 11      | -011     |
|       | 5, 7       | 01-1     |
|       | 9, 11      | 10-1     |

| Group | Minterms   | Variable              |
|-------|------------|-----------------------|
| 0     | 0, 2, 4, 3 | 00--                  |
|       | 0, 8       |                       |
| 6     | 0, 1, 2, 3 | 00-- $\bar{A}\bar{B}$ |
|       | 0, 1, 8, 9 | -00-                  |
|       | 0, 2, 13   | 00-1                  |
|       | 0, 8, 8, 9 | -00- $\bar{B}\bar{C}$ |

|   |          |         |    |
|---|----------|---------|----|
| 1 | 1 3 5 7  | 0 - 1   | AD |
|   | 1 3 9 11 | - 0 - 1 |    |
|   | 1 5 3 7  | 0 - - 1 | BD |
|   | 1 9 3 11 | - 0 - 1 | BD |

| Prime implicant | Primary Value | Minterms |   |   |   |     |     |     |         |
|-----------------|---------------|----------|---|---|---|-----|-----|-----|---------|
| AB              | 0, 1, 2, 3    | x        | x | x | 3 | 5 - | 7 - | 9 - | 11 14   |
| B̄C             | 0, 1, 8, 9    | x        | x |   |   |     | x   | x   |         |
| ĀD             | 1, 3, 5, 7    | x        |   | x | x | x   |     |     |         |
| B̄D             | 1, 3, 9, 11   | x        | x |   |   |     | x   | x   |         |
|                 |               | 0        | 1 | 2 | 3 | 5   | 7   | 8   | 9 11 14 |

Q Your minterms are (0, 2, 3, 5, 7, 9, 11, 14)  
(1, 4, 6, 10) don't care.


|   |   |   |   |   |   |    |     |          |
|---|---|---|---|---|---|----|-----|----------|
| 0 | 2 | 3 | 5 | 7 | 9 | 14 |     |          |
| x | x | x |   | x |   |    | BD  | 1 3 9 11 |
| x | x |   |   |   | x |    | ĀB | 0 1 2 3  |
| x |   |   |   | x |   |    | B̄C | 0 1 8 9  |
|   | x | x | x | x |   |    | ĀD | 1 3 5 7  |

$$\bar{A}\bar{B} + \bar{A}D$$

11/8/17

## Combinational Circuits

Works only on present input

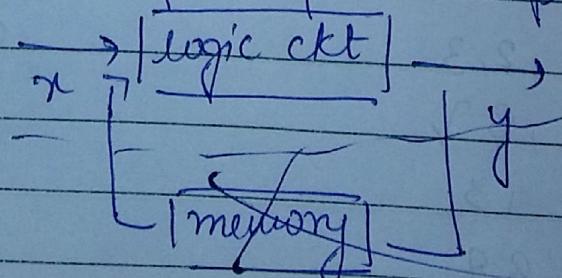

|   |          |         |            |
|---|----------|---------|------------|
| 1 | 1 3 5 7  | 0 - - 1 | $\bar{A}D$ |
|   | 1 3 9 11 | - 0 - 1 |            |
|   | 1 5 3 7  | 0 - - 1 | $\bar{B}D$ |
|   | 1 9 3 11 | - 0 - 1 | $\bar{B}D$ |

| Prime implicant  | Primary Value | Minterms   |
|------------------|---------------|--|
| $\bar{A}B$       | 0, 1, 2, 3    | x   <del>x</del>   <del>x</del>   3   5   7   9   11   1 |
| $\bar{B}\bar{C}$ | 0, 1, 8, 9    | x   x   x   x   x   x   x   x   x   x                    |
| $\bar{A}D$       | 1, 3, 5, 7    | x   x   x   x   x   x   x   x   x   x                    |
| $\bar{B}D$       | 1, 3, 9, 11   | x   x   x   x   x   x   x   x   x   x                    |
|                  | 0 1 2 3 8     | 0 1 2 3 8 7 8 9 11                                       |

Q Your minterms are (0, 2, 3, 5, 7, 9, 11, 14)  
(1, 8, 11) don't care.


|   |     |   |     |     |   |    |                  |          |
|---|-----|---|-----|-----|---|----|------------------|----------|
| 0 | 2   | 3 | 5   | 7   | 9 | 14 | $\bar{B}D$       | 1 3 9 11 |
|   |     | x |     |     | x |    | $\bar{A}\bar{B}$ | 0 1 2 3  |
| x | (x) | x |     |     |   |    | $\bar{B}\bar{C}$ | 0 1 8 9  |
| x |     |   |     |     | x |    | $\bar{A}D$       | 1 3 5 7  |
|   | x   |   | (x) | (x) |   |    |                  |          |

$$\bar{A}\bar{B} + \bar{A}D$$

1/8/17

## Combinational Circuits

works only on present input

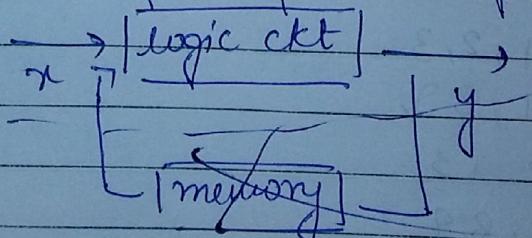

## Adders



Addition of bits

↳ half adder

it adds 2 bit at a time ( $A+B$ )

| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0   | 0     |
| 0 | 1 | 1   | 0     |
| 1 | 0 | 1   | 0     |
| 1 | 1 | 0   | 1     |

K-Maps for  $S \& C$

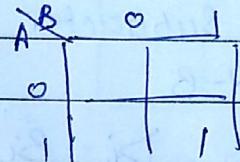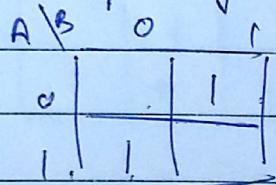

$$\begin{aligned} \text{Sum} &= \bar{A}\bar{B} + A\bar{B} \\ &= A \oplus B \end{aligned}$$

$$\text{Carry} = AB$$

→ Full adder

it adds 3 bit at a time ( $A+B+C$ )

| A | B | C | S | Carry |
|---|---|---|---|-------|
| 0 | 0 | 0 | 0 | 0     |
| 0 | 0 | 1 | 1 | 0     |
| 0 | 1 | 0 | 1 | 0     |
| 0 | 1 | 1 | 0 | 1     |
| 1 | 0 | 0 | 1 | 0     |
| 1 | 0 | 1 | 0 | 1     |
| 1 | 1 | 0 | 0 | 1     |
| 1 | 1 | 1 | 1 | 1     |

K-Maps

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | .  | 1  |    | 1  |
| 1      | 1  |    | 1  |    |

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

| A \ BC | 00 | 01  | 11  | 10  |
|--------|----|-----|-----|-----|
| 0      | .  |     | (1) |     |
| 1      |    | (1) | (1) | (1) |

$$C = BC + AC + AB$$

Subtractor

→ Half Subtractor  
 $A - B$

| A | B | D <sub>i</sub> | B <sub>i</sub> |
|---|---|----------------|----------------|
| 0 | 0 | 0              | 0              |
| 0 | 1 | 1              | 1              |
| 1 | 0 | 1              | 0              |
| 1 | 1 | 0              | 0              |

K-Maps

| A \ B | 0 | 1 |
|-------|---|---|
| 0     |   | 1 |
| 1     | 1 |   |

| A \ B | 0 | 1 |
|-------|---|---|
| 0     |   | 1 |
| 1     | 1 |   |

$$D = A\bar{B} + \bar{A}B$$

$$B = \bar{A}B$$

→ Full Subtractor

$$A - B - C$$

| A | B | C | D | B |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 |

K-Maps

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 0  | 1  | 1  | 1  |
| 1      | 1  | *  | 1  | 1  |

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 0  | 1  | 1  | 1  |
| 1      | 1  | 1  | 0  | 1  |


$$D = A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC$$

$$B = AC + \bar{A}B + BC$$

- Design a 4 bit parallel adder  
 Design a 4 bit look ahead carry generator
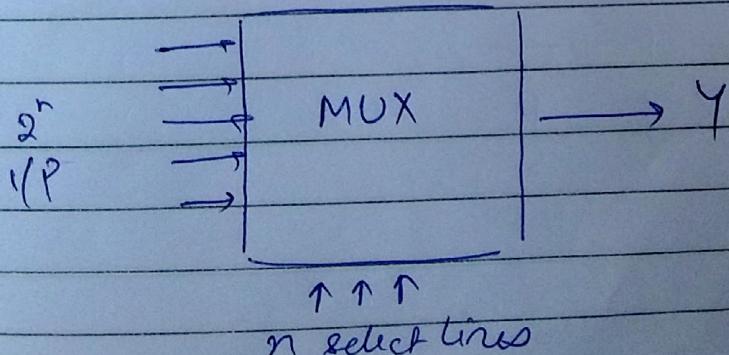
## MULTIPLEXER (MUX)


Converts parallel input data to serial output  
 (many to single)




They are used to increase the amount of data that can be sent over the network within a certain amt. of time by bandwidth

Also called a data selector, is a logic ckt. that accepts several data inputs and allows only one of them to get through to the output

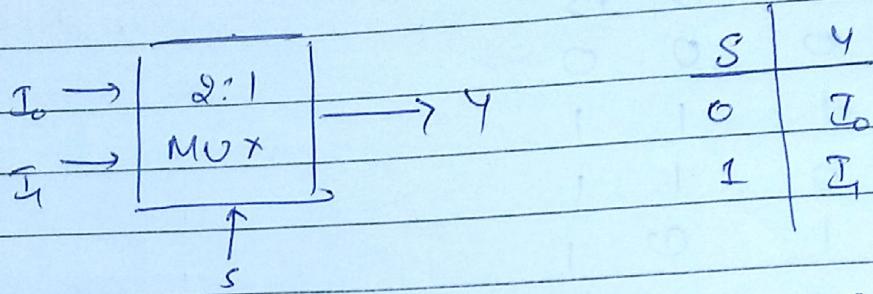Multiplexing means sharing. A multiplexer makes it possible for several signals to share one device and/or resource



$$\therefore Y = \bar{S} I_0 + S I_1$$

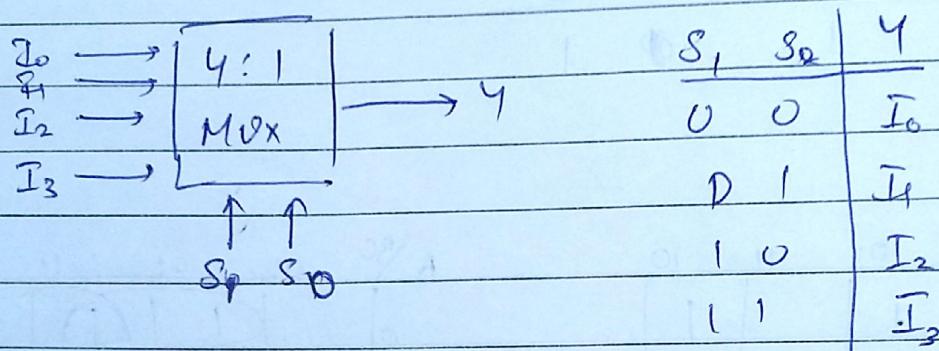

| $S_1$ | $S_2$ | $Y$         |
|-------|-------|-------------|
| 0     | 0     | $I_0$       |
| 0     | 1     | $\bar{I}_1$ |
| 1     | 0     | $I_2$       |
| 1     | 1     | $\bar{I}_3$ |

$$\therefore Y = \bar{S}_1 \bar{S}_2 I_0 + \bar{S}_1 S_2 \bar{I}_1 + S_1 \bar{S}_2 I_2 + S_1 S_2 \bar{I}_3$$

Q Implement the following boolean funct" using

a) 16:1 MUX


b) 8:1 MUX

c) 4:1 MUX

d) 2:1 MUX

$$f = \sum m(0, 1, 3, 4, 7, 8, 9, 11, 14, 15)$$

Ans 4 variable funct

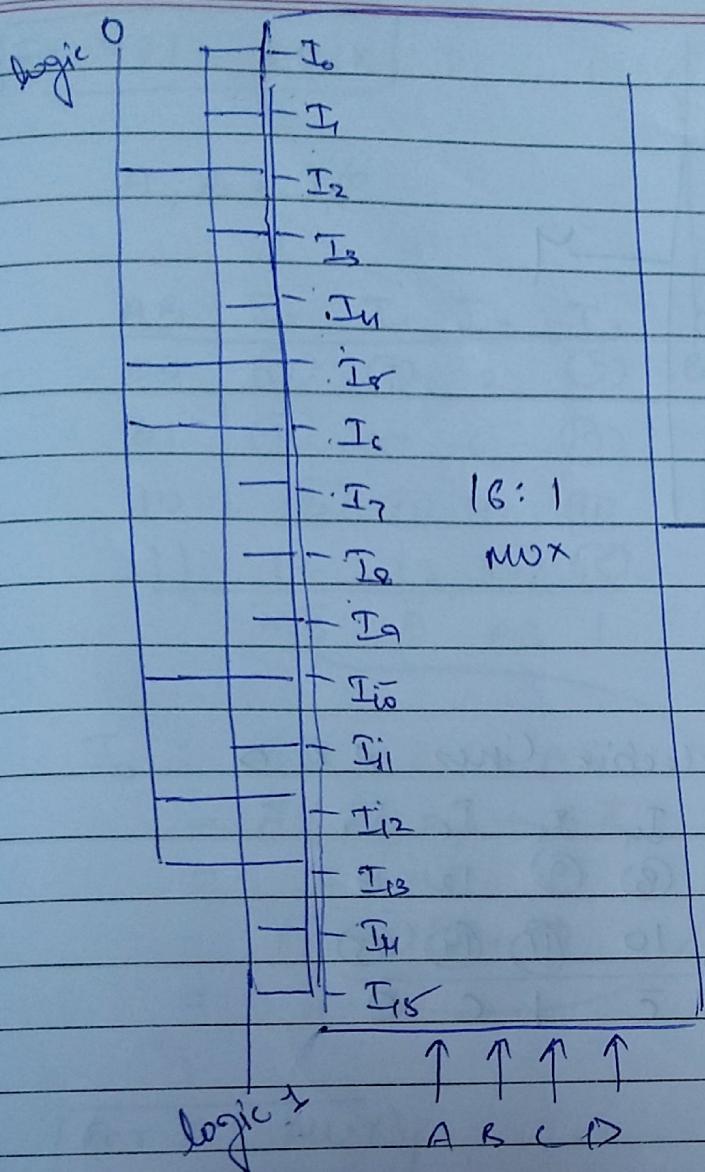


|    | A | B | C | D |
|----|---|---|---|---|
| 0  | 0 | 0 | 0 | 0 |
| 1  | 0 | 0 | 0 | 1 |
| 2  | 0 | 0 | 1 | 0 |
| 3  | 0 | 0 | 1 | 1 |
| 4  | 0 | 1 | 0 | 0 |
| 5  | 0 | 1 | 0 | 1 |
| 6  | 0 | 1 | 1 | 0 |
| 7  | 0 | 1 | 1 | 1 |
| 8  | 1 | 0 | 0 | 0 |
| 9  | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |
| 11 | 1 | 0 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 |
| 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |

[For 8:1 MUX]

$$A = \overline{I_1} / P \quad \therefore B, C, D : \text{select lines}$$


|           | I <sub>0</sub> | I <sub>1</sub> | I <sub>2</sub> | I <sub>3</sub> | I <sub>4</sub> | I <sub>5</sub> | I <sub>6</sub> | I <sub>7</sub>                 |
|-----------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|--------------------------------|
| $\bar{A}$ | (0)            | (1)            | 2              | (3)            | (4)            | 5              | 6              | (7) → High terms<br>(question) |
| A         | (8)            | (9)            | 10             | (11)           | 12             | 13             | (14)           | (15)                           |
|           | 1              | 1              | 0              | 1              | $\bar{A}$      | 0              | A              | 1                              |

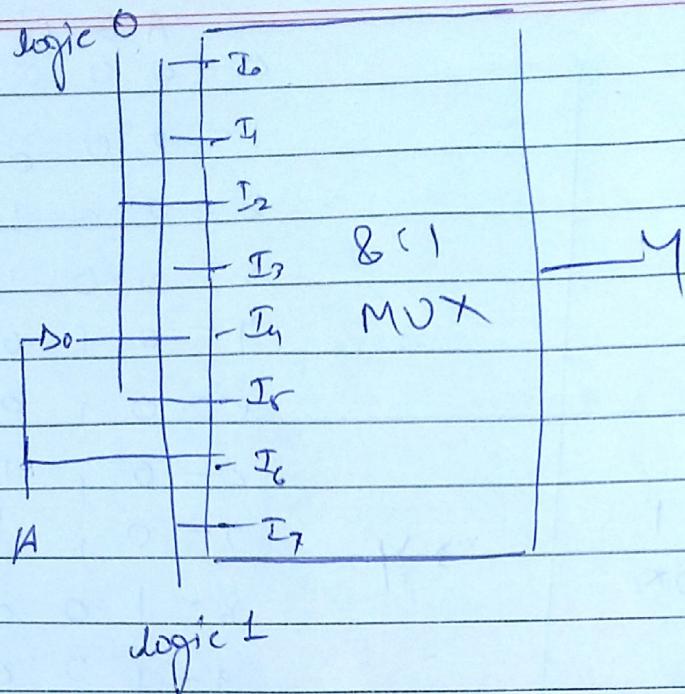

Input = C ; selective lines A B D

| I <sub>0</sub> | I <sub>1</sub> | I <sub>2</sub> | I <sub>3</sub> | I <sub>4</sub> | I <sub>5</sub> | I <sub>6</sub> | I <sub>7</sub> |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| $\bar{C}$      | ⑥              | ⑦              | ⑨              | 5              | ⑧              | ⑩              | 12             |
| C              | 2              | ③              | 6              | ⑦              | 10             | ⑪              | ⑭              |


logic 1

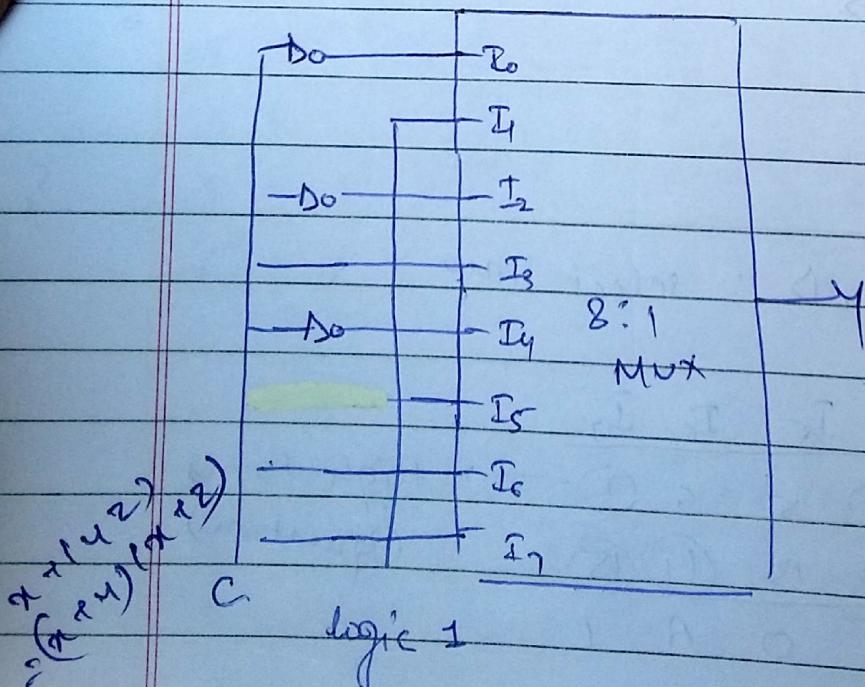

For 4:1 MUX

$$A, B = I/P$$

| AB | I <sub>0</sub>      | I <sub>1</sub> | I <sub>2</sub> | I <sub>3</sub> |
|----|---------------------|----------------|----------------|----------------|
| 00 | (C)                 | (D)            | 2              | (3)            |
| 01 | (4)                 | 5              | 6              | (7)            |
| 10 | (8)                 | (9)            | 10             | (11)           |
| 11 | 12                  | 13             | (14)           | (15)           |
|    | $\bar{A} + \bar{B}$ | $\bar{B}$      | AB             | 1              |

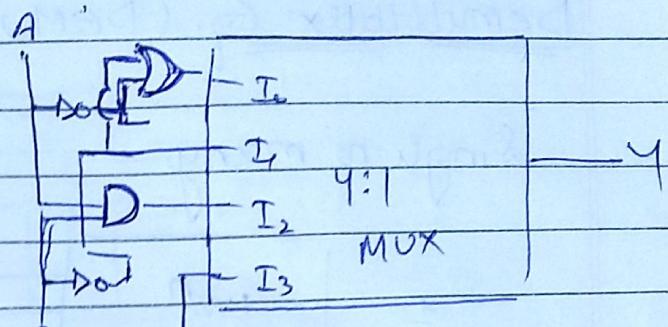


logic 1

$$\begin{aligned}
 I_0 &: \bar{A}\bar{B} + \bar{A}B + A\bar{B} \\
 &= \bar{A}(\bar{B} + B) + A\bar{B} \\
 &= \bar{A} + A\bar{B} \\
 &= (\bar{A} + A)(\bar{A} + B) \\
 &= \bar{A} + \bar{B}
 \end{aligned}$$

For 2:1 MUX

## Demultiplex Eq. (DEMUX) (called data distributor)

Single to many

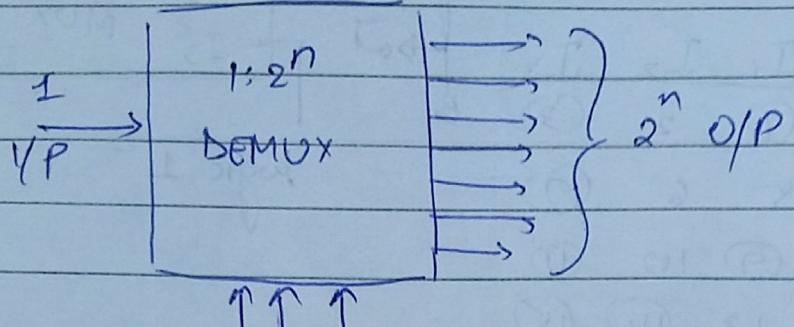

1 : 2

| I/P | S <sub>2</sub> | O/P                             |
|-----|----------------|---------------------------------|
| I   | S              | Y <sub>0</sub> ; Y <sub>1</sub> |
| I   | 0              | I; 0                            |
| I   | 1              | 0; I                            |

$$Y_0 = \bar{S}I$$

$$Y_1 = SI$$


1 : 4

| I/P | S <sub>1</sub> | S <sub>0</sub> | Y <sub>0</sub> | Y <sub>1</sub> | Y <sub>2</sub> | Y <sub>3</sub> |
|-----|----------------|----------------|----------------|----------------|----------------|----------------|
| I   | 0              | 0              | I              | 0              | 0              | 0              |
| I   | 0              | 1              | 0              | I              | 0              | 0              |
| I   | 1              | 0              | 0              | 0              | I              | 0              |
| I   | 1              | 1              | 0              | 0              | 0              | I              |

Q Design a full ~~adder~~ ladder using DEMUX


$$S = \sum m(1, 2, 4, 7)$$

$$C = \sum m(3, 5, 6, 7)$$

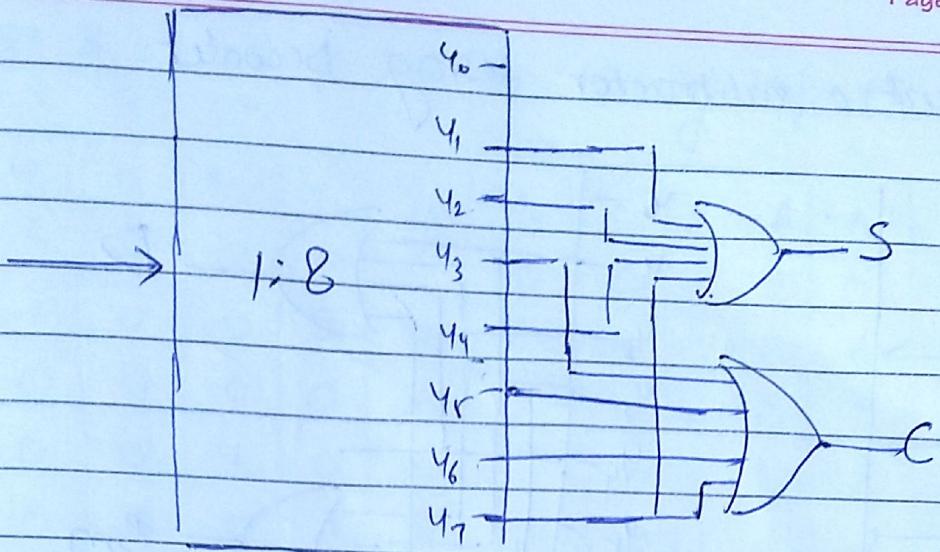
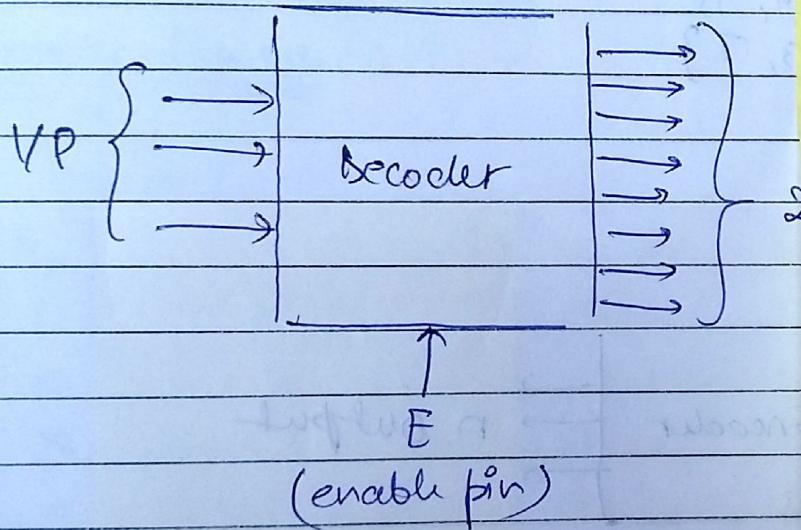
## DECODER

It converts  $n$  inputs into  $2^n$  outputs



### DECODER


It is a combinational logic ckt. that converts a binary integer value to an associated pattern of output bits.

used in data demultiplexing, memory address decoding.

2 to 4

| E | A | B | Y <sub>3</sub> | Y <sub>2</sub> | Y <sub>1</sub> | Y <sub>0</sub> |
|---|---|---|----------------|----------------|----------------|----------------|
| 0 | x | x | 0              | 0              | 0              | 0              |
| 1 | 0 | 0 | 1              | 0              | 0              | 0              |
| 1 | 0 | 1 | 0              | 1              | 0              | 0              |
| 1 | 1 | 0 | 0              | 0              | 1              | 0              |
| 1 | 1 | 1 | 0              | 0              | 0              | 1              |


I Implement a subtractor using Decoder

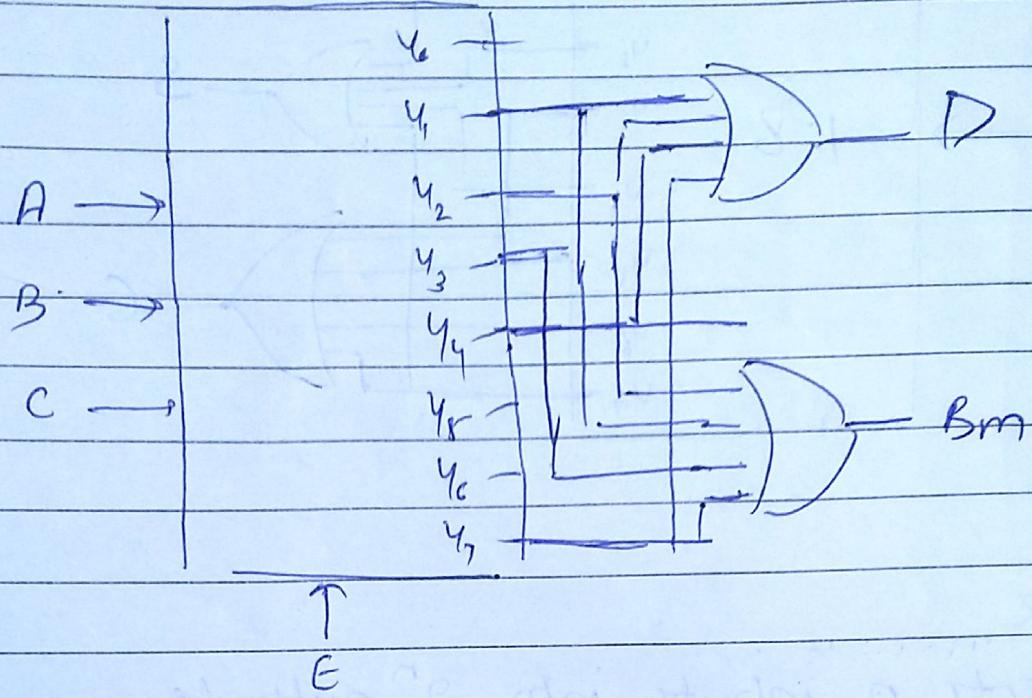

$$D = \{1, 2, 4, 7\}$$

$$B_m = \{1, 2, 3, 7\}$$

### ENCODER

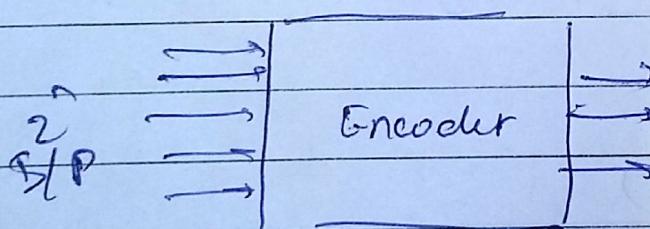

4:2


| E | A | B | C | D |
|---|---|---|---|---|
| 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |

### ENCODER

It is a device / ckt. that converts info. from one format or code to another for the purpose of standardization, speed or compression.

It receives digits, alphabets, or special symbols. It converts

0 1  
1 0  
1 1

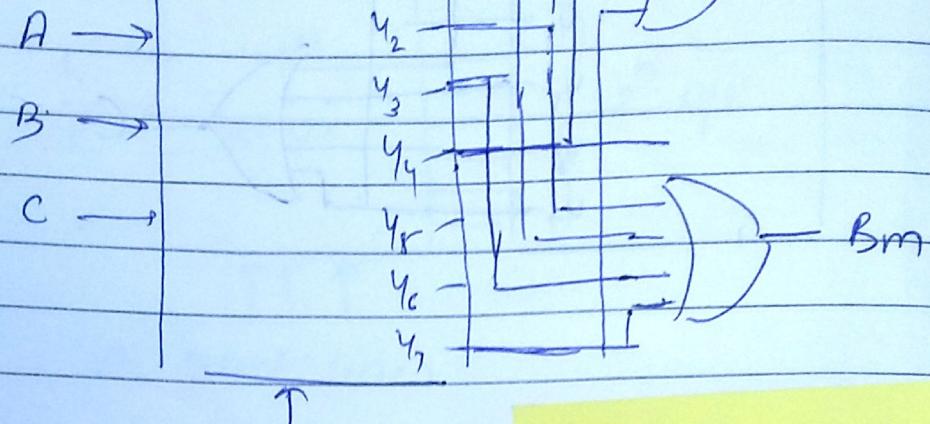


$$D = \{1, 2, 4, 7\}$$

$$B_m = \{1, 2, 3, 7\}$$

them to their respective binary codes  
 $2^n: I/P \rightarrow n: O/P$

### ENCODER

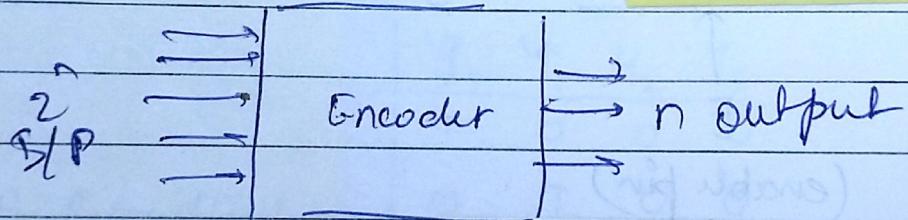

4:2

| E | A | B | C | D | Y <sub>0</sub> | Y <sub>1</sub> | Y <sub>2</sub> |
|---|---|---|---|---|----------------|----------------|----------------|
| 0 | 1 | 0 | 0 | 0 | 0              | 0              | 0              |
| 1 | 0 | 1 | 0 | 0 | 0              | 1              | 0              |

8: 3

## Octal to binary input

| $y_0$ | $y_1$ | $y_2$ | $y_3$ | $y_4$ | $y_5$ | $y_6$ | $y_7$ | A | B | C | E |
|-------|-------|-------|-------|-------|-------|-------|-------|---|---|---|---|
| 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0 | 0 | 0 | 1 |
| 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0 | 0 | 1 | 1 |
| 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0 | 1 | 0 | 1 |
| 0     | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0 | 1 | 1 | 1 |
| 0     | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 1 | 0 | 0 | 1 |
| 0     | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 1 | 0 | 1 | 1 |
| 0     | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 1 | 1 | 0 | 1 |
| 0     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1 | 1 | 1 | 1 |

Priority Encoder

4: 2

| $y_0$ | $y_1$ | $y_2$ | $y_3$ | A | B | E |
|-------|-------|-------|-------|---|---|---|
| 1     | 0     | 0     | 0     | 0 | 0 | 1 |
| x     | 1     | 0     | 0     | 0 | 1 | 1 |
| x     | x     | 1     | 0     | 1 | 0 | 1 |
| x     | x     | x     | 1     | 1 | 1 | 1 |

PRIORITY ENCODER

It is a ckt. that compresses multiple binary inputs to into a smaller number of outputs.

A single bit 4 to 2 encoder, where highest priority inputs are to the left  
'x' indicates an

| $y_0$ | $y_1$ | $y_2$ | $y_3$ | $y_4$ | $y_5$ | $y_6$ | $y_7$ | $y_8$ | $y_9$ | $y_{10}$ | $y_{11}$ |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|----------|
| 00    |       | 1     | 1     | 1     | 1     |       |       | 000   | 000   | 00       |          |
| 01    |       | 1     | 1     | 1     | 1     |       |       | 001   | 001   | 00       |          |
| 10    |       | 1     | 1     | 1     | 1     |       |       | 010   | 010   | 00       |          |
| 11    |       | 1     | 1     | 1     | 1     |       |       | 011   | 011   | 00       |          |

$$y = y_2 + y_3$$

el to binary input

|   | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $Q_1$ | $Q_0$ | $E$ |
|---|-------|-------|-------|-------|-------|-------|-----|
| 0 | 0     | 0     | 0     | 0     | X     | X     | 0   |
| 0 | 0     | 0     | 0     | 1     | 0     | 0     | 1   |
| 0 | 0     | 0     | 1     | X     | 0     | 1     | 1   |
| 0 | 1     | 1     | X     | X     | 1     | 0     | 1   |
| 1 | X     | X     | X     | X     | 1     | 1     | 1   |

irrelevant value, i.e.  
any I/P here yields  
same O/P since it is  
superseded by higher  
priority I/P

| $I_3$ | $I_2$ | $I_1$ | $I_0$ | $Q_1$ | $Q_0$ | $E$ |
|-------|-------|-------|-------|-------|-------|-----|
| 0     | 0     | 0     | 0     | X     | X     | 0   |
| 0     | 0     | 0     | 1     | 0     | 0     | 1   |
| 0     | 0     | 1     | X     | 0     | 1     | 1   |
| 0     | 1     | 1     | X     | 1     | 0     | 1   |
| 1     | X     | X     | X     | 1     | 1     | 1   |

B E

B

1.

1


1

1

$Y_2$

## UNIT - II

### Sequential Circuits

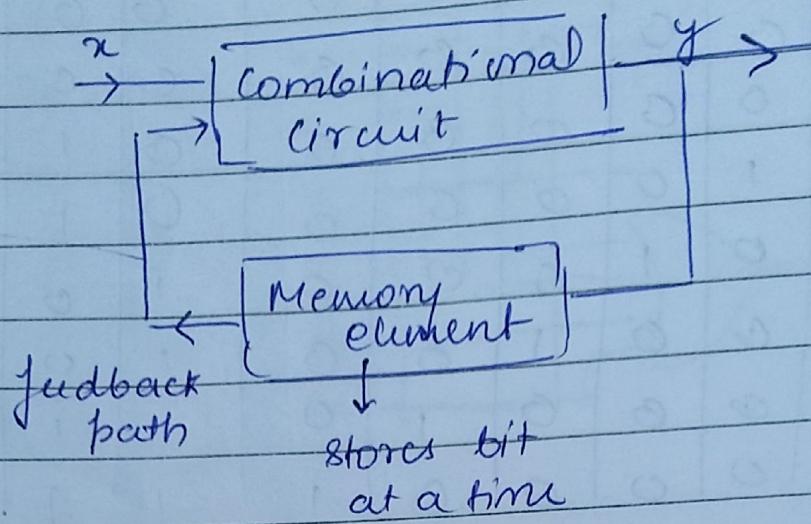

Register = combination of no. of flip flops  
(1 flip flop stores 1 bit at a time)

### Types

① Synchronous S. c.

(clocked)

input and output

are synchronised


② Asynchronous s.c.

(unclocked)


latch

Triggering → level      +ve, -ve  
                → edge      +ve, -ve

clock pulse : wave of square chain

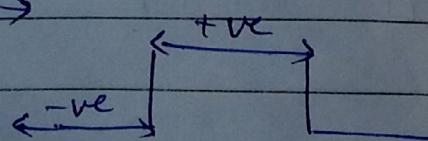

edge triggering

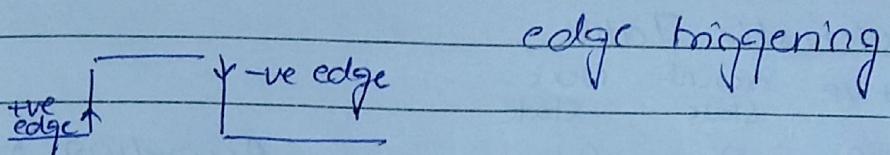


\* Difference b/w a latch and a flip-flop
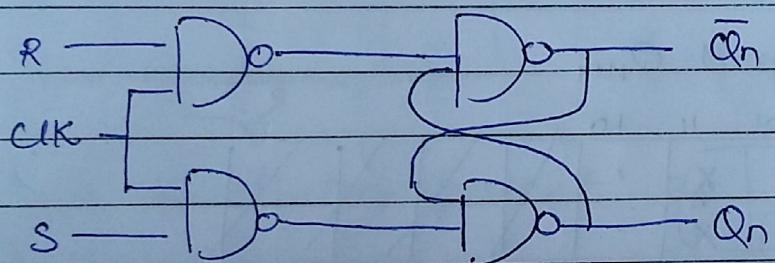
### Types of flip flop

↓      ↓      ↓      ↓  
RS      D      JK      T

① RS: Reset / Set flip flop → limitation: we cannot give 11 in RS



Truth table: tells the present state  $\rightarrow Q_n$

Characteristic table: ~~tells~~ tells next state

Excitation table

### Truth Table

| C | R | S | $Q_n$ | $\bar{Q}_n$ |                  |
|---|---|---|-------|-------------|------------------|
| 1 | 0 | 0 | $Q_n$ | $\bar{Q}_n$ | no change state  |
| 1 | 0 | 1 | 1     | 0           | Set state        |
| 1 | 1 | 0 | 0     | 1           | Reset state      |
| 1 | 1 | 1 | X     | X           | Prohibited state |


Characteristic Table

| Present VP | Present State | Next State | $Q_{n+1}$                         |
|------------|---------------|------------|-----------------------------------|
| 0          | 0             | 0          | $Q_n = 0$                         |
| 0          | 0             | 1          | $Q_n = 1$                         |
| 0          | 1             | 0          | 1                                 |
| 0          | 1             | 1          | 1                                 |
| 1          | 0             | 0          | 0                                 |
| 1          | 0             | 1          | 0                                 |
| 1          | 1             | 0          | $X \rightarrow \text{don't care}$ |
| 1          | 1             | 1          | $X$                               |

According to the values of  $R$  &  $S$ , the value of  $Q_n$  is substituted in  $Q_{n+1}$  and then the value of  $Q_n$  is checked

[from Truth Table]

K-Map to find  $Q_{n+1}$

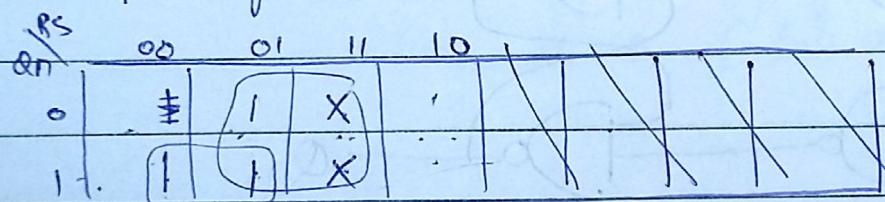


$$\underline{S + \bar{R}Q_n}$$

Excitation Table

| $Q_n$ | $Q_{n+1}$ | R                | S     |
|-------|-----------|------------------|-------|
| 0     | 0         | $X \in \{0, 1\}$ | 0 0   |
| 0     | 1         | 0                | 1     |
| 1     | 0         | 1                | 0     |
| 1     | 1         | 0                | 0 1 X |

## D : Delay flip flop

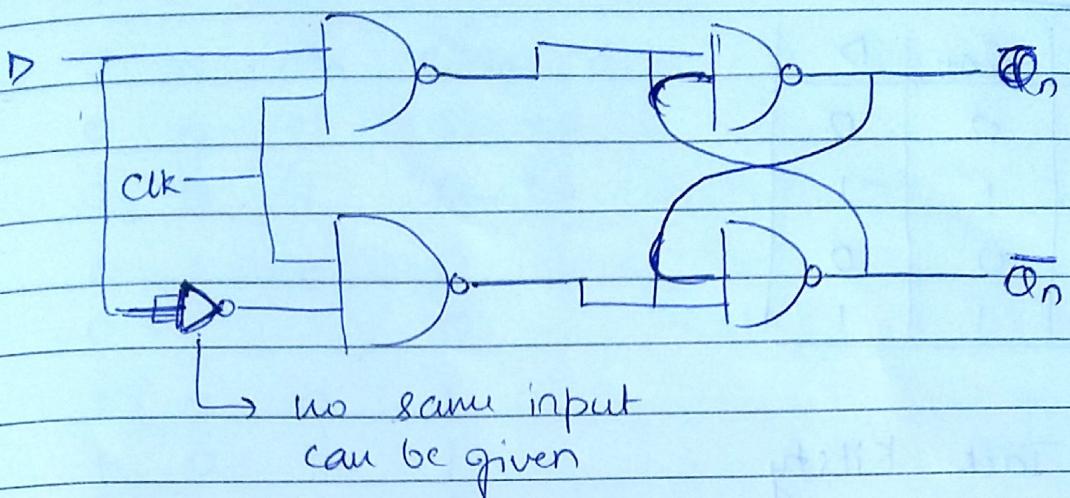

Truth Table

| C | D | Q <sub>n</sub> | Q̄ <sub>n</sub> |
|---|---|----------------|-----------------|
| 1 | 0 | 0              | 1               |
| 1 | 1 | 1              | 0               |

Since the output is reversed  
of input D

It is called transparent as input = output

21/8/17

## Delay

Characteristic Table

| D | Q <sub>n</sub> | Q <sub>n+1</sub> |
|---|----------------|------------------|
| 0 | 0              | 0                |
| 0 | 1              | 0                |
| 1 | 0              | 1                |
| 1 | 1              | 1                |


$$\underline{| Q_{n+1} = D |}$$

Excitation Table

| $d_n$ | $d_{n+1}$ | $D$ |
|-------|-----------|-----|
| 0     | 0         | 0   |
| 0     | 1         | 1   |
| 1     | 0         | 0   |
| 1     | 1         | 1   |

③ JK : Jack Kilby

It is the modified version of RS flip flop

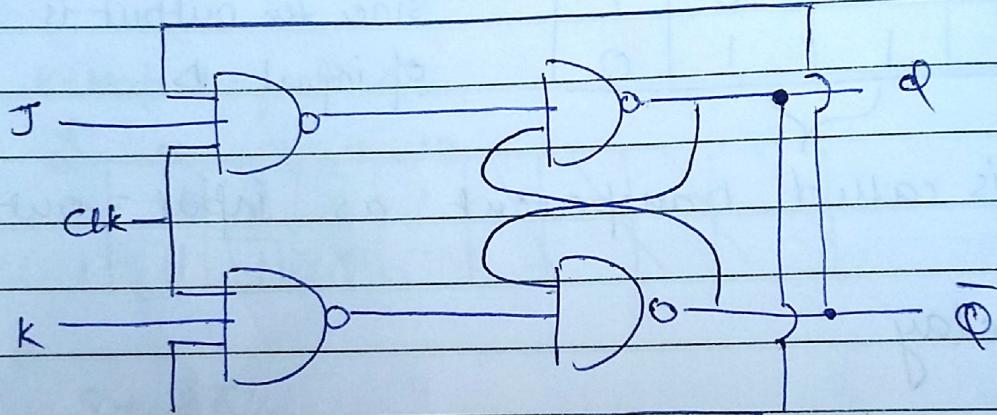Truth Table

| C | J | K | Q         | $\bar{Q}$ |
|---|---|---|-----------|-----------|
| 1 | 0 | 0 | Q         | $\bar{Q}$ |
| 1 | 0 | 1 | 0         | 1         |
| 1 | 1 | 0 | 1         | 0         |
| 1 | 1 | 1 | $\bar{Q}$ | Q         |

→ No change state

→ Reset state

→ Set state

→ Toggle state

(inverse of last output)


Characteristic Tabl

| J | K | $Q_n$ | $Q_{n+1}$       |
|---|---|-------|-----------------|
| 0 | 0 | 0     | $Q_n = 0$       |
| 0 | 0 | 1     | $Q_n = 1$       |
| 0 | 1 | 0     | 0               |
| 0 | 1 | 1     | 0               |
| 1 | 0 | 0     | 1               |
| 1 | 0 | 1     | 1               |
| 1 | 1 | 0     | $\bar{Q}_n = 1$ |
| 1 | 1 | 1     | $\bar{Q}_n = 0$ |

Excitation Tabl

| $d_n$ | $Q_{n+1}$ | J | K |
|-------|-----------|---|---|
| 0     | 0         | 0 | 0 |
| 0     | 1         | 1 | 0 |
| 1     | 0         | x | 0 |
| 1     | 1         | x | 0 |

④ T : Toggle

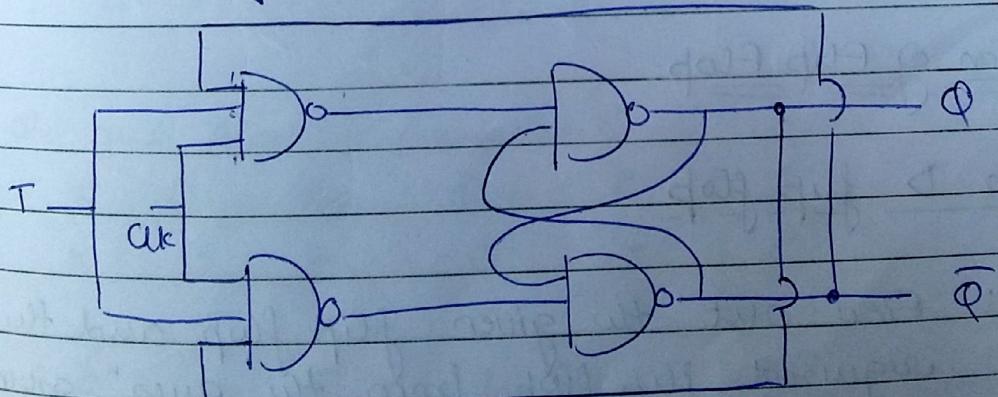

### Truth Table

| C | T | Q           | $\bar{Q}$   |
|---|---|-------------|-------------|
| 1 | 0 | $Q_n$       | $\bar{Q}_n$ |
| 1 | 1 | $\bar{Q}_n$ | $Q_n$       |

### Characteristic Table

| T | $Q_n$ | $Q_{n+1}$         |
|---|-------|-------------------|
| 0 | 0     | 0 ( $Q_n$ )       |
| 0 | 1     | 1 ( $Q_n$ )       |
| 1 | 0     | 1 ( $\bar{Q}_n$ ) |
| 1 | 1     | 0 ( $\bar{Q}_n$ ) |

### Excitation Table

| $Q_n$ | $Q_{n+1}$ | T |
|-------|-----------|---|
| 0     | 0         | 0 |
| 0     | 1         | 1 |
| 1     | 0         | 1 |
| 1     | 1         | 0 |

### Conversion of Flip Flop

#### ① RS to D flip-flop

- \* Step 1 : Find out the given flip flop and the required flip flop from the ques' given
- Step 2 : Design a excitation table of given flip flop.

Step 3: Design a characteristic table of required flip flop

Step 4: Make a conversion table using these two tables

Step 5: Find out the required expression of required flip flops using k-map

Step 6: Design block diagram of required flip flop

[RS to D]

1. RS → Given      D → Required



|   | cl <sub>n</sub> | cl <sub>n+1</sub> | R | S |
|---|-----------------|-------------------|---|---|
| 0 | 0               | x                 | 0 |   |
| 0 | 1               | 0                 | 1 |   |
| 1 | 0               | 1                 | 0 |   |
| 1 | 1               | 0                 | x |   |

| 3. | D | Q <sub>n</sub> | Q <sub>n+1</sub> |
|----|---|----------------|------------------|
| 0  | 0 | 0              |                  |
| 0  | 1 | 0              |                  |
| 1  | 0 | 1              |                  |
| 1  | 1 | 1              |                  |

4. Q<sub>n</sub> and Q<sub>n+1</sub> is common

|   | R | S | Q <sub>n</sub> | Q <sub>n+1</sub> | R | S |
|---|---|---|----------------|------------------|---|---|
| x | 0 | 0 | 0              | x                | 0 |   |
| + | 0 | 1 | 0              | 0                | 0 |   |
| g | 1 | 0 | 1              | 0                | 1 |   |
| g | 1 | 1 | 1              | 0                | x |   |


5. we take present value not futuristic

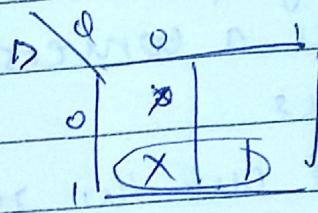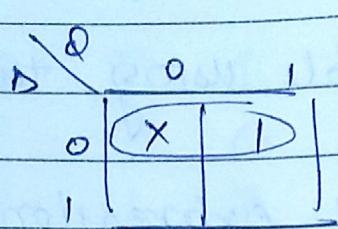

$$R = \bar{D}$$

$$S = D$$

6

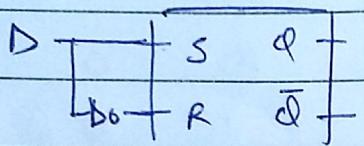

② JK to T

1.  $JK \rightarrow T$


| $Q_n$ | $Q_{n+1}$ | J | K |  |
|-------|-----------|---|---|--|
| 0     | 0         | 0 | X |  |
| 0     | 1         | 1 | X |  |
| 1     | 0         | X | 1 |  |
| 1     | 1         | X | 0 |  |

3  $T \text{ } Q_n \text{ } Q_{n+1}$

|   |   |   |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

u.


| T | Qn | Qn+1 | J | K |
|---|----|------|---|---|
| 0 | 0  | 0    | 0 | X |
| 1 | 0  | 1    | 1 | X |
| 1 | 1  | 0    | X | 1 |
| 0 | 1  | 1    | X | 0 |

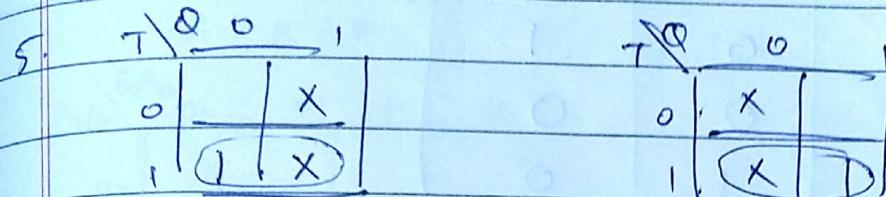

$$J = T$$

$$K = T$$

6

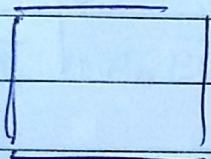

Q What is race around condition and how do we eliminate it

- Race-around condition is due to level triggering
- Master-slave flip flop  
we apply 2 flip flops

Comparator1-bit magnitude comparator

| A | B | $A > B$ | $A = B$ | $A < B$ |
|---|---|---------|---------|---------|
| 0 | 0 | 0       | 1       | 0       |
| 0 | 1 | 0       | 0       | 1       |
| 1 | 0 | 1       | 0       | 0       |
| 1 | 1 | 0       | 1       | 0       |

$$A > B = A\bar{B}$$

| $A \setminus B$ | 0 | 1 |
|-----------------|---|---|
| 0               | 1 | 1 |
| 1               | 1 | 0 |

$$A = B : \bar{A}\bar{B} + AB$$

| $A \setminus B$ | 0 | 1 |
|-----------------|---|---|
| 0               | 1 | 1 |
| 1               | 1 | 0 |

$$A < B = \bar{A}B$$

| $A \setminus B$ | 0 | 1 |
|-----------------|---|---|
| 0               | 1 | 1 |
| 1               | 1 | 0 |

2-bit magnitude comparator

| A           | B           | $A > B$ | $A = B$ | $B > A$ |
|-------------|-------------|---------|---------|---------|
| $A_1 \ A_0$ | $B_1 \ B_0$ | 0       | 1       | 0       |
| 0 0         | 0 0         | 0       | 1       | 0       |
| 0 0         | 0 1         | 0       | 0       | 1       |
| 0 0         | 1 0         | 0       | 0       | 1       |
| 0 0         | 1 1         | 0       | 0       | 1       |
| 0 1         | 0 0         | 1       | 0       | 0       |
| 0 1         | 0 1         | 0       | 1       | 0       |
| 0 1         | 1 0         | 0       | 0       | 1       |
| 0 1         | 1 1         | 0       | 0       | 1       |
| 1 0         | 0 0         | 1       | 0       | 0       |
| 1 0         | 0 1         | 1       | 0       | 0       |
| 1 0         | 1 0         | 0       | 1       | 0       |
| 1 0         | 1 1         | 0       | 0       | 1       |

|   |   |   |   |   |   |   |
|---|---|---|---|---|---|---|
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 |

 $A > B$ 

| $A_1 A_0 \setminus B_1 B_0$ | 00 | 01 | 11 | 10 |
|-----------------------------|----|----|----|----|
| 00                          |    |    |    |    |
| 01                          | 1  |    |    |    |
| 11                          | 1  | 1  |    |    |
| 10                          | 1  | 1  | 1  |    |

 $A = B$ 

| $A_1 A_0 \setminus B_1 B_0$ | 00 | 01 | 11 | 10 |
|-----------------------------|----|----|----|----|
| 00                          | 1  |    |    |    |
| 01                          |    | 1  |    |    |
| 11                          |    |    | 1  |    |
| 10                          |    |    | 1  | 1  |

$$= A_1 \bar{B}_1 + A_0 \bar{B}_0 \bar{B}_1 + A_1 A_0 \bar{B}_0 =$$

 $A < B$ 

| $A_1 A_0 \setminus B_1 B_0$ | 00 | 01 | 11 | 10 |
|-----------------------------|----|----|----|----|
| 00                          |    |    |    |    |
| 01                          |    |    |    |    |
| 11                          |    |    |    |    |
| 10                          |    |    |    | 1  |

## 4-bit magnitude comparator

### Code converter

① Binary to BCD (Binary Coded Decimal)

BCD: Valid from 0 to 9

Binary

|   |    |   |
|---|----|---|
| 2 | 24 | 0 |
| 2 | 12 | 0 |
| 2 | 6  | 0 |
| 2 | 3  | 1 |
|   | 1  |   |

24

BCD

24  
0010  
0100

(100100) BCD

(11000)<sub>2</sub>

## ① 4-bit binary code

|    | A | B | C | D | B <sub>4</sub> | B <sub>3</sub> | B <sub>2</sub> | B <sub>1</sub> | B <sub>0</sub> |
|----|---|---|---|---|----------------|----------------|----------------|----------------|----------------|
| 0  | 0 | 0 | 0 | 0 | 0              | 0              | 0              | 0              | 0              |
| 1  | 0 | 0 | 0 | 1 | 0              | 0              | 0              | 0              | 1              |
| 2  | 0 | 0 | 1 | 0 | 0              | 0              | 0              | 1              | 0              |
| 3  | 0 | 0 | 1 | 1 | 0              | 0              | 0              | 1              | 1              |
| 4  | 0 | 1 | 0 | 0 | 0              | 0              | 1              | 0              | 0              |
| 5  | 0 | 1 | 0 | 1 | 0              | 0              | 1              | 0              | 1              |
| 6  | 0 | 1 | 1 | 0 | 0              | 0              | 1              | 1              | 0              |
| 7  | 0 | 1 | 1 | 1 | 0              | 0              | 1              | 1              | 1              |
| 8  | 1 | 0 | 0 | 0 | 0              | 1              | 0              | 0              | 0              |
| 9  | 1 | 0 | 0 | 1 | →              | 0              | 1              | 0              | 1              |
| 10 | 1 | 0 | 1 | 0 | 1              | 0              | 0              | 0              | 0              |
| 11 | 1 | 0 | 1 | 1 | 1              | 0              | 0              | 0              | 1              |
| 12 | 1 | 1 | 0 | 0 | 1              | 0              | 0              | 1              | 0              |
| 13 | 1 | 1 | 0 | 1 | 1              | 0              | 0              | 1              | 1              |
| 14 | 1 | 1 | 1 | 0 | 1              | 0              | 1              | 0              | 0              |
| 15 | 1 | 1 | 1 | 1 | 1              | 0              | 1              | 0              | 1              |

0001115

|    |    | $B_4$ |    |     |     |
|----|----|-------|----|-----|-----|
|    |    | 00    | 01 | 11  | 10  |
| AB | CD | 1     |    |     |     |
| 00 |    |       |    |     |     |
| 01 |    | 1     | 1  | (1) | (1) |
| 11 |    |       |    |     |     |
| 10 |    |       |    |     |     |

$$= AB + AC$$

|    |    | $B_3$ |     |    |    |
|----|----|-------|-----|----|----|
|    |    | 00    | 01  | 11 | 10 |
| AB | CD | 1     |     |    |    |
| 00 |    |       |     |    |    |
| 01 |    |       |     |    |    |
| 11 |    |       |     |    |    |
| 10 |    | (1)   | (1) |    |    |

$$= A\bar{B}\bar{C}$$

|    |    | $B_2$ |    |     |     |
|----|----|-------|----|-----|-----|
|    |    | 00    | 01 | 11  | 10  |
| AB | CD | 1     |    |     |     |
| 00 |    | 1     | 1  | (1) | (1) |
| 01 |    |       |    |     |     |
| 11 |    |       |    |     |     |
| 10 |    |       |    |     |     |

|    |    | $B_1$ |     |    |    |
|----|----|-------|-----|----|----|
|    |    | 00    | 01  | 11 | 10 |
| AB | CD | 1     |     |    |    |
| 00 |    |       |     |    |    |
| 01 |    |       |     |    |    |
| 11 |    | (1)   | (1) |    |    |
| 10 |    |       |     |    |    |


$$= \bar{A}B\bar{C} + BC$$

$$AB\bar{C} + \bar{A}C$$

$B_4$

|    |    | $B_0$ |    |    |    |
|----|----|-------|----|----|----|
|    |    | 00    | 01 | 11 | 10 |
| AB | CD | 1     |    |    |    |
| 00 |    | 1     | 1  |    |    |
| 01 |    |       | 1  | 1  |    |
| 11 |    | 1     | 1  | 1  | 1  |
| 10 |    |       | 1  | 1  | 1  |

$$= D$$

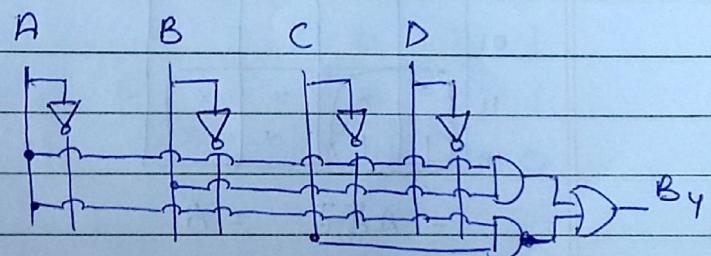

2

BCD to Binary

|   | A | B | C | D |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |

|   | $B_3$ | $B_2$ | $B_1$ | $B_0$ |
|---|-------|-------|-------|-------|
| 0 | 0     | 0     | 0     | 0     |
| 1 | 0     | 0     | 0     | 1     |
| 2 | 0     | 0     | 1     | 0     |
| 3 | 0     | 0     | 1     | 1     |

|    |   |   |   |   |
|----|---|---|---|---|
| 4  | 0 | 1 | 0 | 0 |
| 5  | 0 | 1 | 0 | 1 |
| 6  | 0 | 1 | 1 | 0 |
| 7  | 0 | 1 | 1 | 1 |
| 8  | 1 | 0 | 0 | 0 |
| 9  | 1 | 0 | 0 | 1 |
| 10 | x | x | x | x |
| 11 | x |   |   | x |
| 12 | x |   |   | x |
| 13 | x |   |   | x |
| 14 | x |   |   | x |
| 15 | x | x | x | x |

|   |   |   |   |
|---|---|---|---|
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| x | x | x | x |

 $B_3$ 

| AB | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 |    |    |    |    |    |
| 01 |    |    |    |    |    |
| 11 |    | x  | x  | x  | x  |
| 10 |    | 1  | 1  | x  | x  |

$$= A \# B = A$$

 $B_2$ 

| AB | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 |    |    |    |    |    |
| 01 |    |    |    |    |    |
| 11 |    | 1  | 1  | 1  | 1  |
| 10 |    | x  | x  | x  | x  |

$$= B$$

# Binary to Gray / Reflected Code / Unit Distance Code

| A | B | C | D | $q_3$                      | $q_2$ | $q_1$ | $q_0$ | $q_3$ | $q_2$ | $q_1$ | $q_0$ |
|---|---|---|---|----------------------------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | A.                         | $A+B$ | $B+C$ | $C+D$ | 0     | 0     | 0     | 0     |
| 0 | 0 | 0 | 1 |                            |       |       |       | 0     | 0     | 0     | 1     |
| 0 | 0 | 1 | 0 | Here in                    |       |       |       | 0     | 0     | 1     | 1     |
| 0 | 0 | 1 | 1 | $1+1=10$                   |       |       |       | 0     | 0     | 1     | 0     |
| 0 | 1 | 0 | 0 | $\therefore 0$ is taken by |       |       |       | 0     | 1     | 1     | 0     |
| 0 | 1 | 0 | 1 | 1 is rejected              |       |       |       | 0     | 1     | 1     | 1     |
| 0 | 1 | 1 | 0 |                            |       |       |       | 0     | 1     | 0     | 1     |
| 0 | 1 | 1 | 1 |                            |       |       |       | 0     | 1     | 0     | 0     |
| 1 | 0 | 0 | 0 |                            |       |       |       | 1     | 1     | 0     | 0     |
| 1 | 0 | 0 | 1 |                            |       |       |       | 1     | 1     | 0     | 1     |
| 1 | 0 | 1 | 0 |                            |       |       |       | 1     | 1     | 1     | 1     |
| 1 | 0 | 1 | 1 |                            |       |       |       | 1     | 1     | 1     | 0     |
| 1 | 1 | 0 | 0 |                            |       |       |       | 1     | 0     | 1     | 0     |
| 1 | 1 | 0 | 1 |                            |       |       |       | 1     | 0     | 1     | 1     |
| 1 | 1 | 1 | 0 |                            |       |       |       | 1     | 0     | 0     | 1     |
| 1 | 1 | 1 | 1 |                            |       |       |       | 1     | 0     | 0     | 0     |

| $q_3$ | $AB \setminus CD$ | w | or | u | v |
|-------|-------------------|---|----|---|---|
| 00    |                   |   |    |   |   |
| 01    |                   |   |    |   |   |
| 11    | (1 1 1 1)         |   |    |   |   |
| 10    | (1 1 1 1)         |   |    |   |   |

$= A$

| $q_2$ | $AB \setminus CD$ | w | or | u | v |
|-------|-------------------|---|----|---|---|
| 00    |                   |   |    |   |   |
| 01    | (1 1 1 1)         |   |    |   |   |
| 11    |                   |   |    |   |   |
| 10    | (1 1 1 1)         |   |    |   |   |

$= \bar{A}B + A\bar{B}$        $A \oplus B$

| $q_1$ | $AB \setminus CD$ | w | or | u | v |
|-------|-------------------|---|----|---|---|
| 00    |                   |   |    |   |   |
| 01    | (1 1 1 1)         |   |    |   |   |
| 11    | (1 1 1 1)         |   |    |   |   |
| 10    | (1 1 1 1)         |   |    |   |   |

$= BC + \bar{B}\bar{C}$

$\bar{B}C$

$B \oplus C$

| $q_0$ | $AB \setminus CD$ | w | or | u | v |
|-------|-------------------|---|----|---|---|
| 00    |                   |   |    |   |   |
| 01    |                   |   |    |   |   |
| 11    |                   |   |    |   |   |
| 10    |                   |   |    |   |   |

$= \bar{C}D + \bar{C}\bar{D}$

$C \oplus D$

## Gray to Binary

| $G_3$ | $G_2$ | $G_1$ | $G_0$ | $(G_3 + G_2 + G_1 + G_0)$ |
|-------|-------|-------|-------|---------------------------|
| 0     | 0     | 0     | 0     | 0000                      |
| 0     | 0     | 0     | 1     | 0001                      |
| 0     | 0     | 1     | 0     | 0011                      |
| 0     | 0     | 1     | 1     | 0010                      |
| 0     | 1     | 0     | 0     | 0111                      |
| 0     | 1     | 0     | 1     | 0110                      |
| 0     | 1     | 1     | 0     | 0100                      |
| 0     | 1     | 1     | 1     | 0101                      |
| 1     | 0     | 0     | 0     | 1111                      |
| 1     | 0     | 0     | 1     | 1110                      |
| 1     | 0     | 1     | 0     | 1100                      |
| 1     | 0     | 1     | 1     | 1101                      |
| 1     | 1     | 0     | 0     | 1000                      |
| 1     | 1     | 0     | 1     | 1001                      |
| 1     | 1     | 1     | 0     | 1011                      |
| 1     | 1     | 1     | 1     | 1010                      |

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 |

| $G_3$ | $G_2$ | $G_1$ | $G_0$ |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     |
| 0     | 0     | 0     | 1     |
| 0     | 0     | 1     | 1     |
| 0     | 0     | 1     | 0     |
| 1     | 1     | 1     | 1     |
| 1     | 1     | 1     | 0     |
| 1     | 1     | 0     | 1     |
| 1     | 1     | 0     | 0     |
| 1     | 0     | 0     | 0     |
| 1     | 0     | 0     | 1     |
| 1     | 0     | 1     | 0     |
| 1     | 0     | 1     | 1     |
| 1     | 0     | 1     | 0     |

$$= A \bar{G}_3$$

=

| $\bar{G}_3 \oplus G_2 \oplus G_1$ | $G_3 \bar{G}_2 \bar{G}_1$ | $G_3 \bar{G}_2 G_1$ | $\bar{G}_3 G_2 \bar{G}_1$ | $\bar{G}_3 G_2 G_1$ |
|-----------------------------------|---------------------------|---------------------|---------------------------|---------------------|
| 0                                 | 0                         | 0                   | 0                         | 0                   |
| 0                                 | 0                         | 0                   | 1                         | 1                   |
| 0                                 | 0                         | 1                   | 1                         | 0                   |
| 0                                 | 0                         | 1                   | 0                         | 1                   |
| 1                                 | 1                         | 1                   | 1                         | 0                   |
| 1                                 | 1                         | 1                   | 0                         | 1                   |
| 1                                 | 1                         | 0                   | 1                         | 0                   |
| 1                                 | 1                         | 0                   | 0                         | 1                   |
| 1                                 | 0                         | 0                   | 0                         | 0                   |
| 1                                 | 0                         | 0                   | 1                         | 1                   |
| 1                                 | 0                         | 1                   | 0                         | 0                   |
| 1                                 | 0                         | 1                   | 1                         | 1                   |
| 1                                 | 0                         | 1                   | 0                         | 0                   |

$$= \bar{G}_3 G_2 + G_3 \bar{G}_2$$

| $G_3$ | $G_2$ | $G_1$ | $G_0$ |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     |
| 0     | 0     | 0     | 1     |
| 0     | 0     | 1     | 1     |
| 0     | 0     | 1     | 0     |
| 1     | 1     | 1     | 1     |
| 1     | 1     | 1     | 0     |
| 1     | 1     | 0     | 1     |
| 1     | 1     | 0     | 0     |
| 1     | 0     | 0     | 0     |
| 1     | 0     | 0     | 1     |
| 1     | 0     | 1     | 0     |
| 1     | 0     | 1     | 1     |
| 1     | 0     | 1     | 0     |

| $G_3$ | $G_2$ | $G_1$ | $G_0$ |
|-------|-------|-------|-------|
| 0     | 1     | 1     | 1     |
| 0     | 1     | 1     | 0     |
| 0     | 1     | 0     | 1     |
| 0     | 1     | 0     | 0     |
| 1     | 1     | 1     | 1     |
| 1     | 1     | 0     | 1     |
| 1     | 0     | 1     | 1     |
| 1     | 0     | 1     | 0     |

BCD to Excess-3

|    | A | B | C | D |           | E <sub>3</sub> | E <sub>2</sub> | E <sub>1</sub> | E <sub>0</sub> |
|----|---|---|---|---|-----------|----------------|----------------|----------------|----------------|
| 0  | 0 | 0 | 0 | 0 | 0+3 →     | 0              | 0              | 1              | 1              |
| 1  | 0 | 0 | 0 | 1 | 1+3 →     | 0              | 1              | 0              | 0              |
| 2  | 0 | 0 | 1 | 0 | 2+3 →     | 0              | 1              | 0              | 1              |
| 3  | 0 | 0 | 1 | 1 |           | 0              | 1              | 1              | 0              |
| 4  | 0 | 1 | 0 | 0 |           | 0              | 1              | 1              | 1              |
| 5  | 0 | 1 | 0 | 1 |           | 1              | 0              | 0              | 0              |
| 6  | 0 | 1 | 1 | 0 |           | 1              | 0              | 0              | 1              |
| 7  | 0 | 1 | 1 | 1 |           | 1              | 0              | 1              | 0              |
| 8  | 1 | 0 | 0 | 0 |           | 1              | 0              | 1              | 1              |
| 9  | 1 | 0 | 0 | 1 |           | 1              | 1              | 0              | 0              |
| 10 | 1 | 0 | 1 | 0 | → 10 → 43 | *              | *              | *              | *              |
| 11 | 1 | 0 | 1 | 1 | .         | *              | *              | *              | 0              |
| 12 | 1 | 1 | 0 | 0 | .         | *              | *              | *              | *              |
| 13 | 1 | 1 | 0 | 1 | .         | X              | X              | X              | X              |
| 14 | 1 | 1 | 1 | 0 | .         | X              | X              | X              | X              |
| 15 | 1 | 1 | 1 | 1 | .         | X              | X              | X              | X              |

| AB |    | CD |    | E <sub>3</sub> |    |    |    |
|----|----|----|----|----------------|----|----|----|
| 00 | 01 | 11 | 10 | 00             | 01 | 11 | 10 |
| 00 |    |    |    |                |    |    |    |
| 01 |    |    |    | 1              | 1  | 1  |    |
| 11 |    |    |    | X              | X  | X  | X  |
| 10 |    |    |    | 1              | 1  | X  | X  |
|    |    |    |    | X              | X  | X  | X  |

$$= A + BC + BD$$

| AB |    | CD |    | E <sub>2</sub> |    |    |    |
|----|----|----|----|----------------|----|----|----|
| 00 | 01 | 11 | 10 | 00             | 01 | 11 | 10 |
| 00 |    |    |    |                |    |    |    |
| 01 |    |    |    | 1              |    |    |    |
| 11 |    |    |    | X              |    |    |    |
| 10 |    |    |    | 1              | 1  | X  | X  |
|    |    |    |    | X              | X  | X  | X  |

$$= \overline{B} \overline{C} \overline{D} + \overline{B} D + \overline{B} C$$

| AB |    | CD |    | E <sub>1</sub> |    |    |    |
|----|----|----|----|----------------|----|----|----|
| 00 | 01 | 11 | 10 | 00             | 01 | 11 | 10 |
| 00 |    |    |    | 1              |    |    |    |
| 01 |    |    |    | 1              |    |    |    |
| 11 |    |    |    | X              | X  | X  | X  |
| 10 |    |    |    | 1              | 1  | X  | X  |
|    |    |    |    | X              | X  | X  | X  |

$$= \overline{C} \overline{D} + CD$$

| AB |    | CD |    | D  |    |    |    |
|----|----|----|----|----|----|----|----|
| 00 | 01 | 11 | 10 | 00 | 01 | 11 | 10 |
| 00 |    |    |    | 1  |    |    |    |
| 01 |    |    |    | 1  |    |    |    |
| 11 |    |    |    | X  |    |    |    |
| 10 |    |    |    | 1  | 1  | X  | X  |
|    |    |    |    | X  | X  | X  | X  |

$$= \overline{D}$$

Self Complementing

Date \_\_\_\_\_  
Page \_\_\_\_\_

Excess - 3 to BCD

| $E_3$ | $E_2$ | $E_1$ | $E_0$ |                                   | A1 | B | C | D |
|-------|-------|-------|-------|-----------------------------------|----|---|---|---|
| 0     | 0     | 1     | 1     | 0, 1, 2, 13, 14, 15               | 0  | 0 | 0 | 0 |
| 0     | 1     | 0     | 0     |                                   | 0  | 0 | 0 | 1 |
| 0     | 1     | 0     | 1     | Don't care                        | 0  | 0 | 1 | 6 |
| 0     | 1     | 1     | 0     | as in Excess-3                    | 0  | 0 | 1 | 1 |
| 0     | 1     | 1     | 1     | it starts with 3 and ends with 12 | 0  | 1 | 6 | 0 |
| 1     | 0     | 0     | 0     |                                   | 0  | 1 | 0 | 1 |
| 1     | 0     | 1     | 0     |                                   | 0  | 1 | 1 | 1 |
| 1     | 0     | 1     | 1     |                                   | 1  | 0 | 0 | 0 |
| 1     | 1     | 0     | 0     |                                   | 1  | 0 | 0 | 1 |

| $E_3$ | $E_2$ | $E_1$ | $E_0$ |  |
|-------|-------|-------|-------|--|
| 00    | x     | x     |       |  |
| 01    |       |       |       |  |
| 11    | 1     | x     | x     |  |
| 10    | .     | .     | 1     |  |

$$= E_3 E_2 + E_3 E_1 E_0$$

| $E_3$ | $E_2$ | $E_1$ | $E_0$ |  |
|-------|-------|-------|-------|--|
| 00    | x     | x     |       |  |
| 01    |       |       |       |  |
| 11    | (x)   | x     |       |  |
| 10    |       |       | 1     |  |

$$\begin{aligned}
 &= \bar{E}_2 \bar{E}_0 \\
 &+ E_2 E_1 E_0 \\
 &+ \bar{E}_2 \bar{E}_1 = \bar{E} \bar{E}_2 + E_2 C_1 E_0 \rightarrow E_3 E_1 \bar{E}_0
 \end{aligned}$$

| $E_3$ | $E_2$ | $E_1$ | $E_0$ |  |
|-------|-------|-------|-------|--|
| 00    | x     | (x)   | x     |  |
| 01    |       | 1     | 1     |  |
| 11    | x     | x     | x     |  |
| 10    | 1     | 1     | 1     |  |

$$= E_1 \bar{E}_0 + E_0 \bar{E}_1$$

| $E_3$ | $E_2$ | $E_1$ | $E_0$ |  |
|-------|-------|-------|-------|--|
| 00    | x     | x     |       |  |
| 01    |       |       |       |  |
| 11    | 1     |       | x     |  |
| 10    | 1     | 1     | x     |  |

$$= \bar{E}_0$$

## Registers

### Arrangement of Flip Flops

1 flip flop stores 1 bit

$1001 \rightarrow$  4-bit register

a) on the basis of data movement

- right shift
- left shift
- bidirectional

b) on the basis of mode selection

SISO → Serial In Serial Out


SIPOL → Serial In Parallel Out

PIPO


PISO

Universal

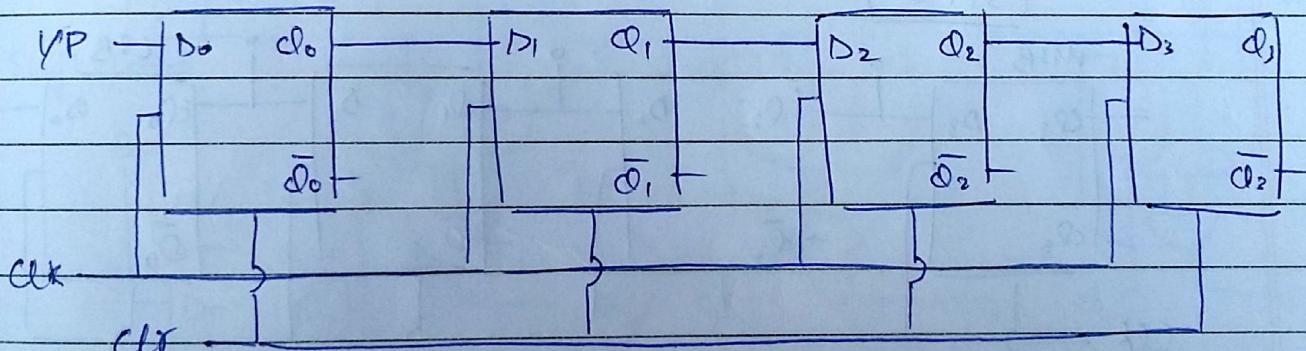\* 4-bit  $\rightarrow$  [SISO] : Right Shift Register [in D flip flop  $YP = O/P$ ] LSB



To store 1001

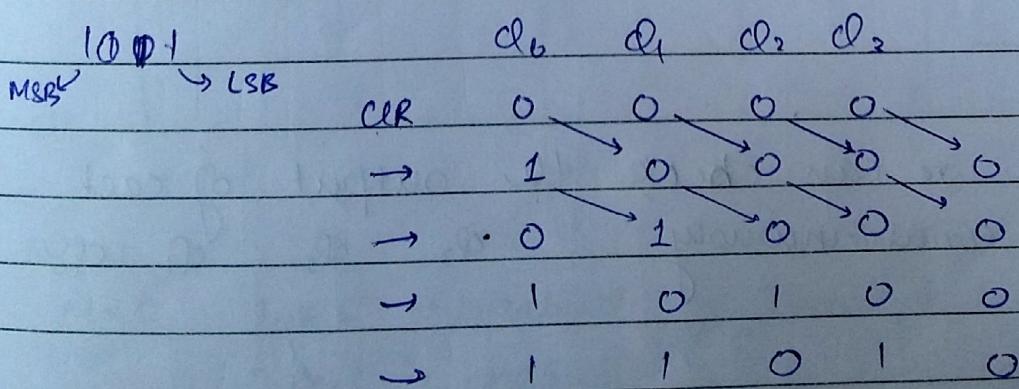


Here, first we give LSB as input

Asynchronous : clock  
Proc w/ clr(reset)

Date \_\_\_\_\_  
Page \_\_\_\_\_

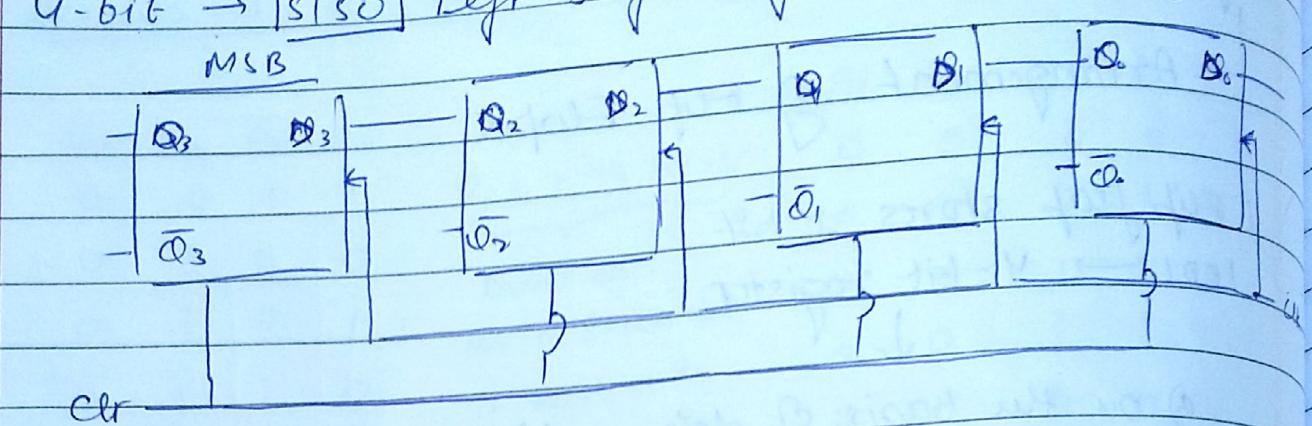4-bit  $\rightarrow$  [SISO] Left shift Register




| MSB | LSB | Clk <sub>3</sub> | Clk <sub>2</sub> | Clk <sub>1</sub> | Clk <sub>0</sub> | Q <sub>0</sub> | clr |
|-----|-----|------------------|------------------|------------------|------------------|----------------|-----|
| 1   | 0   | 1                | 0                | 0                | 0                | 0              | 0   |
| 0   | 0   | 0                | 1                | 0                | 0                | 0              | 0   |
| 0   | 0   | 0                | 0                | 1                | 0                | 0              | 0   |
| 0   | 1   | 0                | 0                | 0                | 1                | 0              | 0   |
| 1   | 0   | 1                | 1                | 0                | 0                | 1              | 0   |

Here first we  
give MSB as IP


\*

[SIPO]

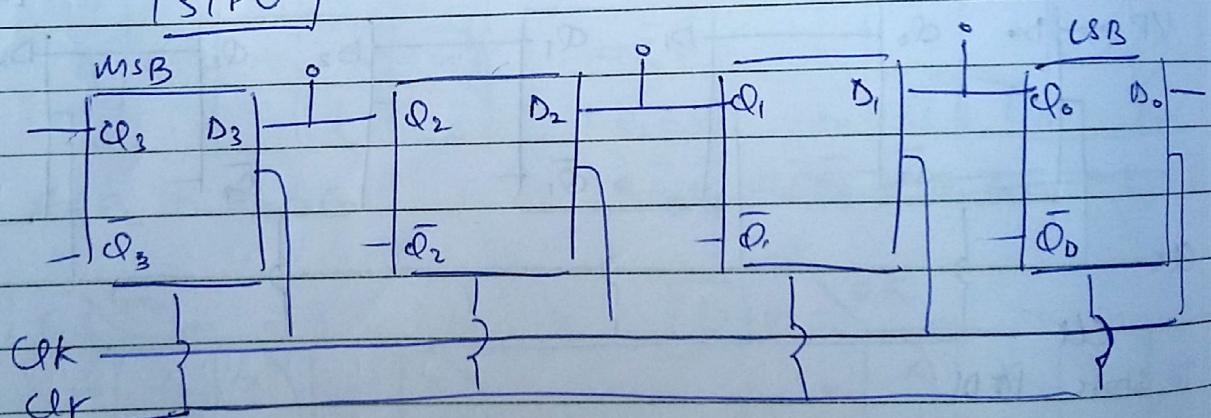


In this we can check the output of each  
block simultaneously

Clk<sub>3</sub> Clk<sub>2</sub> Clk<sub>1</sub> Clk<sub>0</sub>

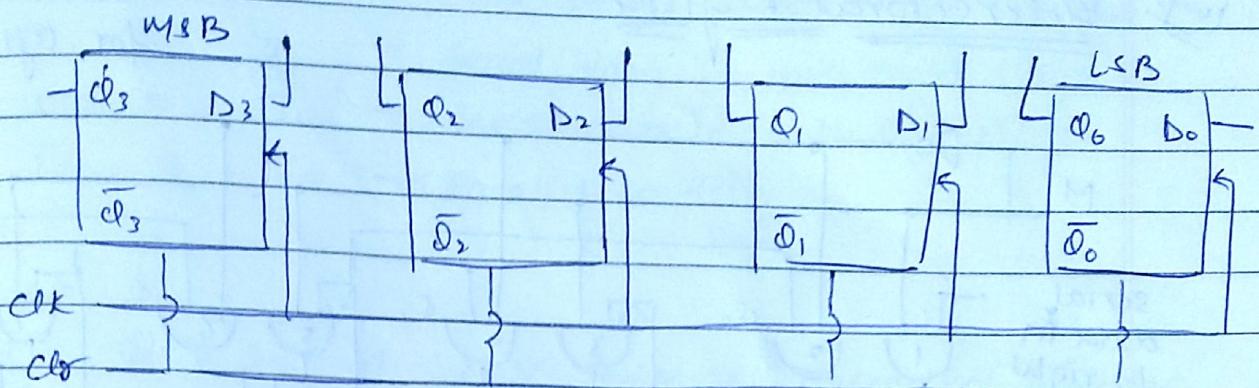IPIO

|       |                |                |                |                |     |
|-------|----------------|----------------|----------------|----------------|-----|
| (011) | D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> |     |
|       | 0              | 0              | 0              | 0              | clr |
|       | 1              | 0              | 1              | 1              |     |

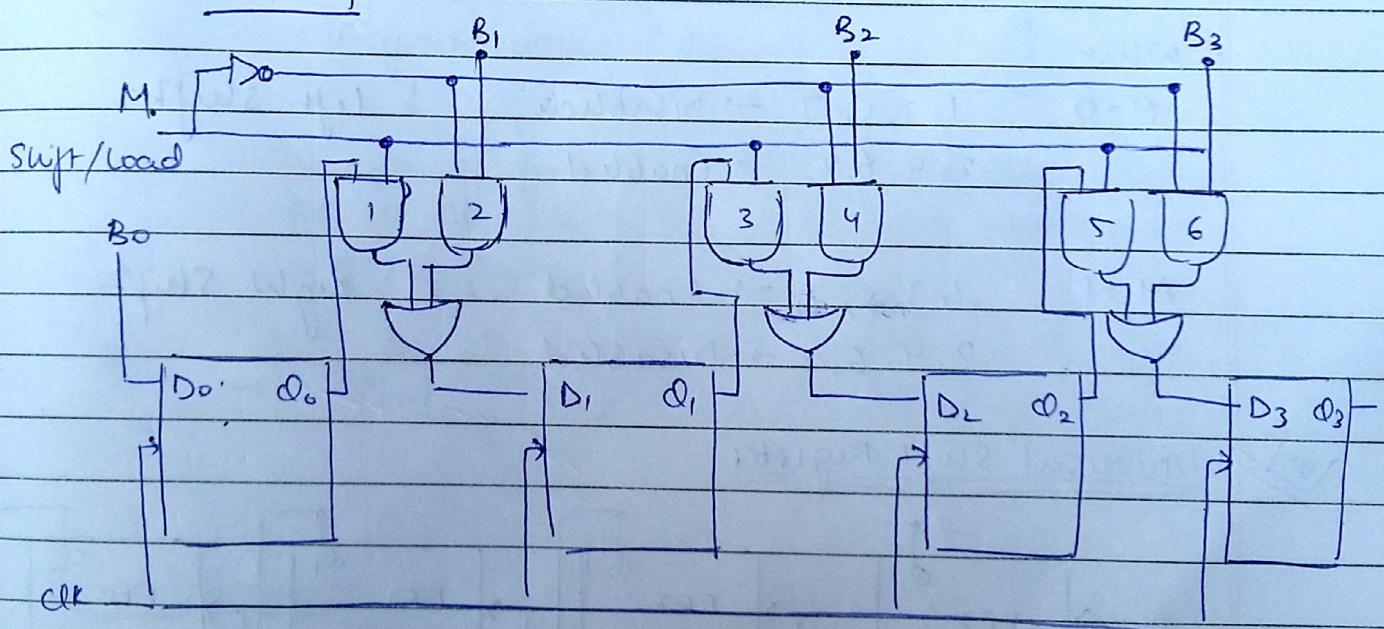PISO

When

M=0      1,3,5 → disabled  
2,4,6 → enabled

Parallel loading


M=1      1,3,5 → enabled  
2,4,6 → disabled

Right shift / left shift

Biecto

## Bi-directional Register

serial data in  
for left shift

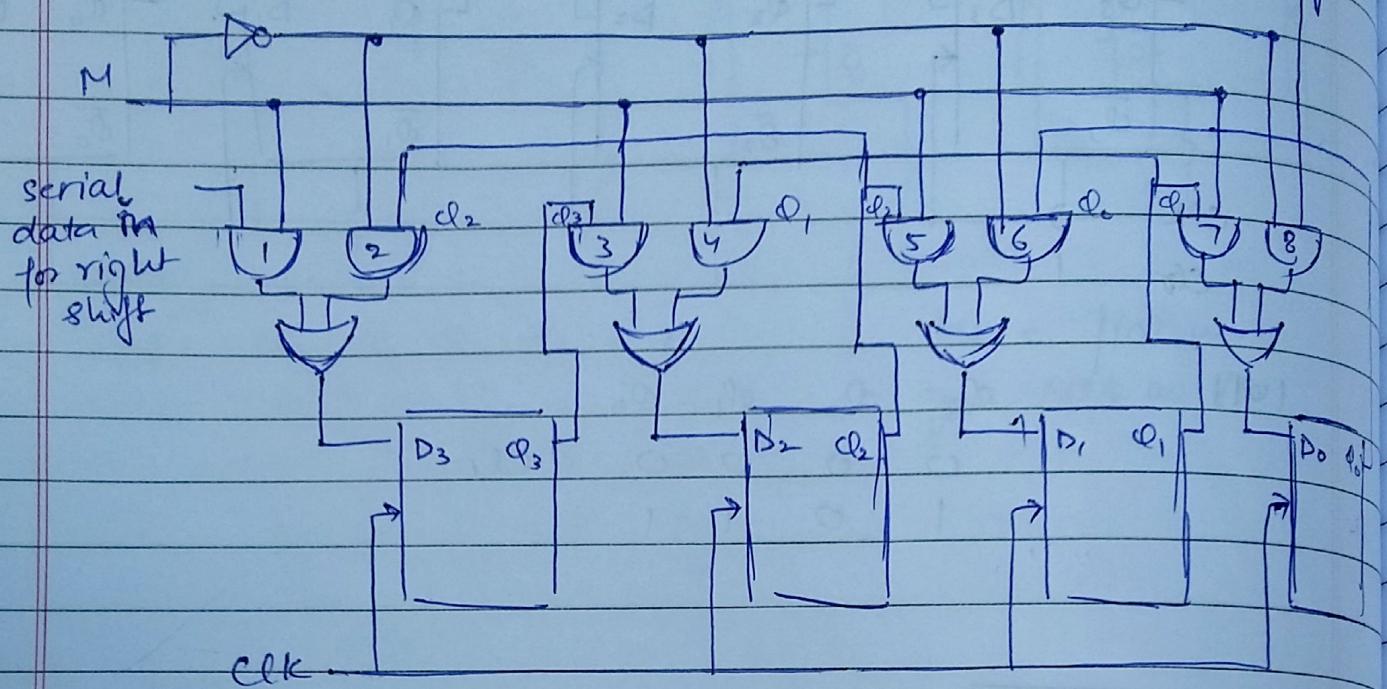


When

$M = 0$        $1, 3, 5, 7 \rightarrow$  Disabled      Left shift.  
 $2, 4, 6, 8 \rightarrow$  Enabled

$M = 1$        $1, 3, 5, 7 \rightarrow$  Enabled      Right shift  
 $2, 4, 6, 8 \rightarrow$  Disabled

## Universal Shift Register

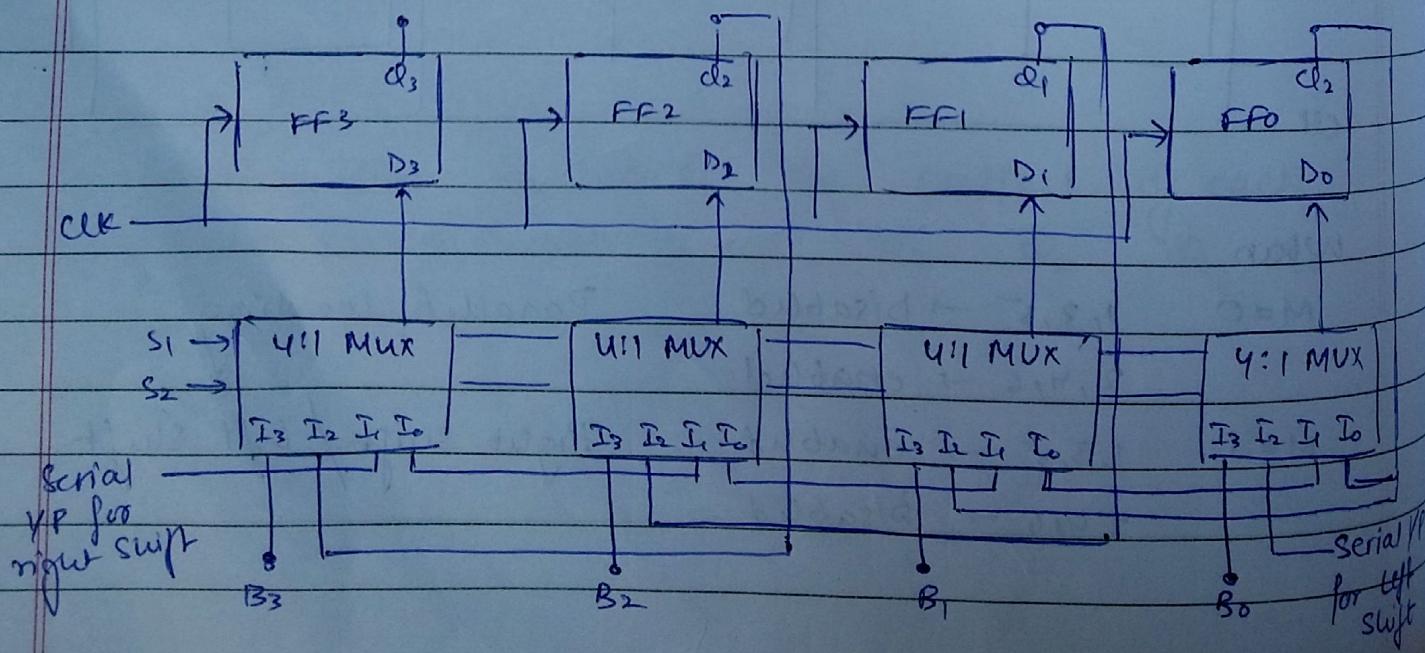

$S_2 \quad S_1 \quad Y$

- $0 \quad 0 \quad I_0 \rightarrow$  Hold state (holds the last output)
- $0 \quad 1 \quad I_1 \rightarrow$  Serial data in with right shift
- $1 \quad 0 \quad I_2 \rightarrow$  Serial data in with left shift
- $1 \quad 1 \quad I_3 \rightarrow$  Parallel loading

Test: Q-N Method, MUX, DEMUX, Decoder, Encoder  
Comparator, code converter

### Counters

Counts the no. of clk. pulses arriving at the ckt.



Types → Synchronous (Parallel) ——————

Asynchronous (Ripple)




The o/p of present flip flop is clk pulse for 2nd flip flop

The clk. impulse is synchronised

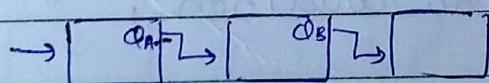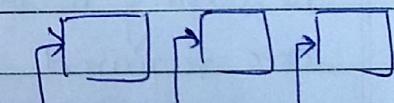

### State Diagram

I/P  $\Rightarrow$  O/P

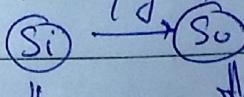

Present state

Next state

$S_2 \quad S_1 \quad Y$

- 0 0  $I_0 \rightarrow$  Hold state (holds the last output)
- 0 1  $I_1 \rightarrow$  Serial data in with right shift
- 1 0  $I_2 \rightarrow$  Serial data in with left shift
- 1 1  $I_3 \rightarrow$  Parallel loading

Test: Q-N Method, MUX, DEMUX, Decoder, Encoder  
Comparator, code converter

### Counters

Counts the no. of clk. pulses arriving at the ckt.



Types  $\rightarrow$  Synchronous (Parallel)  $\longrightarrow$

Asynchronous (Ripple)




The o/p of present flip flop is clk pulse for 2nd flip flop

The clk. impulse is synchronised

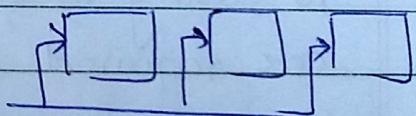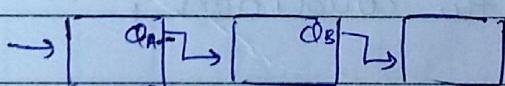

### State Diagram

I/P x/y O/P

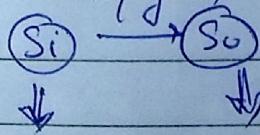


Present state

Next state

→  
+ve  
clk pulse      →  
-ve  
clk pulse

For 2 bit

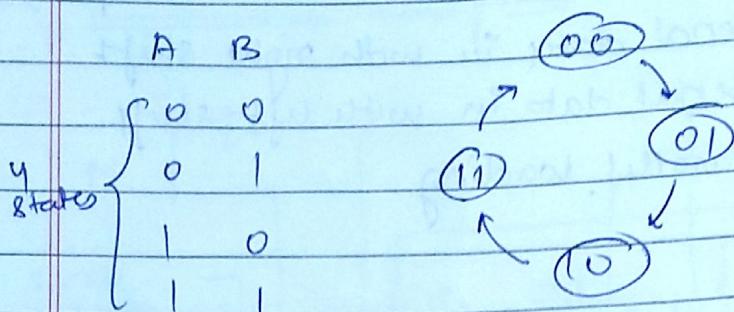

State Table

| P.S. | N.S. | F/F D/P |
|------|------|---------|
| 00   | 01   |         |
| 01   | 10   |         |
| 10   | 11   |         |
| 11   | 00   |         |

MOD Number : Counts the no. of states

~~clock~~

$$\boxed{2^n \geq N} \text{ — CONDITION}$$


no. of bits/flip flop


To design a MOD 'N' counter, 'n' no. of flip flops are required through the condition.

### Asynchronous Counters

Up-counter : inc. order

Down counter : dec. order

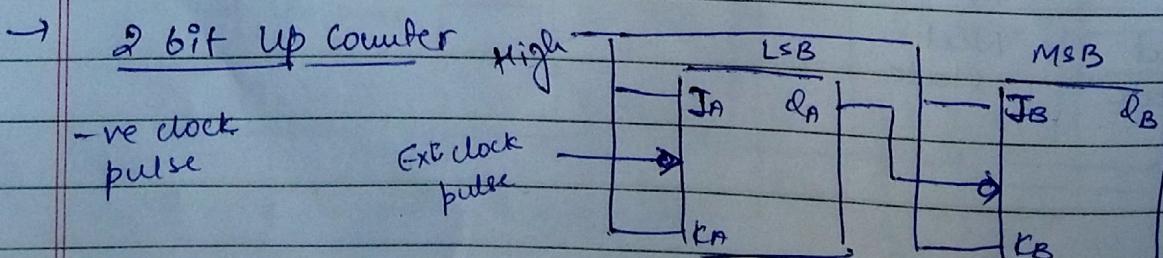

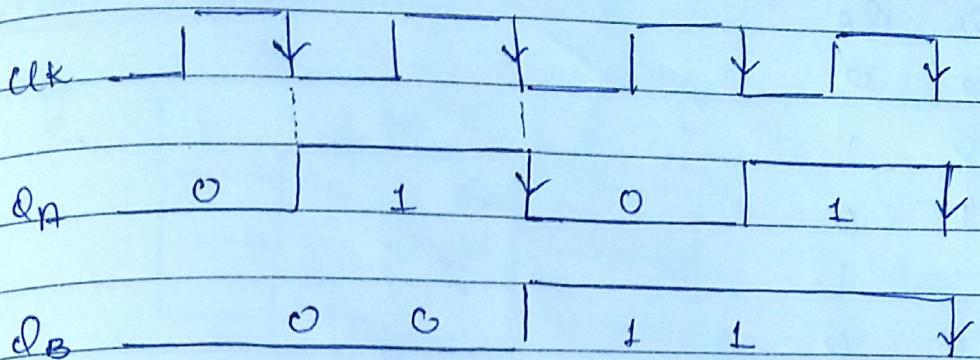

MSB LCB



$Q_B$        $Q_A$

0 1

1      0

1 1


→ 3-bit up counter

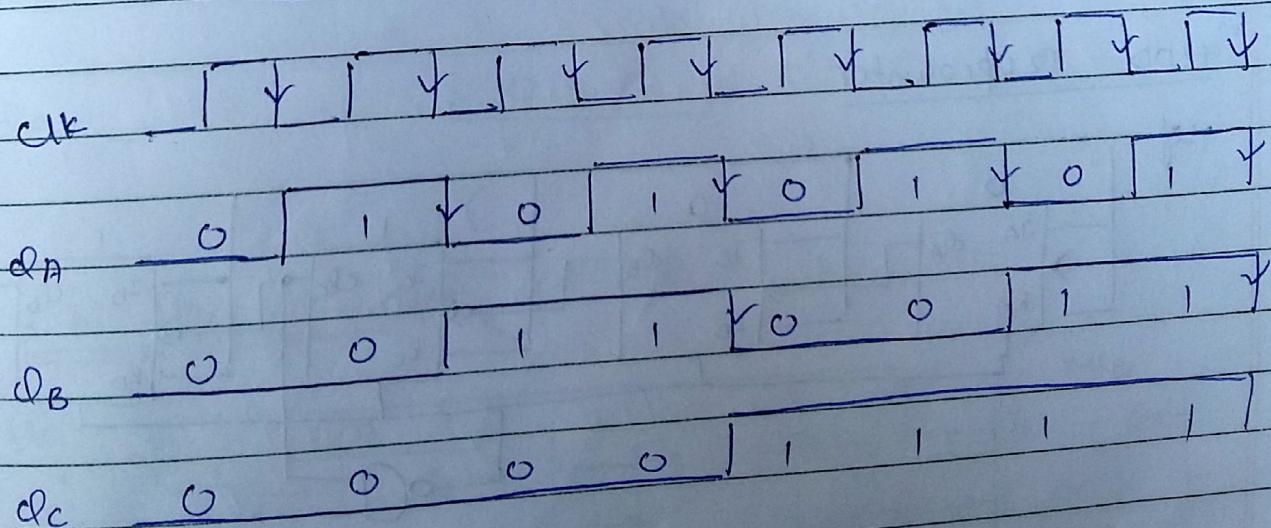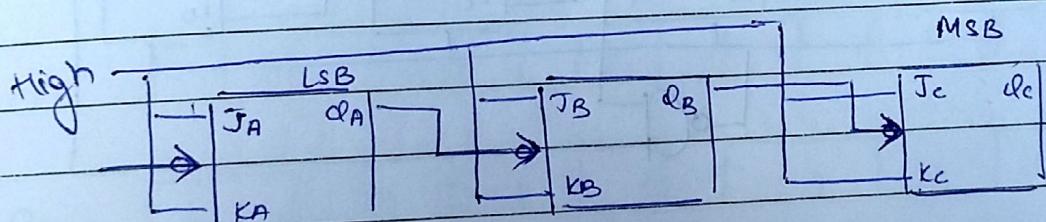


| $Q_C$ | $Q_B$ | $Q_A$ |
|-------|-------|-------|
| 0     | 0     | 0     |
| 0     | 0     | 1     |
| 0     | 1     | 0     |
| 0     | 1     | 1     |
| 1     | 0     | 0     |
| 1     | 0     | 1     |
| 1     | 1     | 0     |
| 1     | 1     | 1     |

4-bit up counter


\* MOD 10 upcounter

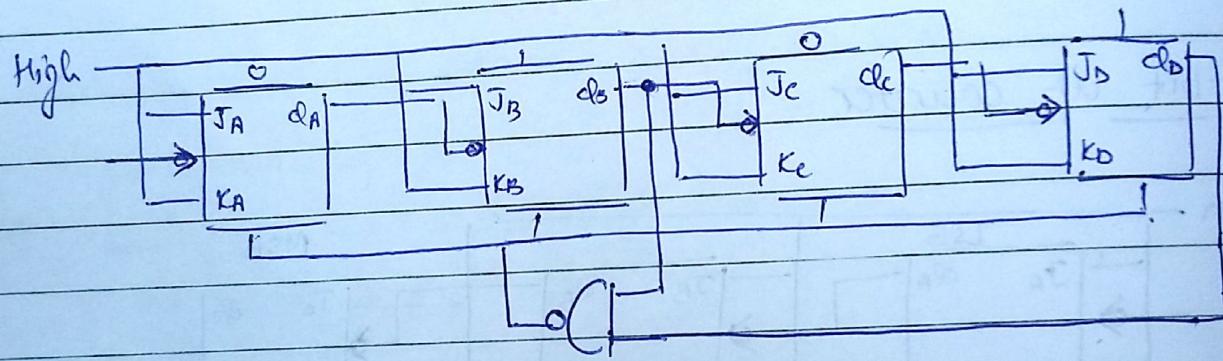


MOD 12 Upcounter

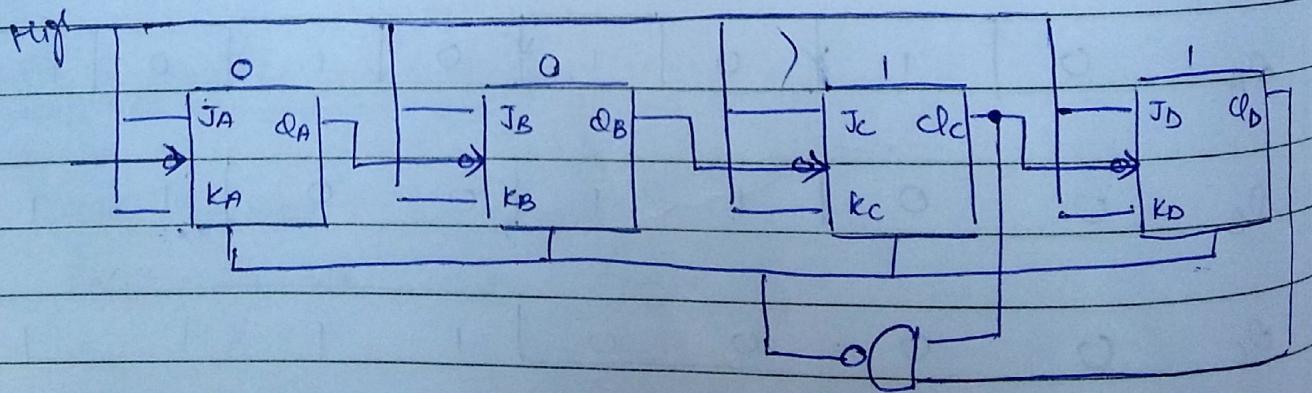

## MOS 54Counter

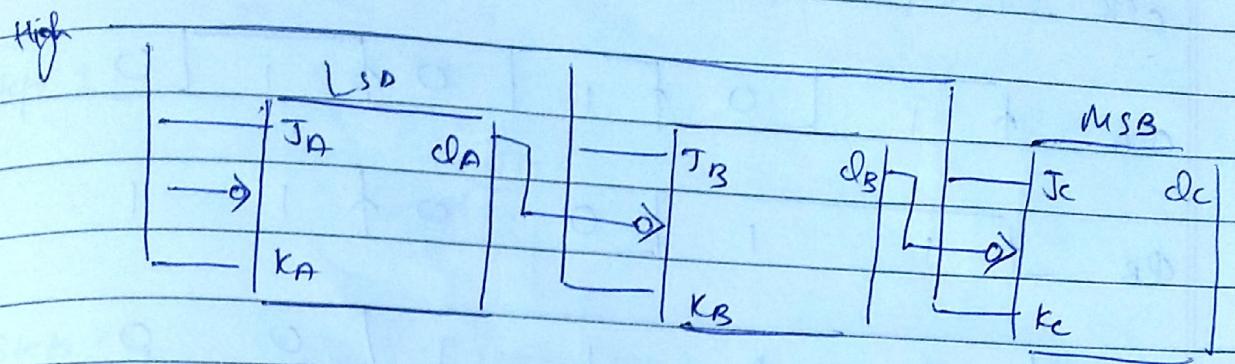

## 2 bit Down Counter

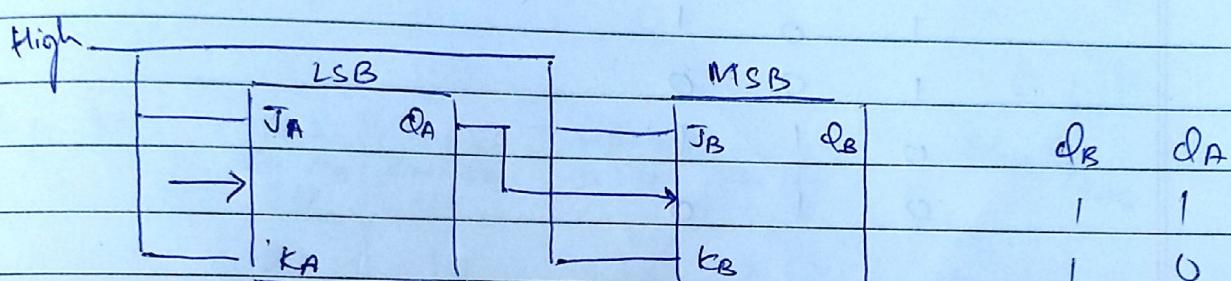


cek t t f f t t f t t

Qn ↑ T L O F.1 6 F.1 L O T.1 1 0

$$Q_B = \boxed{1} \quad \boxed{1} \quad \boxed{2} \quad \boxed{2} \quad \boxed{1} \quad \boxed{1} \quad \boxed{0}$$

## 3 bit Down Counter (MOD 8)

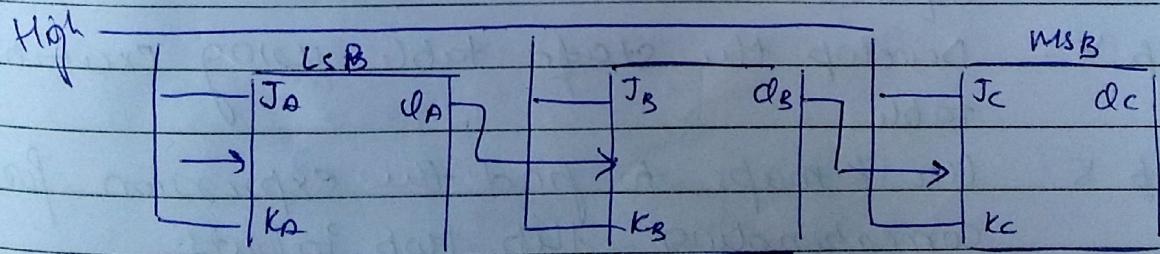

clk  $\rightarrow$   |  +  |  +  +  |

clap, tap, [off], off, [off]

Q.B. At 1 1 | 0 0 At 1 1

Q Q Q Q Q Q Q Q Q Q

| $\vec{z}$ | $\partial_c$ | $\partial_n$ | $\partial_a$ |
|-----------|--------------|--------------|--------------|
| $\vec{x}$ | 1            | 1            | 1            |
| 0         | 1            | 1            | 0            |
| 1         | 0            | 1            | 1            |
| 1         | 0            | 0            | 0            |
| 0         | 1            | 1            | 1            |
| 0         | 1            | 0            | 0            |

## Synchronous Counter

## Step 1: Design procedure

Step 1: Obtain the state diagram from the given information

Step 2: Determine the no. of flip flops required

Step 3 : Write the excitation table of flip flops required


Step 4: Develop the state table using excitation table

Step 5: Use K-maps to find the expression for corresponding flip flop inputs

Step 6: Draw the counter ckt. using flip flops and required gates

# MOD-4 counter - 2bit (up-counter)

Step 1:

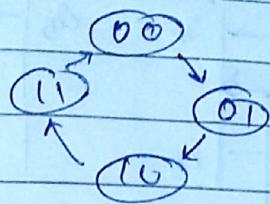

Step 2:  $n=2$  (using JK)


Step 3:  $J_n \ Q_{n+1} \ J \ K$

|   |   |   |   |
|---|---|---|---|
| 0 | 0 | 0 | x |
| 0 | 1 | 1 | x |
| 1 | 0 | x | 1 |
| 1 | 1 | x | 0 |


Step 4:

| P.S.                                | N.S.                                      | FF. UP                                     | State Table |
|-------------------------------------|---|--|-------------|
| Q <sub>A</sub> Q <sub>B</sub><br>00 | Q <sub>A</sub> +1 Q <sub>B</sub> +1<br>01 | J <sub>A</sub> K <sub>A</sub><br>0 X   1 X |             |
| 01                                  | 10  | 1 X   X 1                                  |             |
| 10                                  | 11  | X 0   1 X                                  |             |
| 11                                  | 00  | X 1   X 1                                  |             |


Step 5:

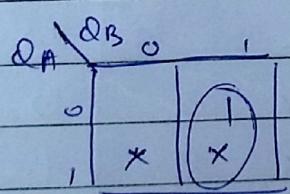


$$J_A = Q_B$$

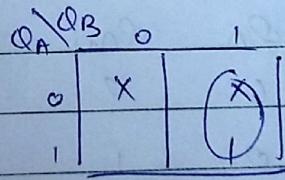


$$K_A = \bar{Q}_B$$

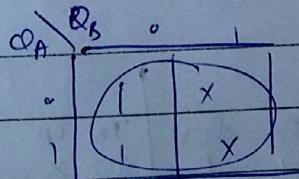

$$J_B = 1$$

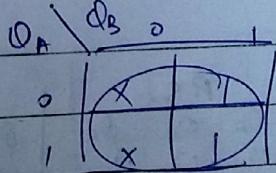


$$K_B = 1$$

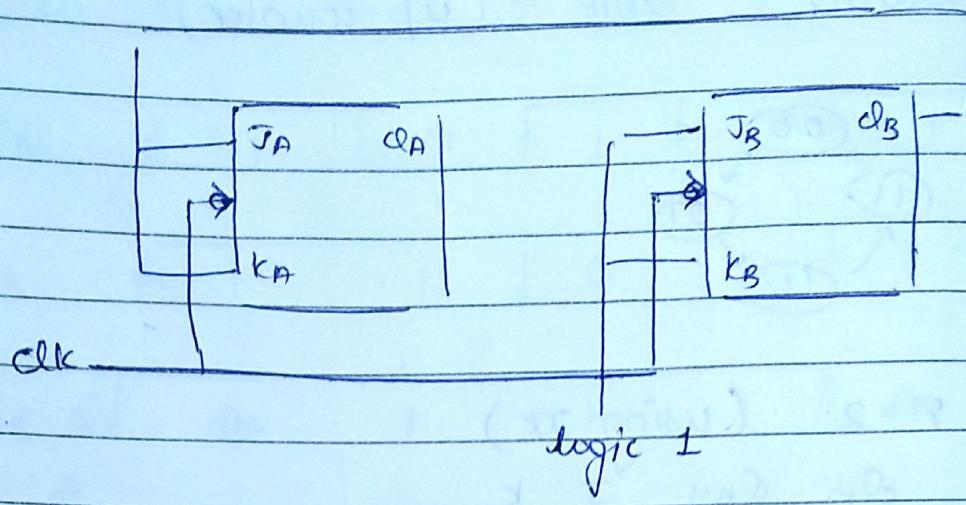

3 bit up counter

Step 1:

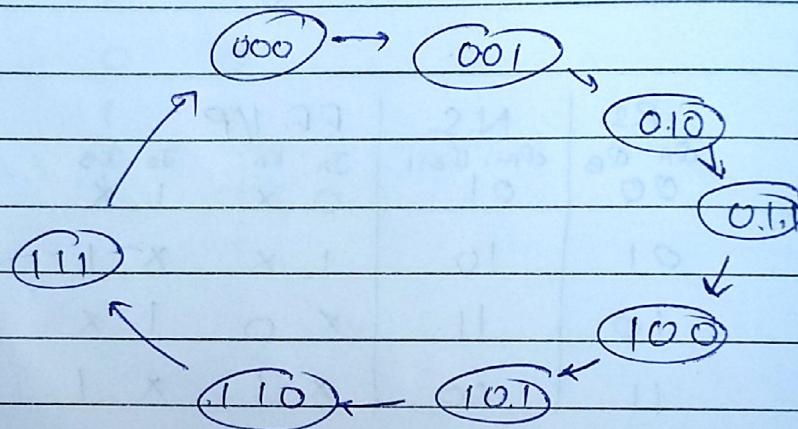

Step 2:  $n = 3$  (JK)

Step 3:  $Q_n \quad Q_{n+1} \quad J \quad K$

|   |   |   |   |
|---|---|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

Step 4:

P.S.

| $Q_A$ | $Q_B$ | $Q_C$ |
|-------|-------|-------|
| 0     | 0     | 0     |

NS

| $Q_{A+1}$ | $Q_{B+1}$ | $Q_{C+1}$ |
|-----------|-----------|-----------|
| 0         | 0         | 1         |

| $J_A$ | $K_A$ | $J_B$ | $K_B$ | $J_C$ | $K_C$ |
|-------|-------|-------|-------|-------|-------|
| 0     | X     | 0     | X     | 1     | X     |

| $Q_A$ | $Q_B$ | $Q_C$ |
|-------|-------|-------|
| 0     | 0     | 1     |

| $Q_{A+1}$ | $Q_{B+1}$ | $Q_{C+1}$ |
|-----------|-----------|-----------|
| 0         | 1         | 0         |

| $J_A$ | $K_A$ | $J_B$ | $K_B$ | $J_C$ | $K_C$ |
|-------|-------|-------|-------|-------|-------|
| 0     | X     | 1     | X     | X     | 1     |

| $Q_A$ | $Q_B$ | $Q_C$ |
|-------|-------|-------|
| 0     | 1     | 0     |

| $Q_{A+1}$ | $Q_{B+1}$ | $Q_{C+1}$ |
|-----------|-----------|-----------|
| 0         | 1         | 1         |

| $J_A$ | $K_A$ | $J_B$ | $K_B$ | $J_C$ | $K_C$ |
|-------|-------|-------|-------|-------|-------|
| 0     | X     | X     | 0     | 1     | X     |

| $Q_A$ | $Q_B$ | $Q_C$ |
|-------|-------|-------|
| 0     | 1     | 1     |

| $Q_{A+1}$ | $Q_{B+1}$ | $Q_{C+1}$ |
|-----------|-----------|-----------|
| 1         | 0         | 0         |

| $J_A$ | $K_A$ | $J_B$ | $K_B$ | $J_C$ | $K_C$ |
|-------|-------|-------|-------|-------|-------|
| 1     | X     | X     | 1     | X     | 1     |

|   |   |   |  |   |   |   |  |   |   |   |   |   |   |
|---|---|---|--|---|---|---|--|---|---|---|---|---|---|
| 1 | 0 | 0 |  | 1 | 0 | 1 |  | X | 0 | 0 | X | 1 | X |
| 1 | 0 | 1 |  | 1 | 1 | 0 |  | X | 0 | 1 | X | X | 1 |
| 1 | 1 | 0 |  | 1 | 1 | 1 |  | X | 0 | X | 0 | 1 | X |
| 1 | 1 | 1 |  | 0 | 0 | 0 |  | X | 1 | X | 1 | X | 1 |

Step 5

| $Q_A$ | $Q_B Q_C$ | 00 | 01 | 11  | 10 |
|-------|-----------|----|----|-----|----|
| 0     |           |    |    | (1) |    |
| 1     |           | X  | X  | (X) | X  |

| $Q_A$ | $Q_B Q_C$ | 00 | 01 | 11  | 10 |
|-------|-----------|----|----|-----|----|
| 0     |           |    |    | (X) | X  |
| 1     |           | X  | X  | (X) | X  |

$J_A = Q_B Q_C$

$K_A = Q_B Q_C$

| $Q_A$ | $Q_B Q_C$ | 00  | 01  | 11 | 10 |
|-------|-----------|-----|-----|----|----|
| 0     |           |     | (1) | X  | X  |
| 1     |           | (1) | X   | X  | X  |

| $Q_A$ | $Q_B Q_C$ | 00 | 01 | 11  | 10  |
|-------|-----------|----|----|-----|-----|
| 0     |           |    | X  | X   | (1) |
| 1     |           | X  | X  | (X) | X   |

$J_B = Q_C$


$K_B = Q_C$

| $Q_A$ | $Q_B Q_C$ | 00  | 01 | 11 | 10  |
|-------|-----------|-----|----|----|-----|
| 0     |           | (1) | X  | X  | (1) |
| 1     |           | (1) | X  | X  | (1) |

| $Q_A$ | $Q_B Q_C$ | 00 | 01  | 11 | 10 |
|-------|-----------|----|-----|----|----|
| 0     |           | X  | (1) | 1  | X  |
| 1     |           | X  | (1) | 1  | X  |


$J_C = 1$

$K_C = 1$

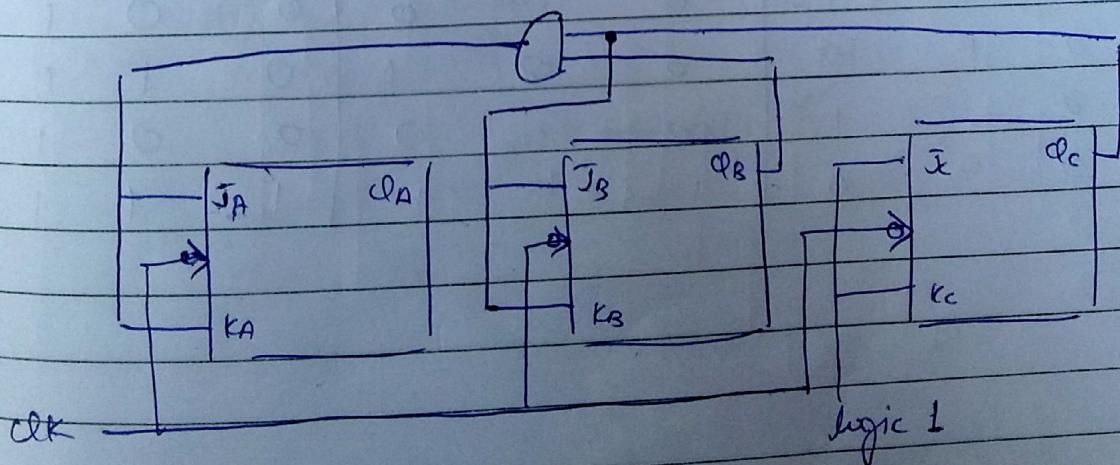

3 bit down counter

using T

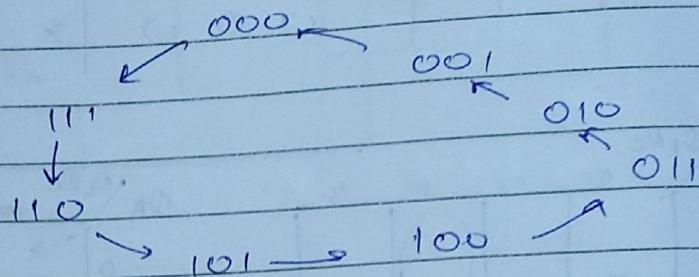


$n = 3$

| $Q_0$ | $Q_{n+1}$ | T |
|-------|-----------|---|
| 0     | 0         | 0 |
| 0     | 1         | 1 |
| 1     | 0         | 1 |
| 1     | 1         | 0 |

RS


NB

| $Q_A$ | $Q_B$ | $Q_C$ | $Q_{A+1}$ | $Q_{B+1}$ | $Q_{C+1}$ | $T_A$ | $T_B$ | $T_C$ |
|-------|-------|-------|-----------|-----------|-----------|-------|-------|-------|
| 1     | 1     | 1     | 1         | 1         | 0         | 0     | 0     | 1     |
| 1     | 1     | 0     | 1         | 0         | 1         | 0     | 1     | 1     |
| 1     | 0     | 1     | 1         | 0         | 0         | 0     | 0     | 1     |
| 1     | 0     | 0     | 0         | 1         | 1         | 1     | 1     | 1     |
| 0     | 1     | 1     | 0         | 1         | 0         | 0     | 0     | 1     |
| 0     | 1     | 0     | 0         | 0         | 1         | 0     | 1     | 1     |
| 0     | 0     | 1     | 0         | 0         | 0         | 0     | 0     | 1     |
| 0     | 0     | 0     | 1         | 1         | 1         | 1     | 1     | 1     |

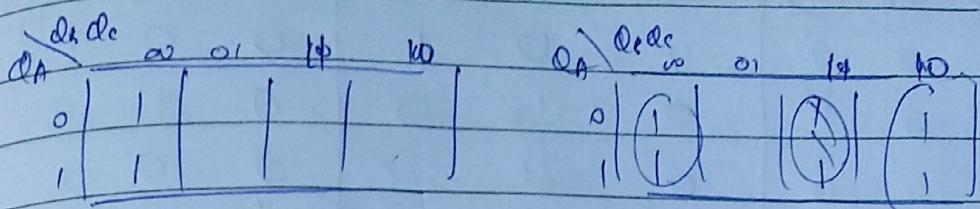

$$T_A = \bar{Q}_B \bar{Q}_C$$

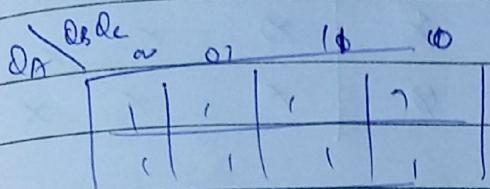
~~$$T_B = \bar{Q}_A \bar{Q}_C + \bar{Q}_B \bar{Q}_C \quad T_B = \bar{Q}_C$$~~



$$T_C = 1$$


| <u><math>T_A</math></u> | <u><math>T_B</math></u> | <u><math>T_C</math></u> |
|-------------------------|-------------------------|-------------------------|
| $T_A$                   | $T_B$                   | $T_C$                   |

Mod-5 counter      up counter

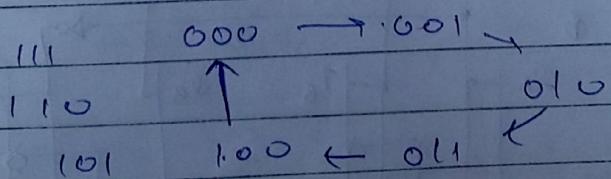


| $Q_n$ | $Q_{n+1}$ | $T$ |
|-------|-----------|-----|
| 0     | 0         | 0   |
| 0     | 1         | 1   |
| 1     | 0         | 1   |
| 1     | 1         | 0   |

| $d_A$ | $d_B$ | $d_C$ | $d_{A+1}$ | $d_{B+1}$ | $d_{C+1}$ | $T_A$ | $T_B$ | $T_C$ |
|-------|-------|-------|-----------|-----------|-----------|-------|-------|-------|
| 0     | 0     | 0     | 0         | 0         | 1         | 0     | 0     | 1     |
| 0     | 0     | 1     | 0         | 1         | 0         | 0     | 1     | 1     |
| 0     | 1     | 0     | 0         | 1         | 1         | 0     | 0     | 1     |
| 0     | 1     | 1     | 1         | 0         | 0         | 1     | 1     | 1     |
| 1     | 0     | 0     | 0         | 0         | 0         | 0     | 0     | 0     |
| 1     | 0     | 1     | *         | *         | *         | *     | x     | x     |
| 1     | 1     | 0     | *         | *         | *         | *     | x     | x     |
| 1     | 1     | 1     | *         | *         | *         | *     | x     | x     |

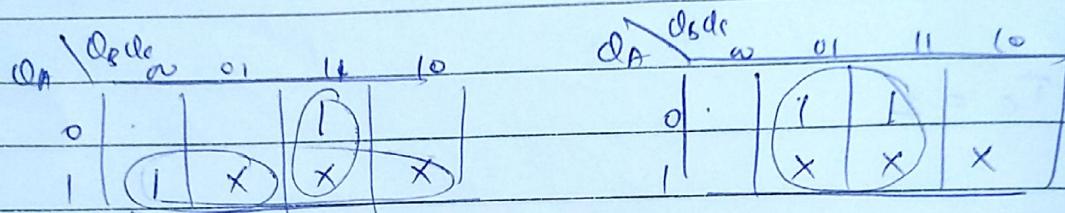

$$T_A = d_A \otimes \bar{d}_B + d_B \otimes \bar{d}_C$$

$$T_B = d_C$$

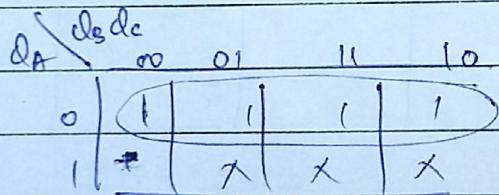

$d_A \setminus d_B \setminus T$


0 0. 0

0 1. 1.

1 0. 1



1 1. 0

$$T_C = \overline{d_A}$$

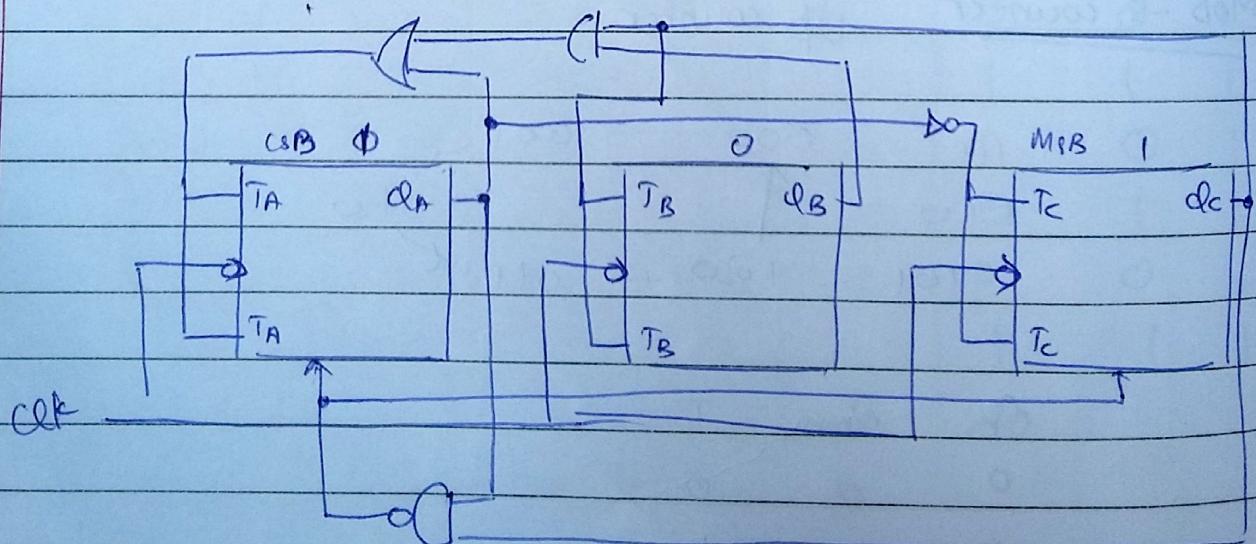


Design a MOD-6 Gray counter using T-flip flop

| $Q_A$ | $Q_B$ | $Q_C$ | $Q_{A+1}$ | $Q_{B+1}$ | $Q_{C+1}$ | $T_A$ | $T_B$ | $T_C$ |
|-------|-------|-------|-----------|-----------|-----------|-------|-------|-------|
| 0     | 0     | 0     | 0         | 0         | 1         | 0     | 0     | 1     |
| 0     | 0     | 1     | 0         | 1         | 1         | 0     | 1     | 0     |
| 0     | 1     | 1     | 0         | 1         | 0         | 0     | 0     | 1     |
| 0     | 1     | 0     | 1         | 1         | 0         | 1     | 0     | 0     |
| 1     | 1     | 0     | 1         | 1         | 1         | 0     | 0     | 1     |
| 1     | 1     | 1     | 0         | 0         | 0         | 1     | 1     | 1     |
| 1     | 0     | 1     | x         | x         | x         | x     | x     | x     |
| 1     | 0     | 0     | x         | x         | x         | x     | x     | x     |

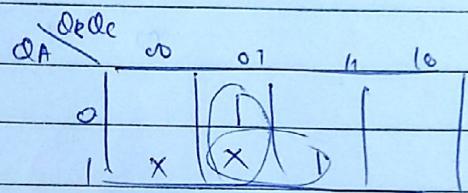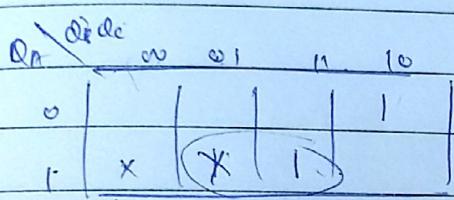


$$T_A = Q_A \bar{Q}_C + \bar{Q}_A Q_B \bar{Q}_C$$

$$T_B = Q_A \cdot Q_C + \bar{Q}_B Q_C$$

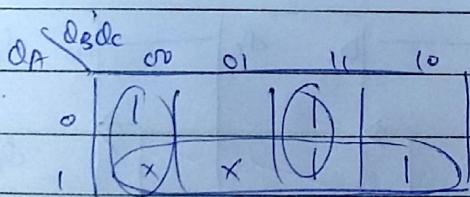


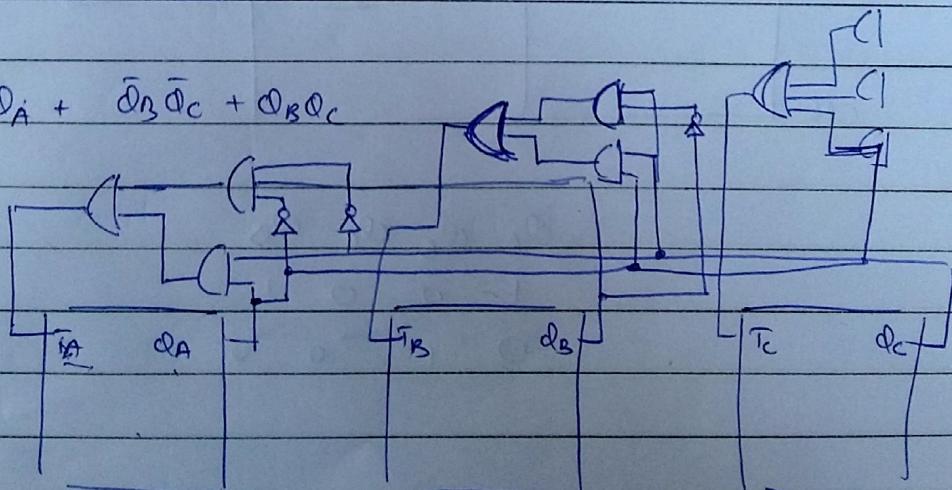
$$T_C = Q_A + \bar{Q}_B \bar{Q}_C + Q_B Q_C$$



Preset  $\rightarrow$  1  
Clear  $\rightarrow$  0

Date \_\_\_\_\_  
Page \_\_\_\_\_

## Ring Counter

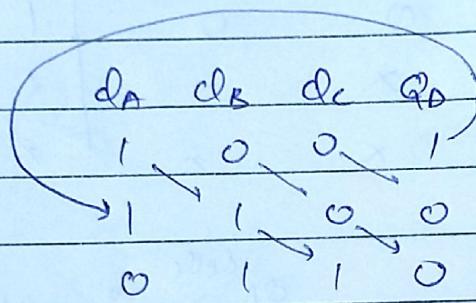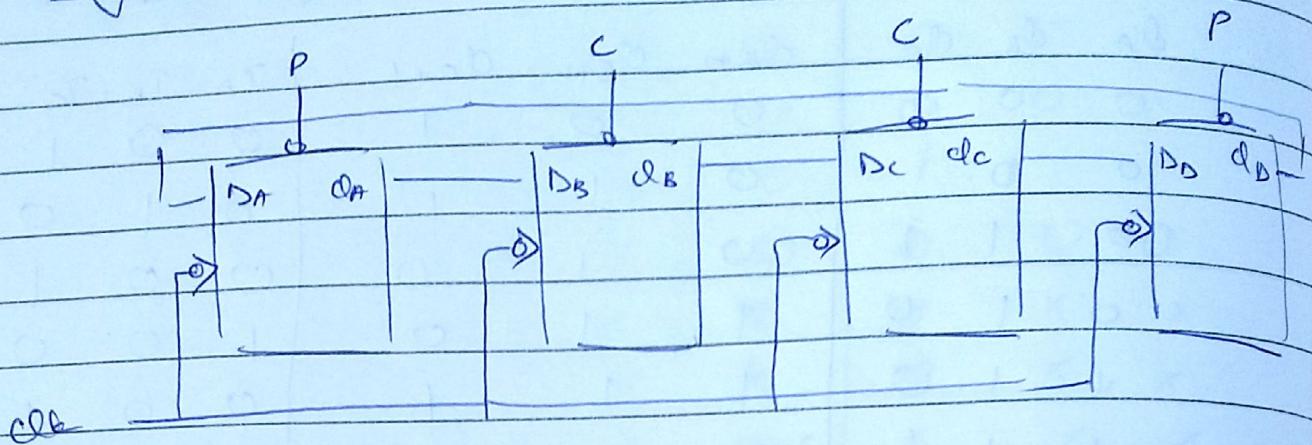

## Johnson Counter

